

## Chapter 7: Microarchitecture

# **Multicycle RISC-V Processor**

# Single- vs. Multicycle Processor

- **Single-cycle:**
  - + simple
  - cycle time limited by longest instruction ( $1_w$ )
  - separate memories for instruction and data
  - 3 adders/ALUs
- **Multicycle processor** addresses these issues by breaking instruction into **shorter steps**
  - shorter instructions take fewer steps
  - can re-use hardware
  - cycle time is faster

# Single- vs. Multicycle Processor

- **Single-cycle:**

- + simple
- cycle time limited by longest instruction ( $t_w$ )
- separate memories for instruction and data
- 3 adders/ALUs

- **Multicycle:**


- + higher clock speed
- + simpler instructions run faster
- + reuse expensive hardware on multiple cycles
- sequencing overhead paid many times

**Same design steps  
as single-cycle:**

- **first datapath**
- **then control**

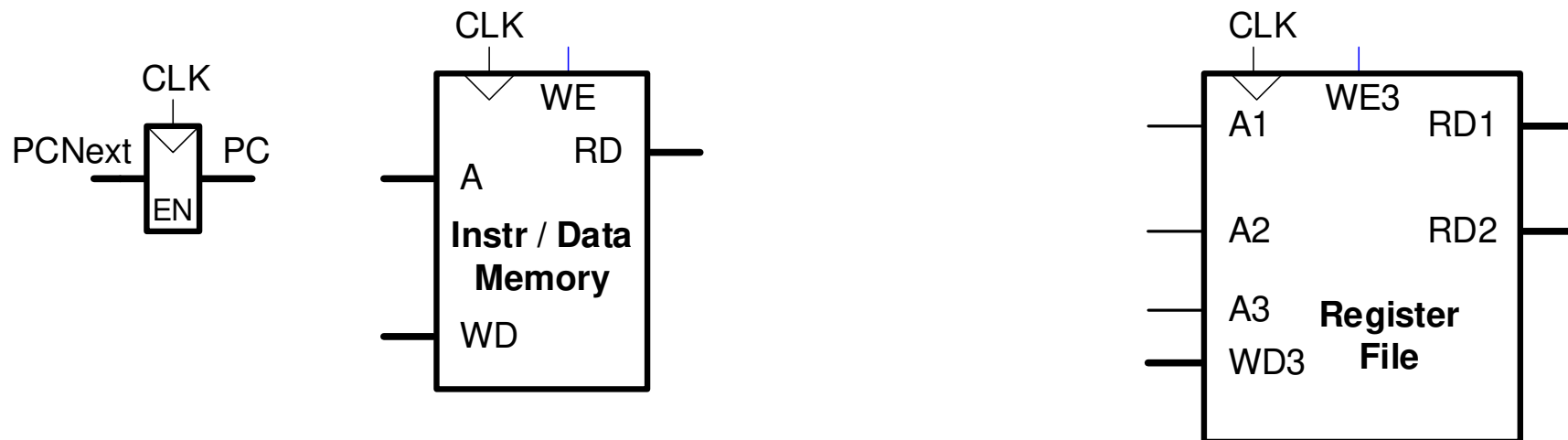
# Multicycle State Elements

Replace separate Instruction and Data memories with a **single unified memory** – more realistic




# Multicycle Datapath: Instruction Fetch

## STEP 1: Fetch instruction

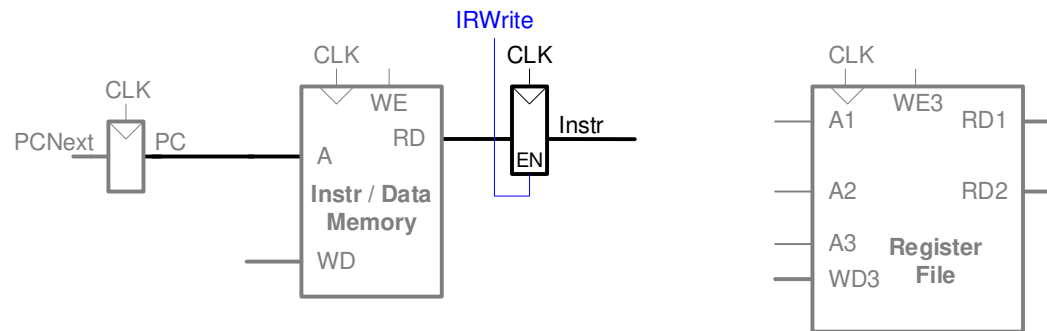

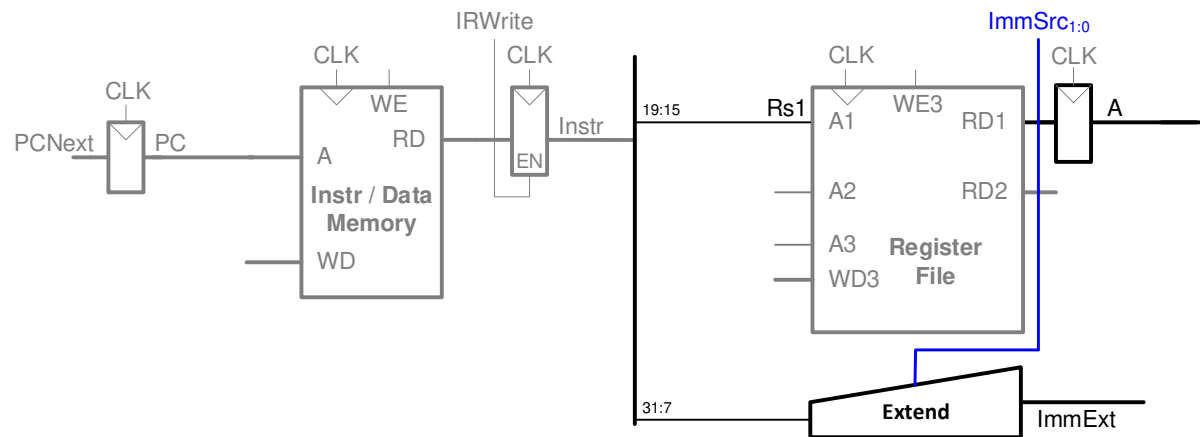
# Multicycle Datapath: $1_w$ Get Sources

**STEP 2:** Read source operand from RF and extend immediate




# Multicycle Datapath: $1_w$ Address

## STEP 3: Compute the memory address

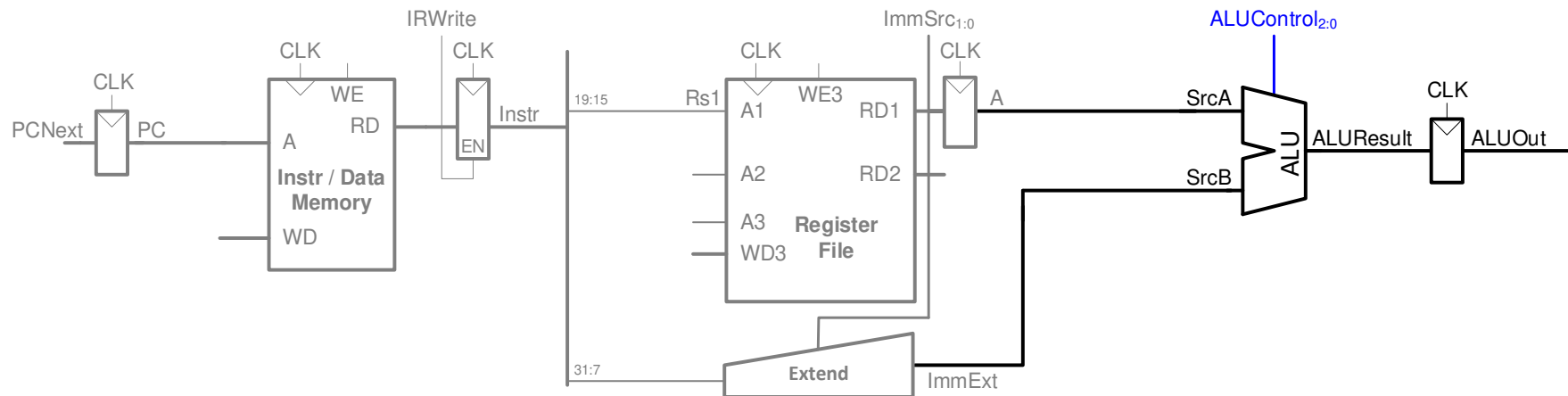

# Multicycle Datapath: $1_w$ Memory Read


## STEP 4: Read data from memory

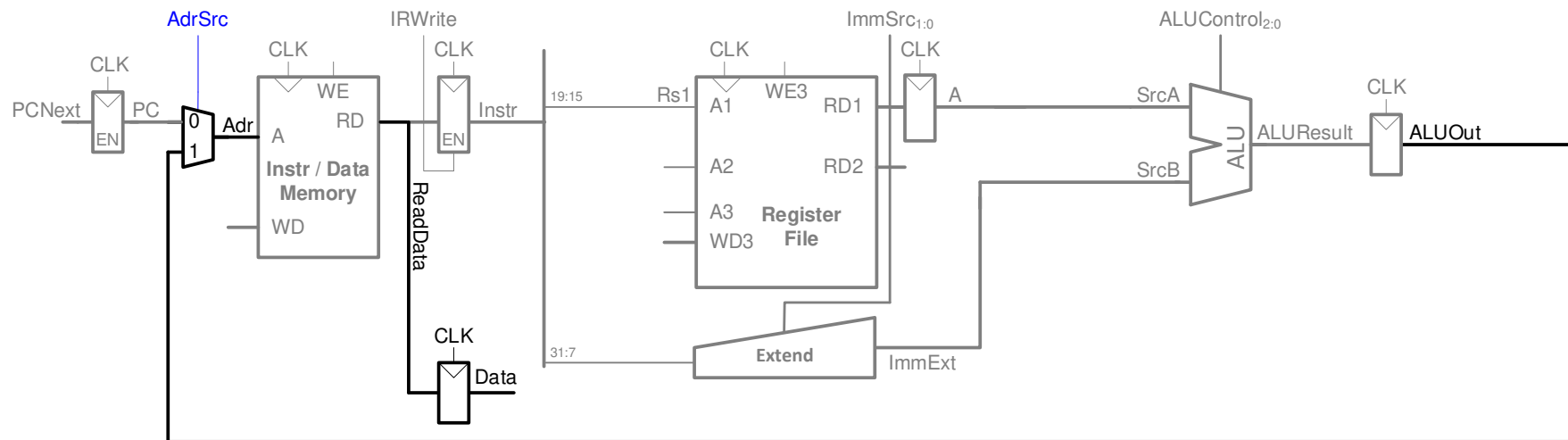




# Multicycle Datapath: $1_W$ Write Register
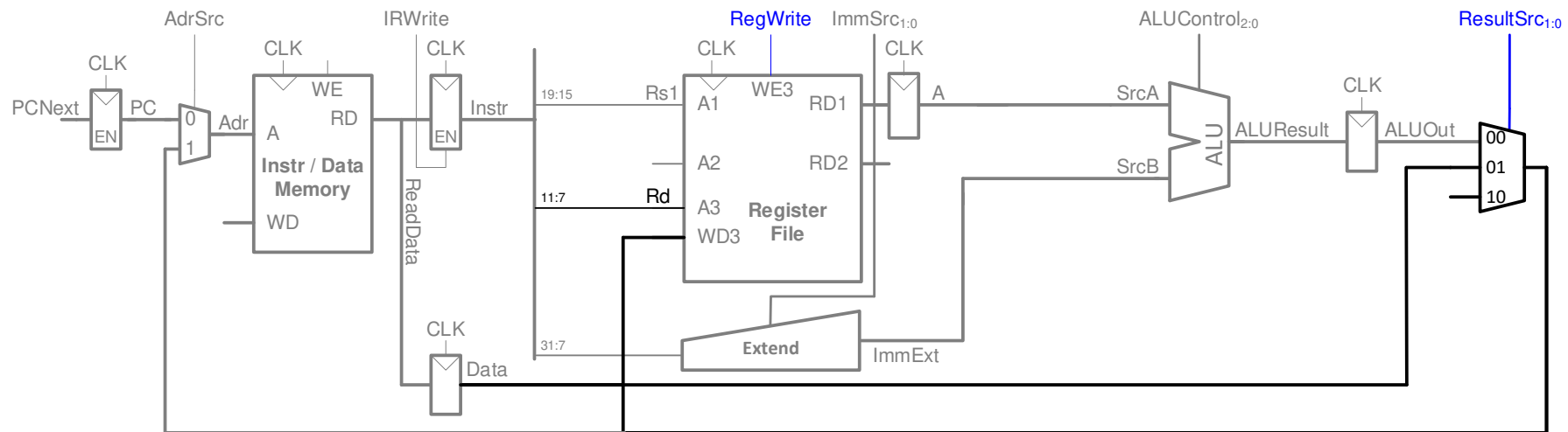
## STEP 5: Write data back to register file



# Multicycle Datapath: Increment PC

## STEP 6: Increment PC: $PC = PC + 4$

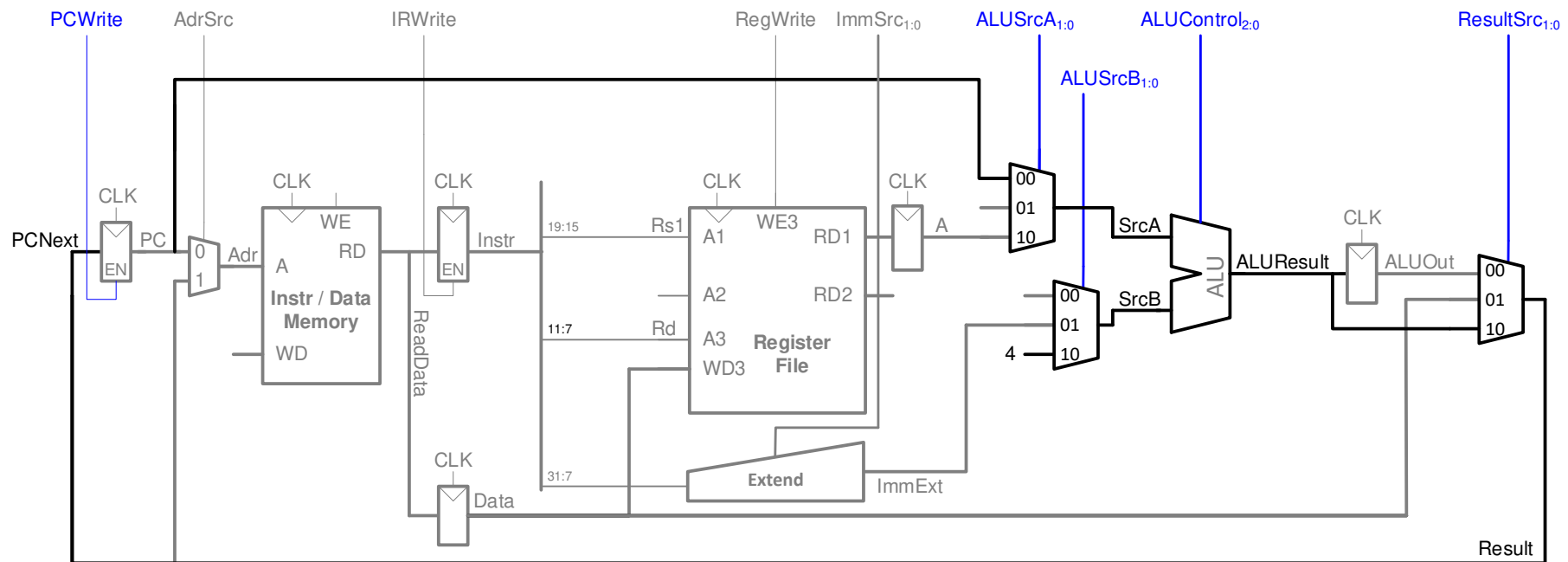


## Chapter 7: Microarchitecture

# **Multicycle Datapath: Other Instructions**

# Multicycle Datapath: $sw$


Write data in **rs2** to memory

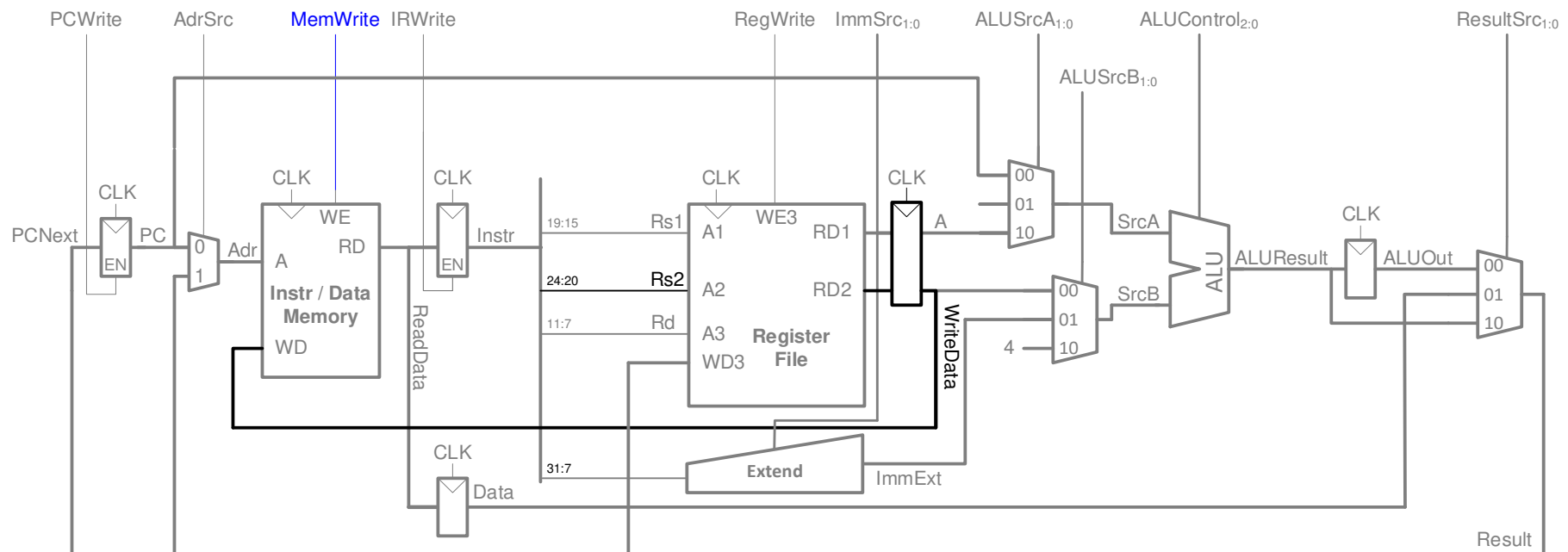

# Multicycle Datapath: beq


Calculate branch target address:

$$\text{BTA} = \text{PC} + \text{imm}$$

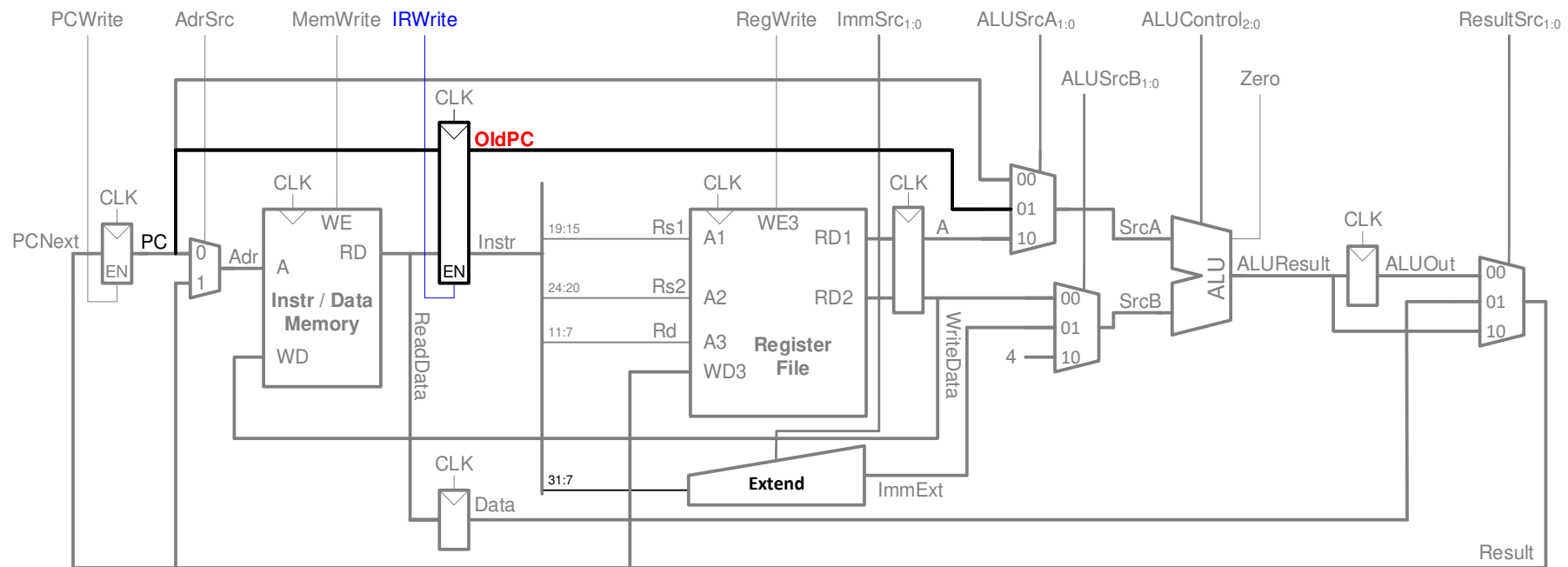

PC is updated in Fetch stage, so need to save **old (current) PC**

# Multicycle RISC-V Processor

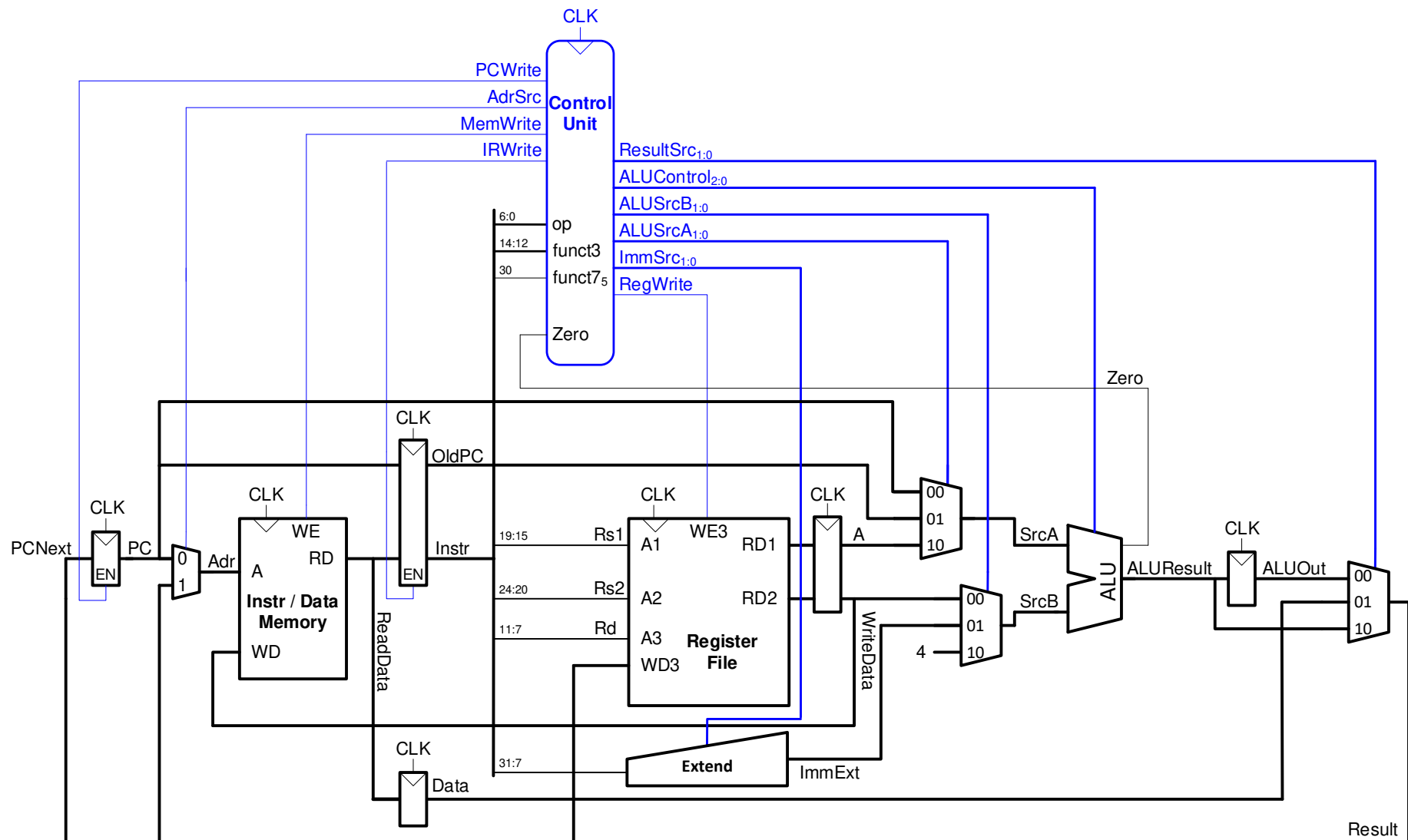


## Chapter 7: Microarchitecture


# **Multicycle Control**

# Multicycle Control

## High-Level View

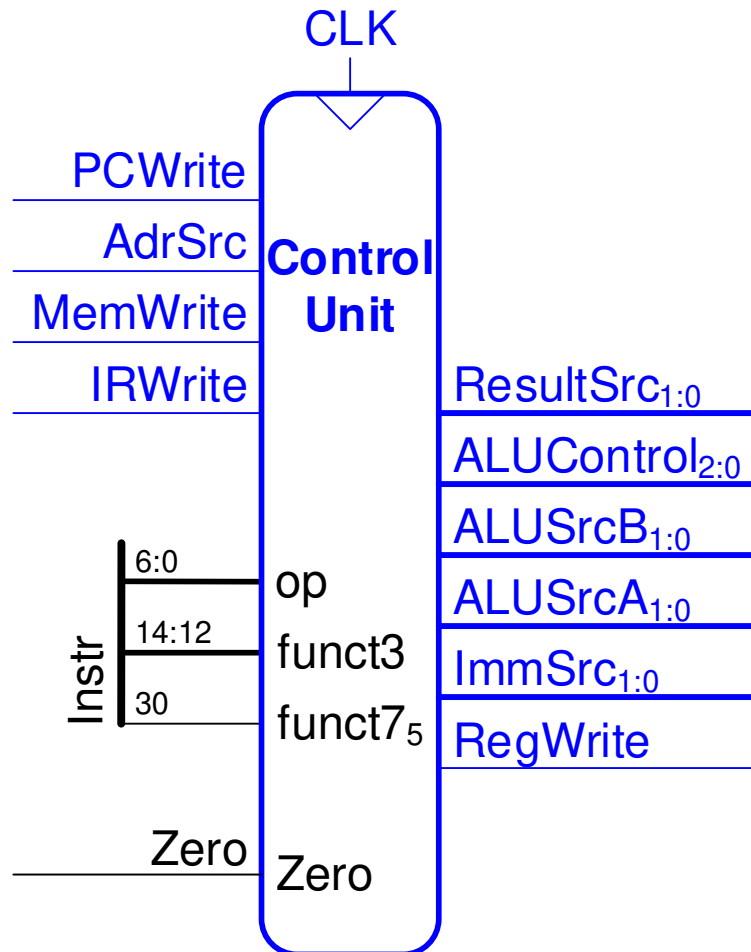


## Low-Level View

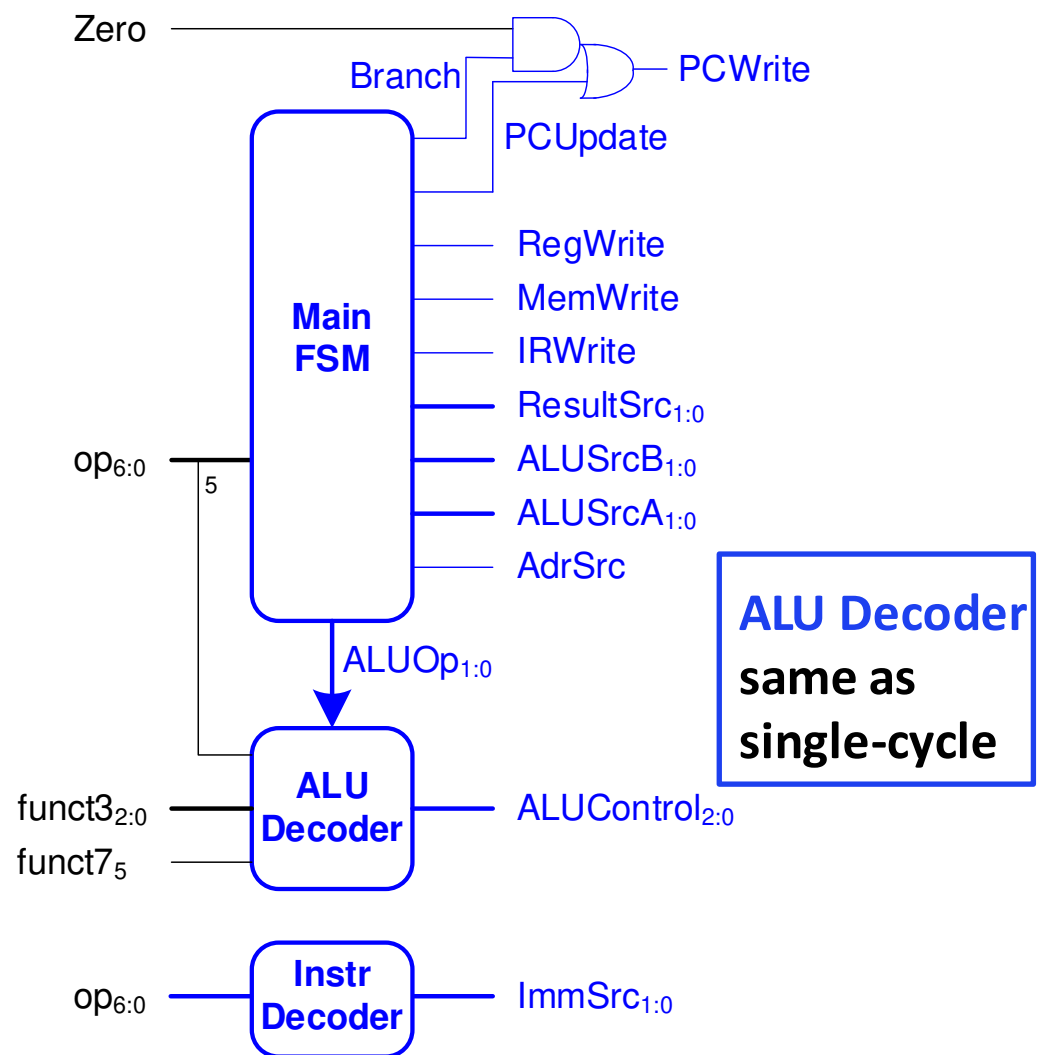



 
# Multicycle Control: Instruction Decoder



op	Instruction	ImmSrc
3	lw	00
35	sw	01
51	R-type	XX
99	beq	10


# Multicycle Control: Main FSM

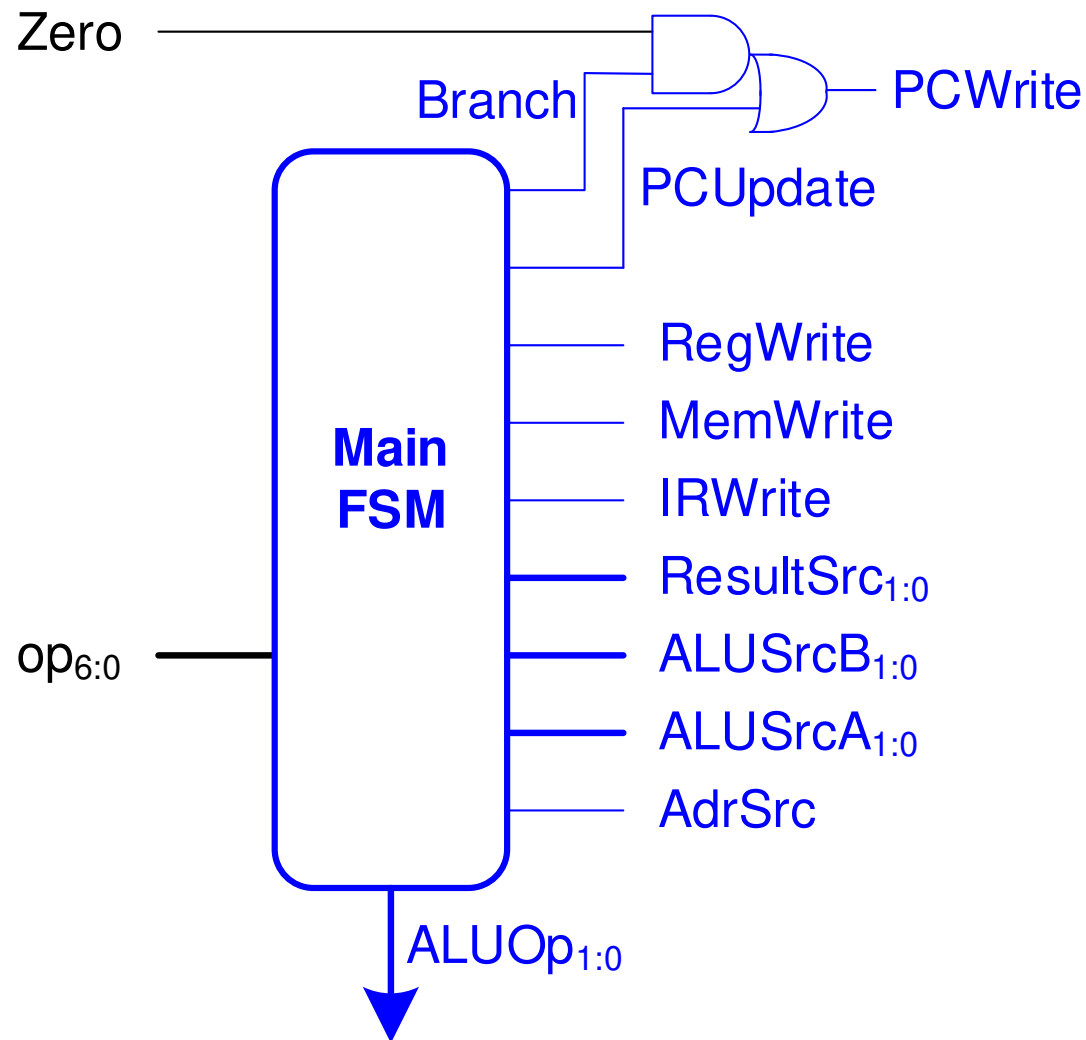


## To declutter FSM:

- **Write enable signals** (RegWrite, MemWrite, IRWrite, PCUpdate, and Branch) are **0** if not listed in a state.
- **Other signals are don't care** if not listed in a state


# Main FSM: Fetch

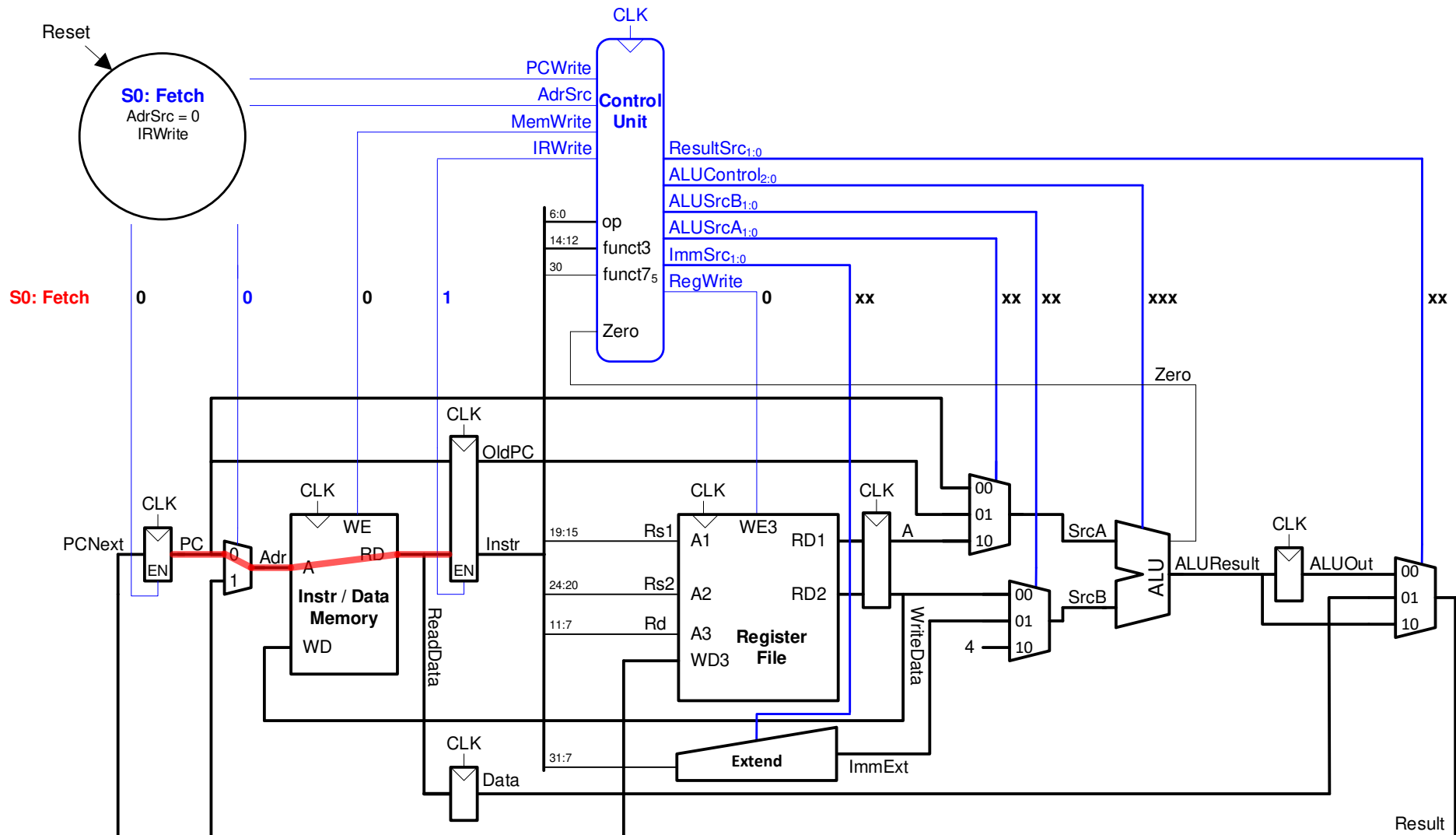


# Main FSM: Decode

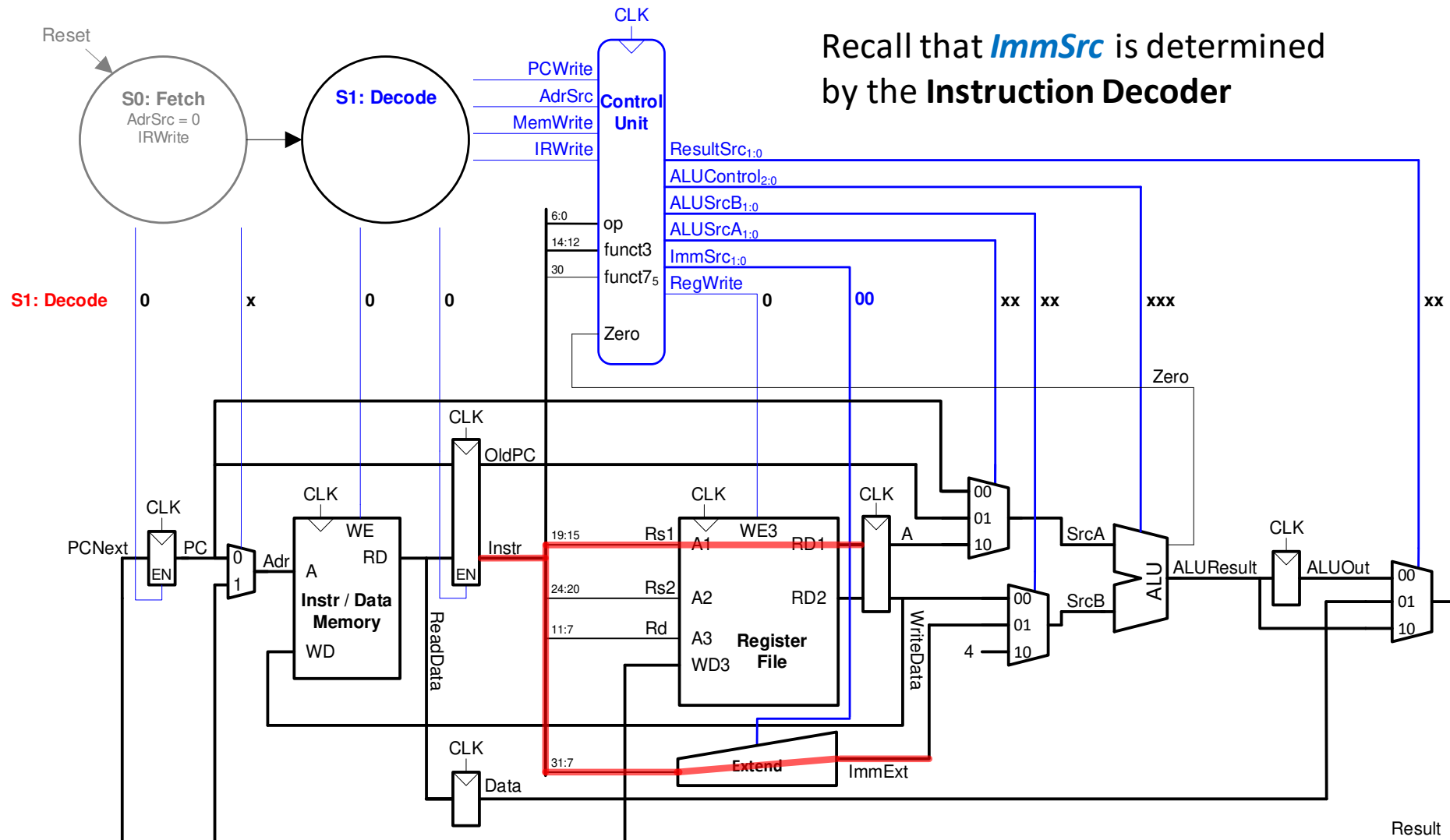


# Main FSM: Address

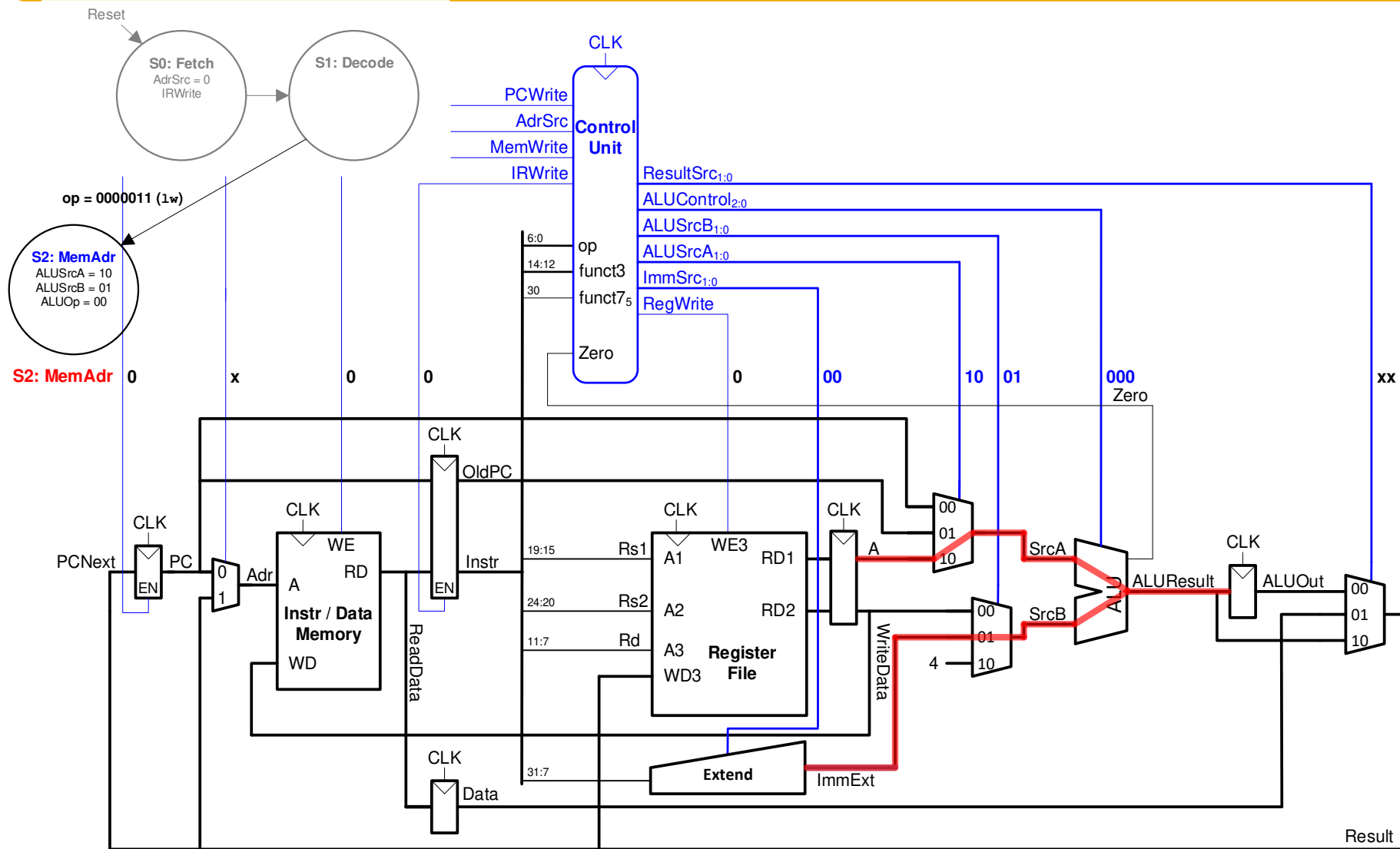


# Main FSM: Read Memory

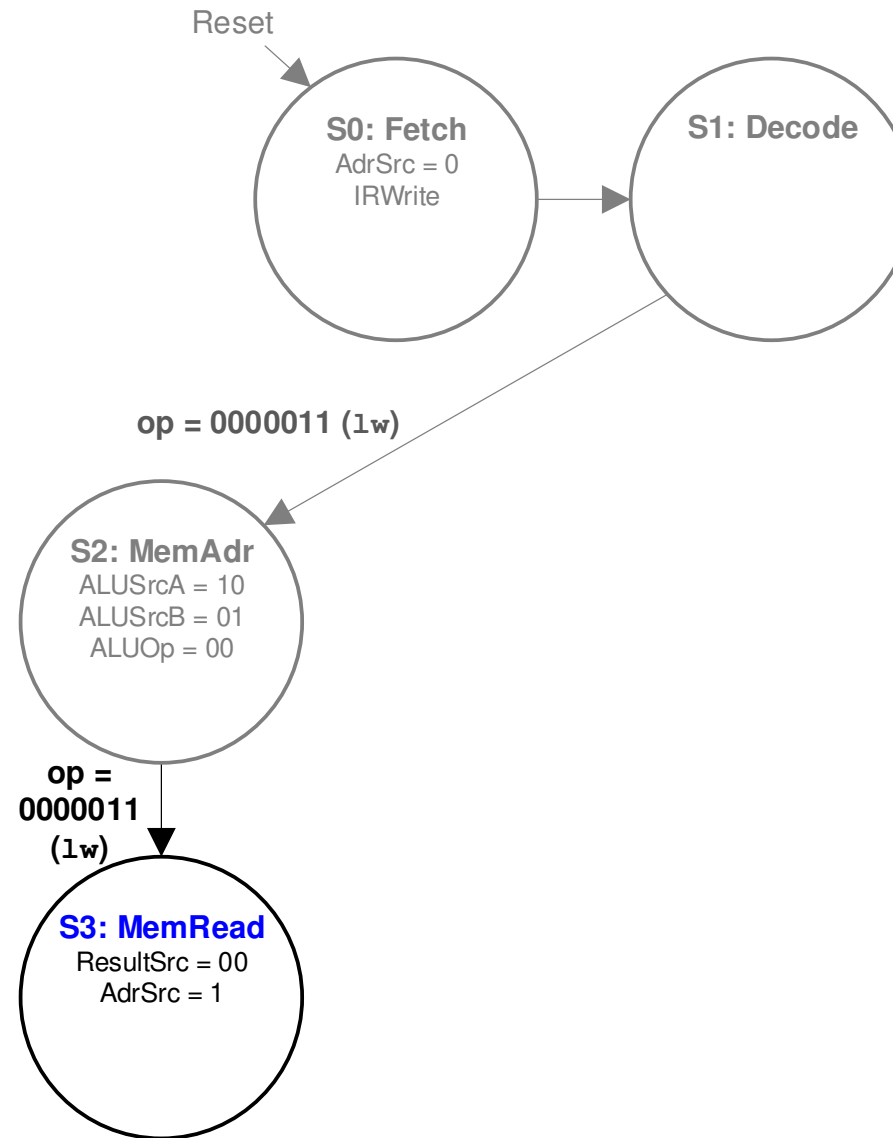

# Main FSM: Read Memory Datapath

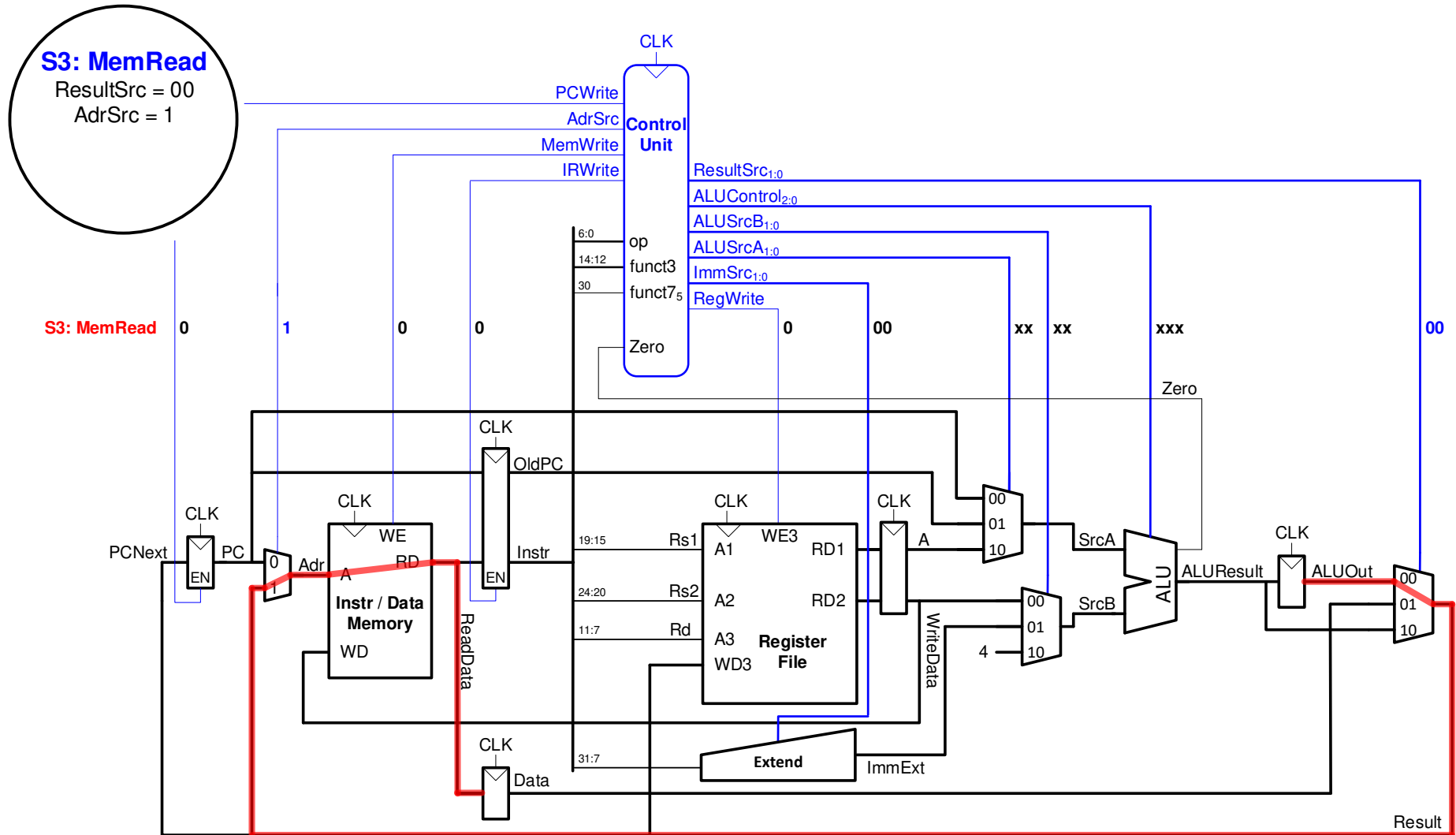


# Main FSM: Write RF

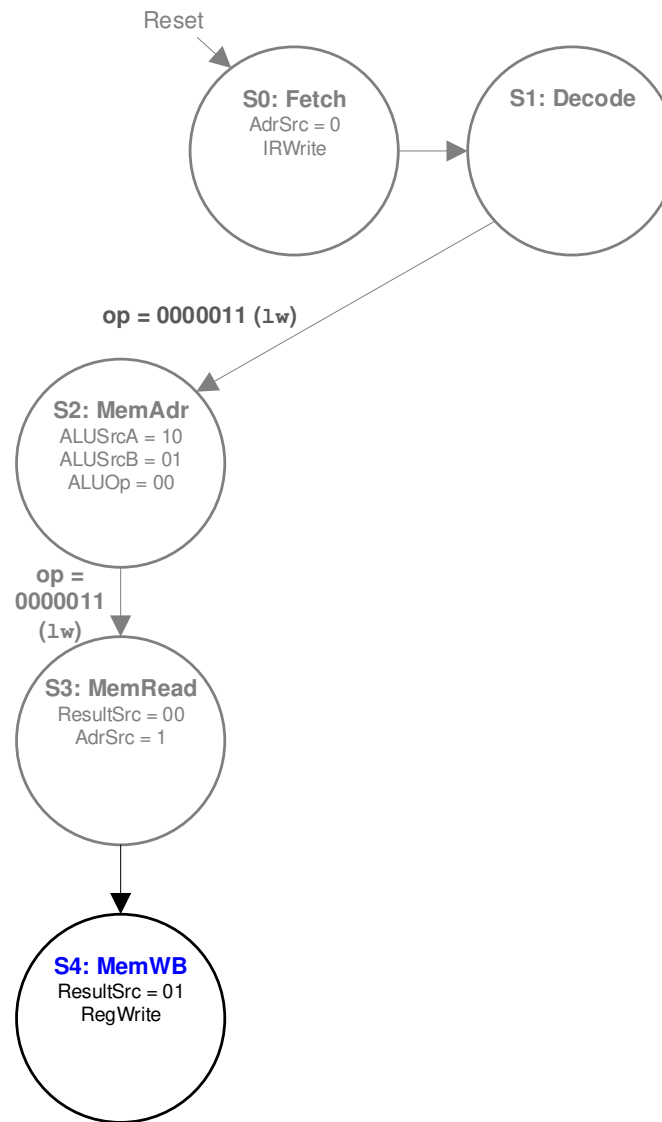




# Main FSM: Write RF Datapath

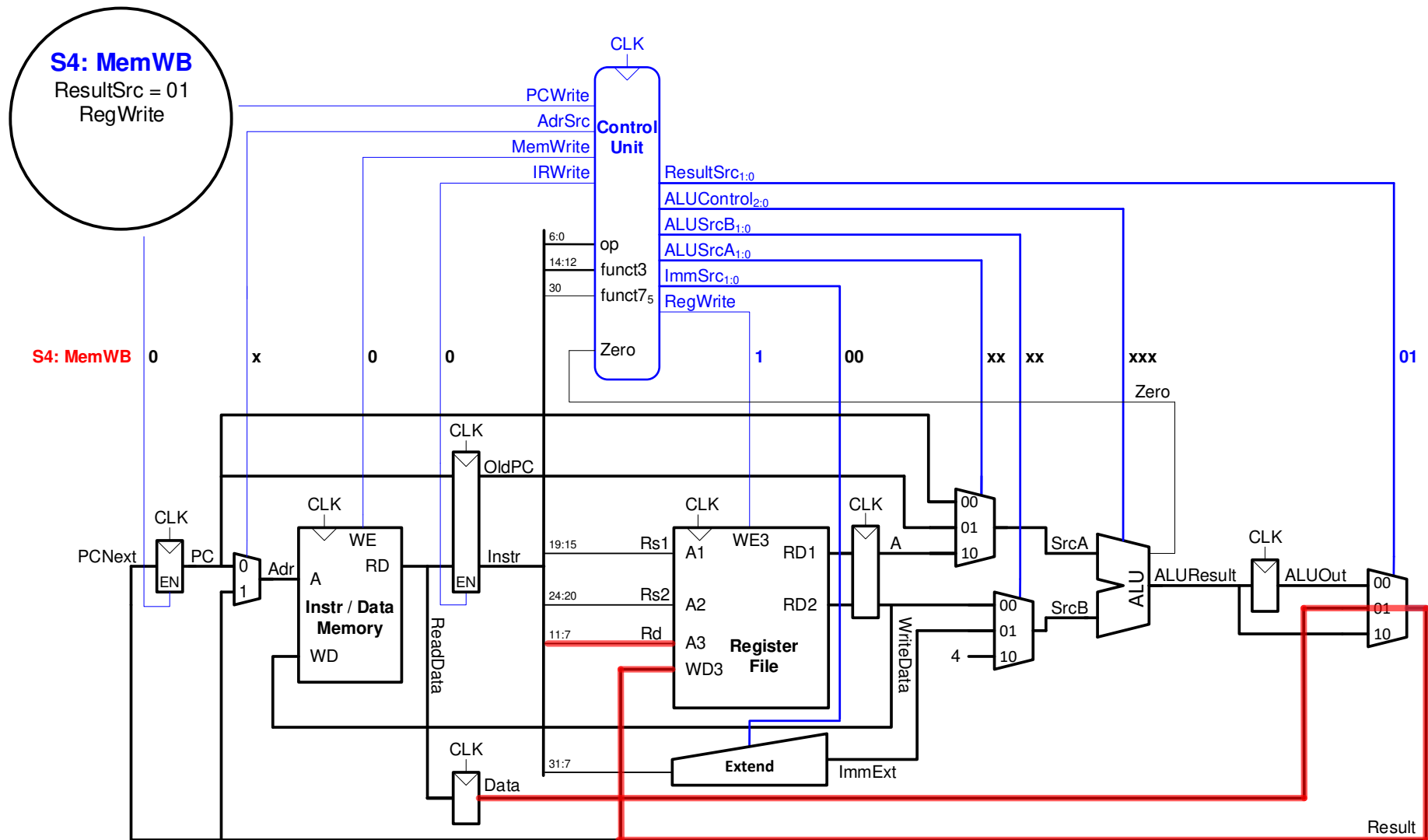

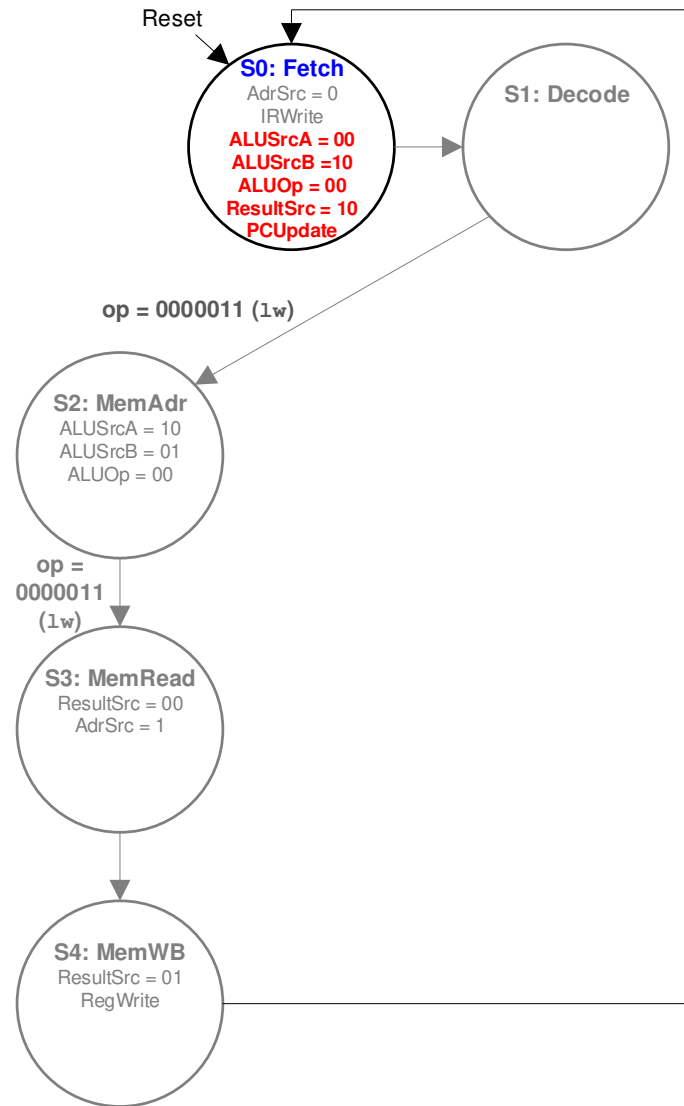
# Main FSM: Fetch Revisited

Calculate **PC+4**  
during Fetch stage  
(ALU isn't being  
used)




# Main FSM: Fetch (PC+4) Datapath

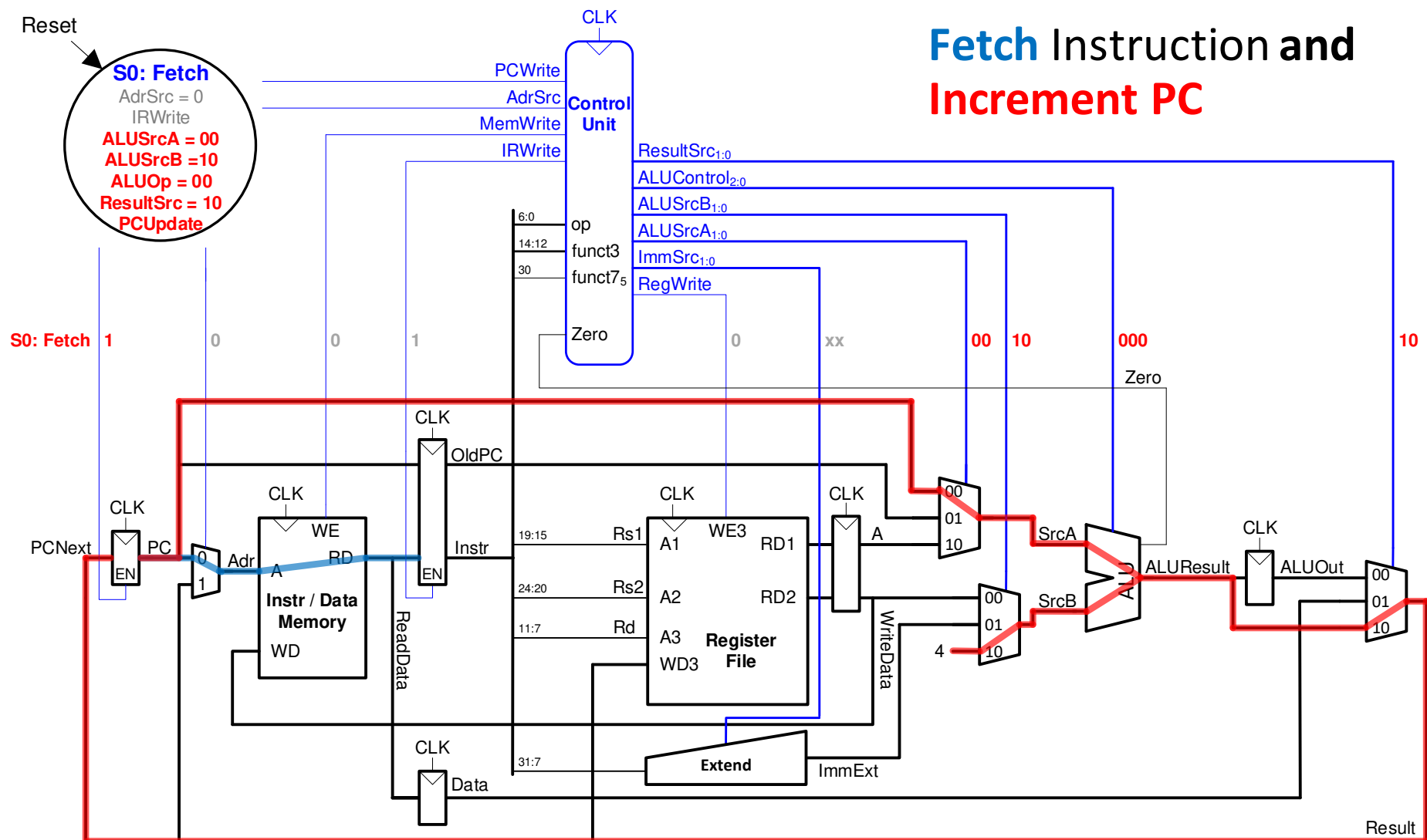


## Chapter 7: Microarchitecture

# **Multicycle Control: Other Instructions**


# Main FSM: sw

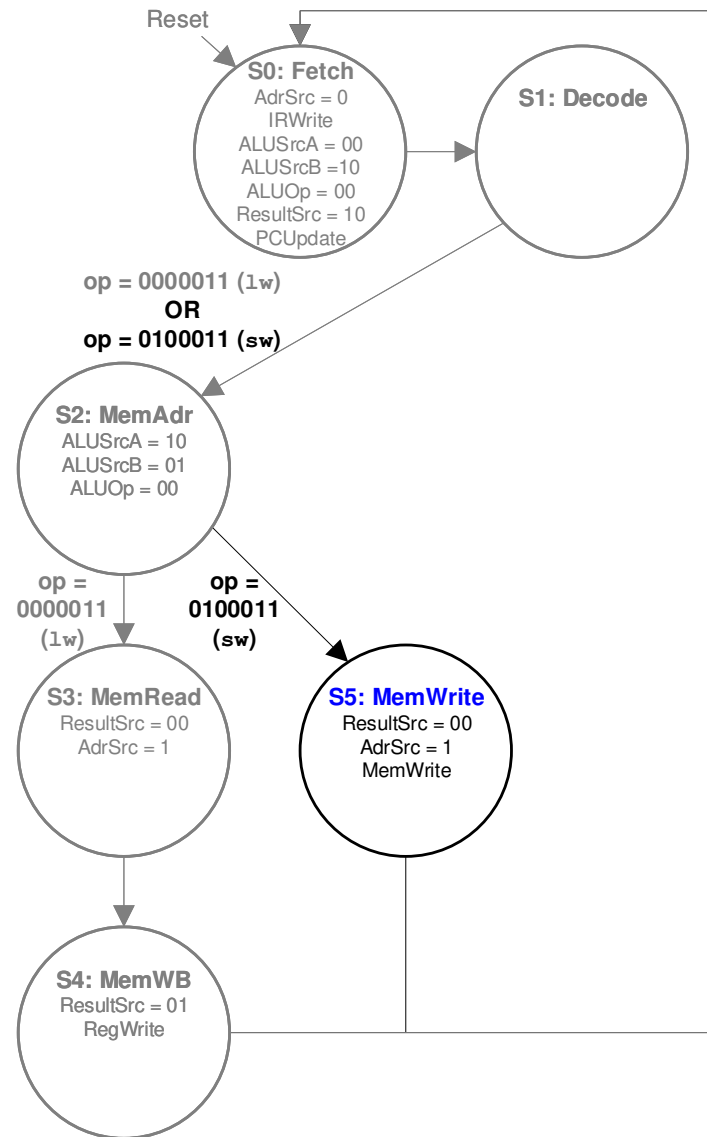


# Main FSM: sw Datapath

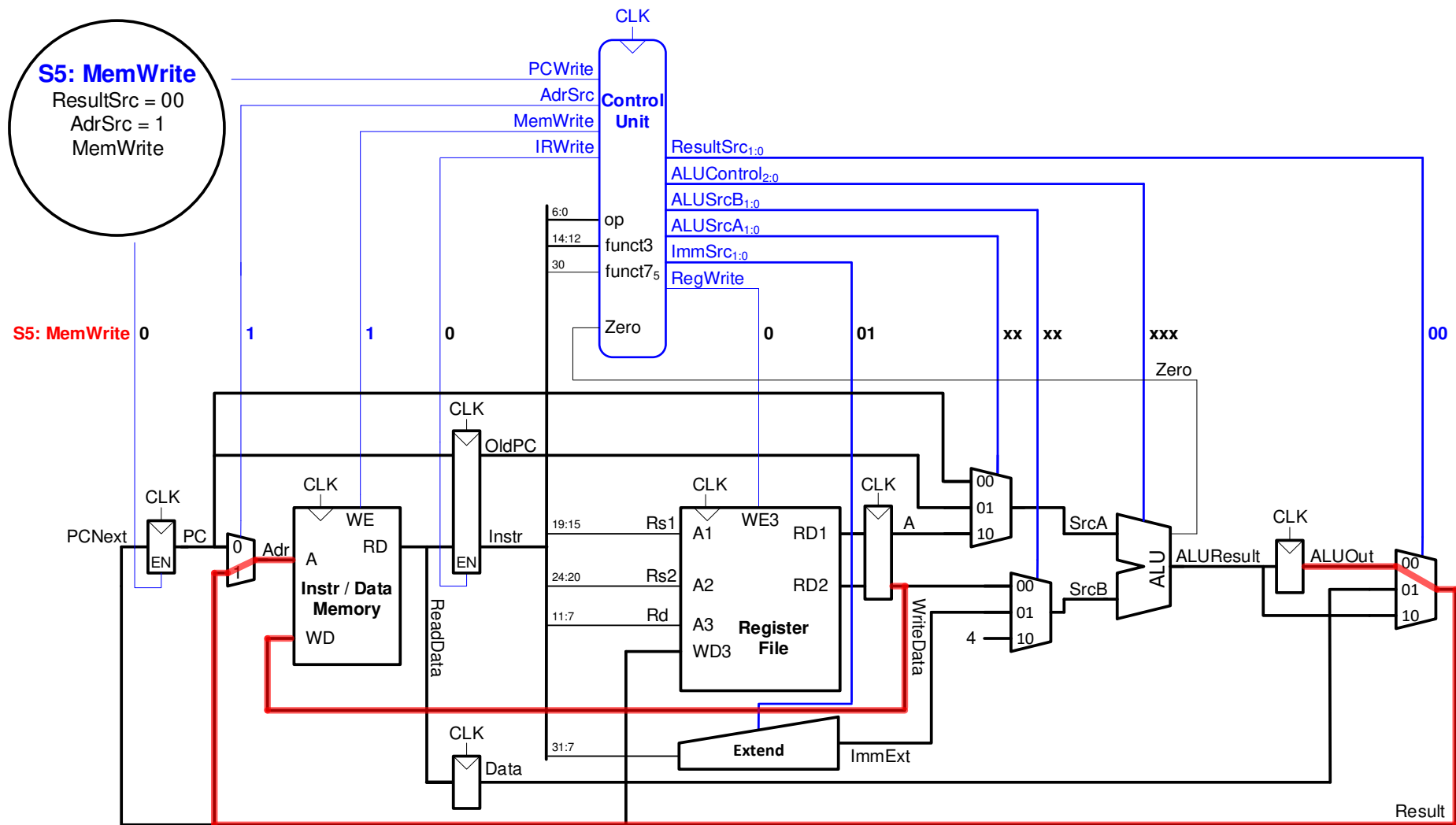

# Main FSM: R-Type Execute

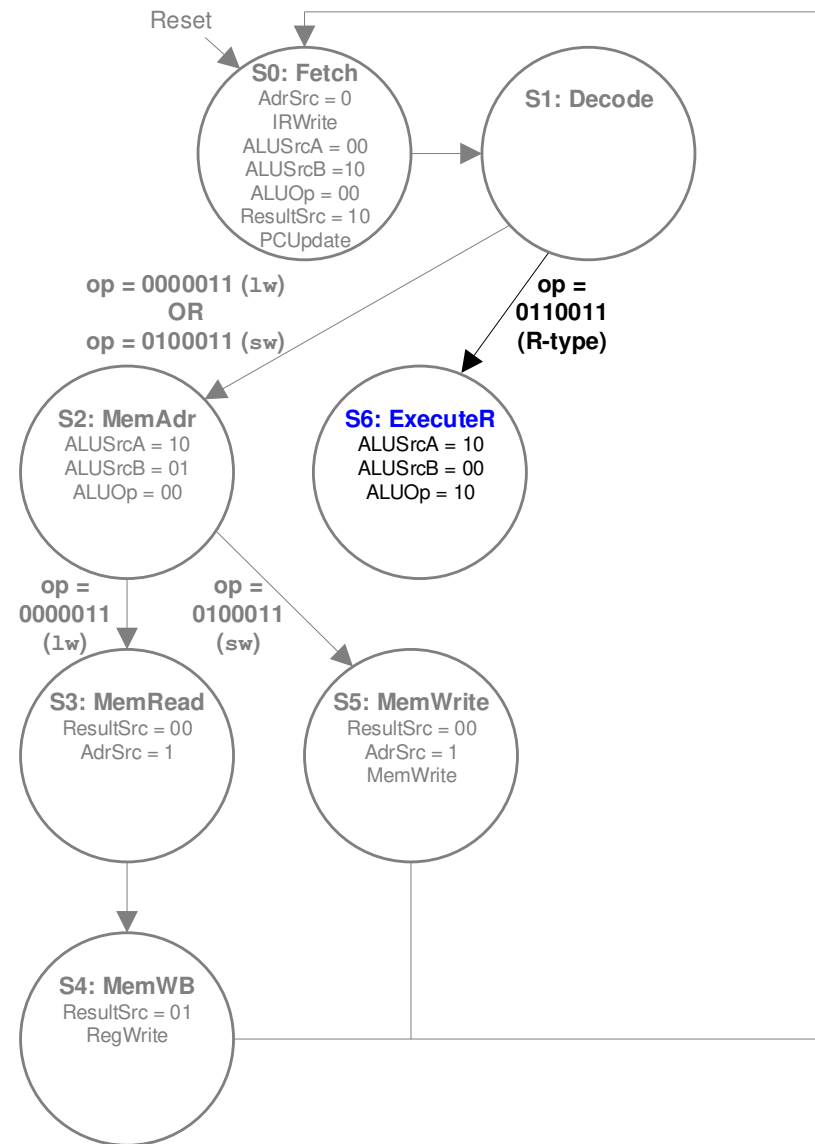


# Main FSM: R-Type Execute Datapath

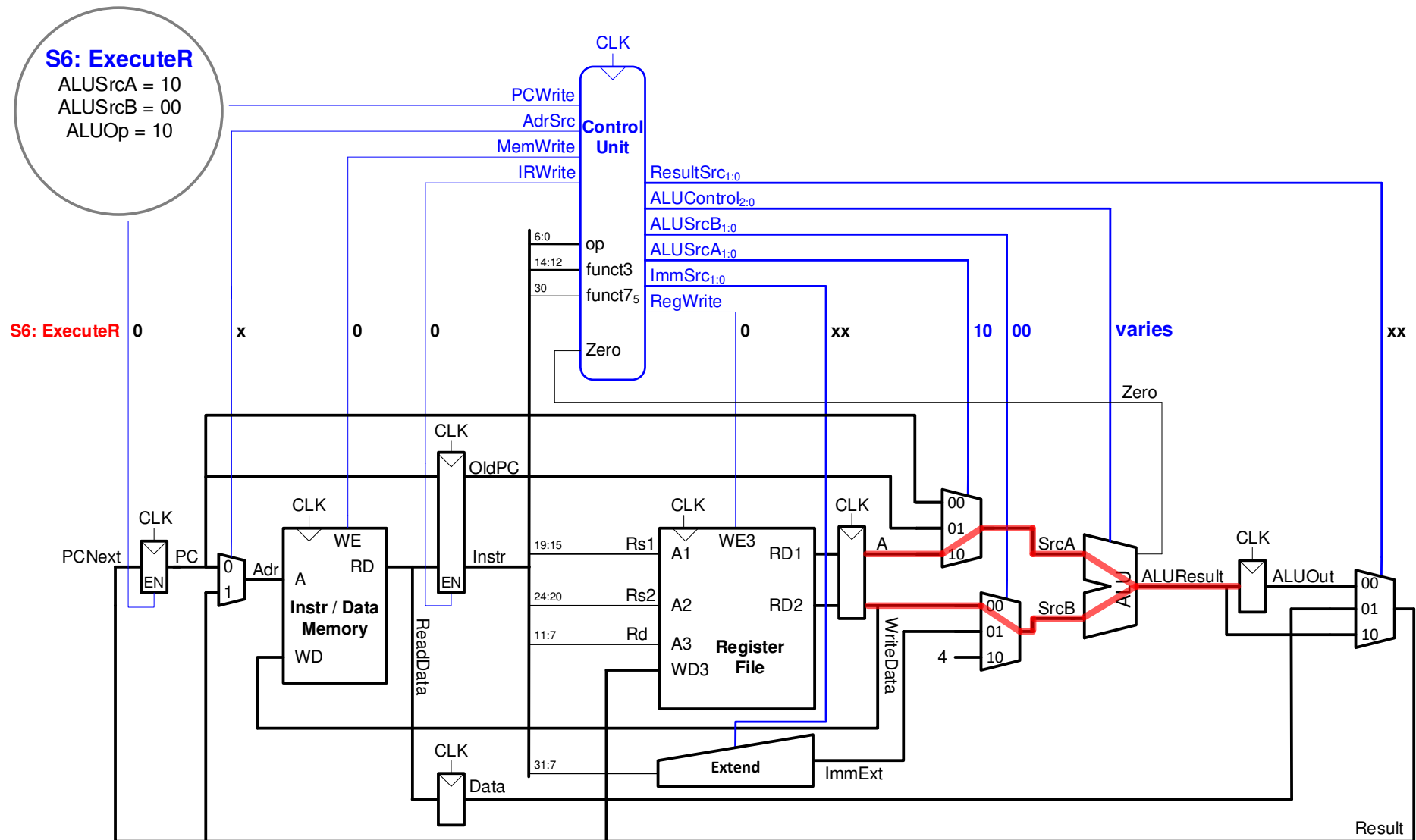




# Main FSM: R-Type ALU Write Back

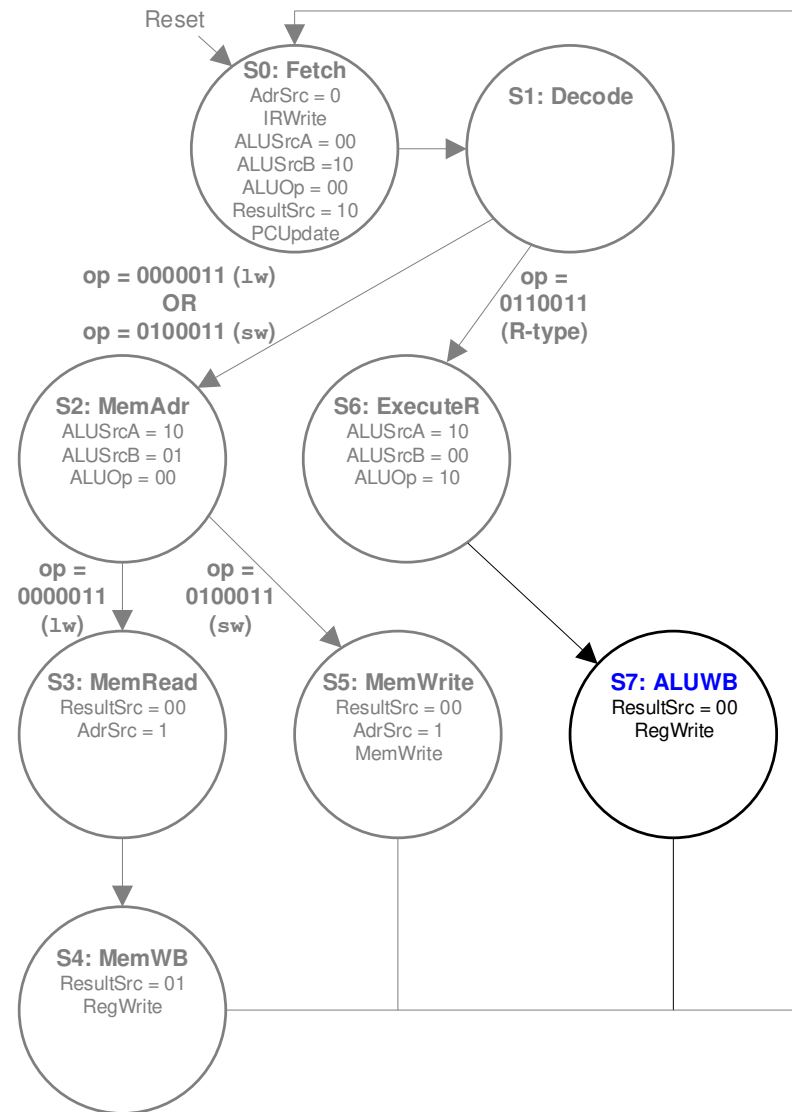


# Main FSM: R-Type ALU Write Back

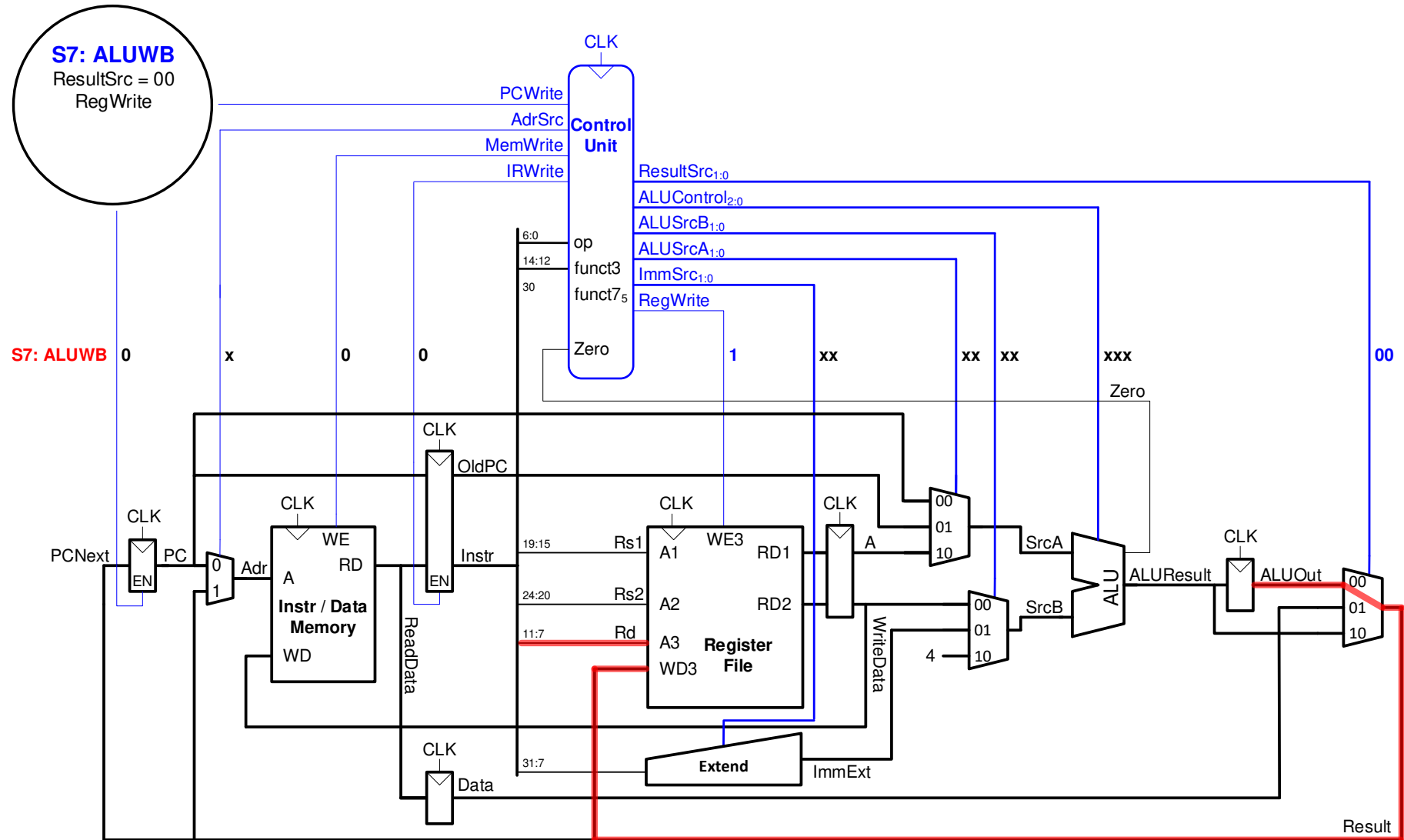


# Main FSM: beq

- **Need to calculate:**
  - Branch Target Address
  - **rs1** - **rs2** (to see if equal)
- **ALU** isn't being used in Decode stage
  - Use it to calculate Target Address ( $PC + imm$ )


# Main FSM: Decode Revisited

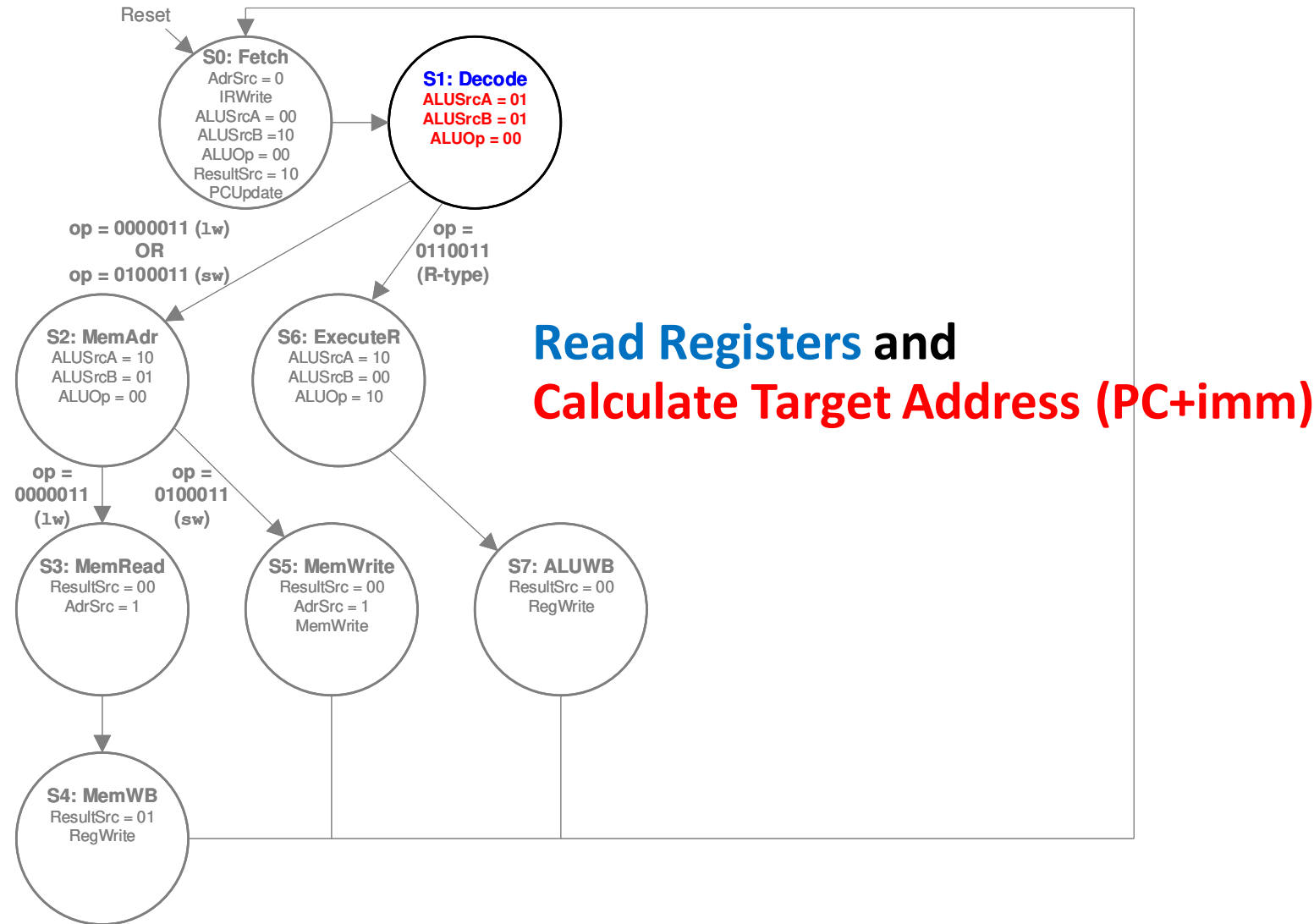


# Main FSM: Decode (Target Address)

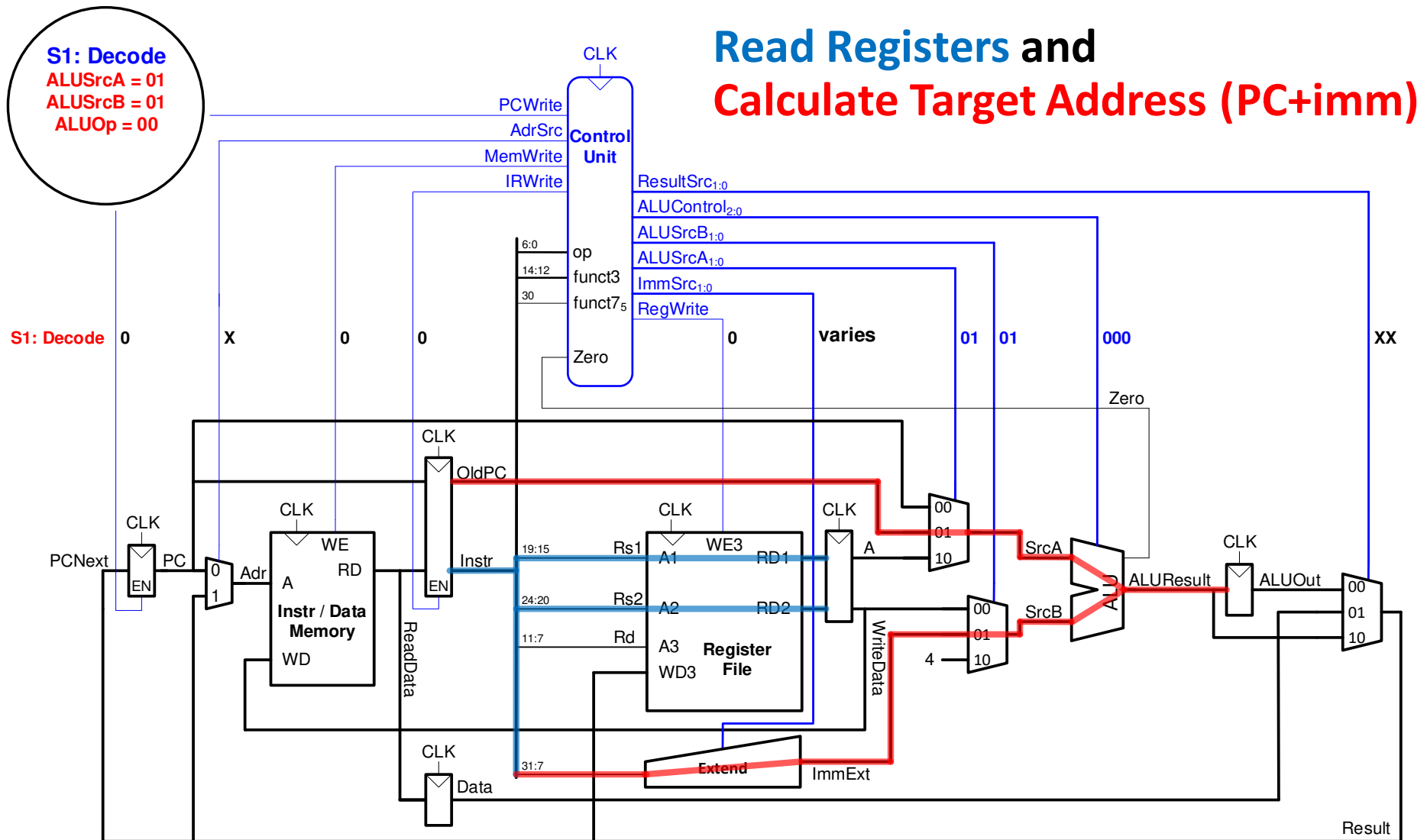

# Main FSM: beq

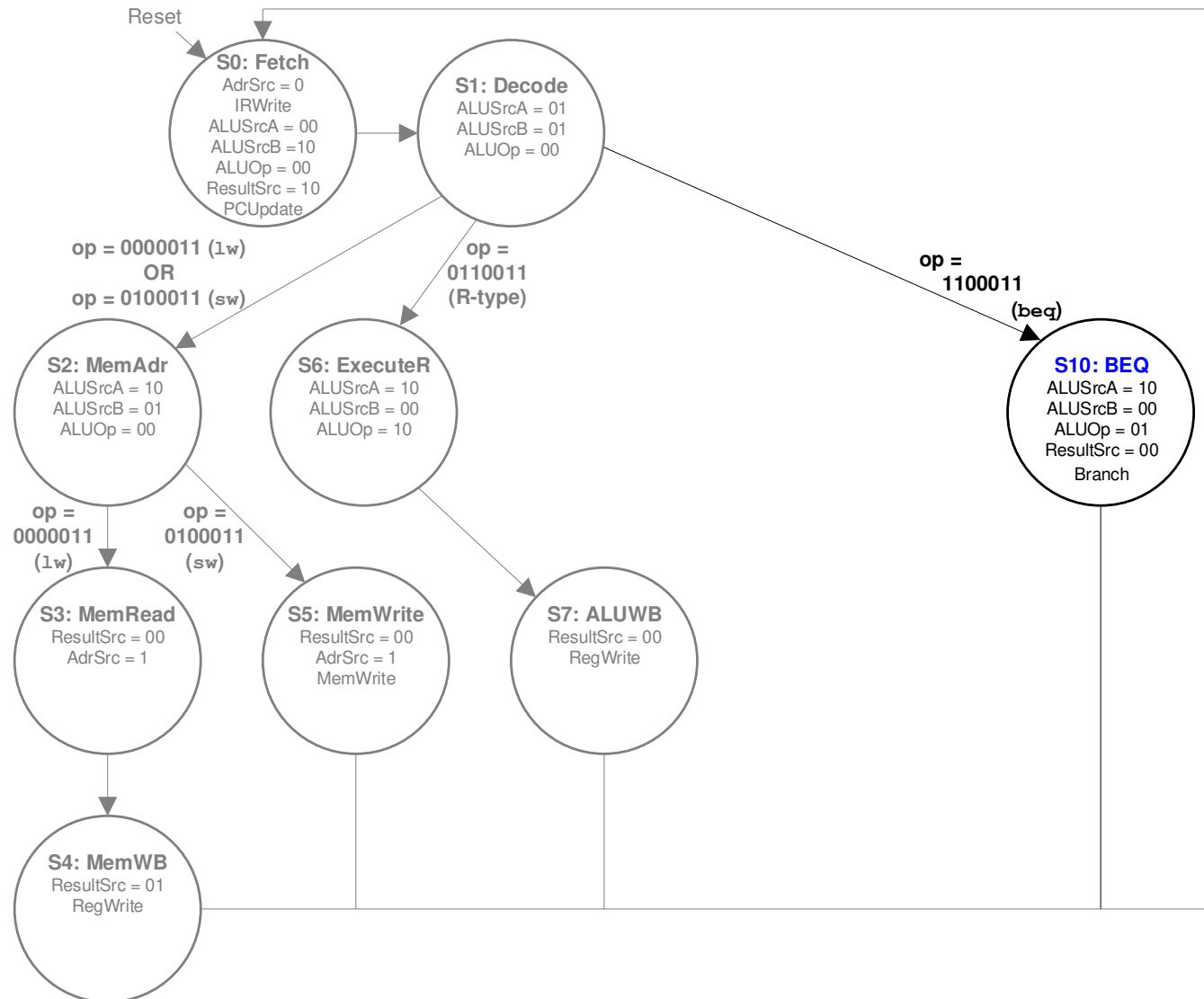

# Main FSM: beq Datapath

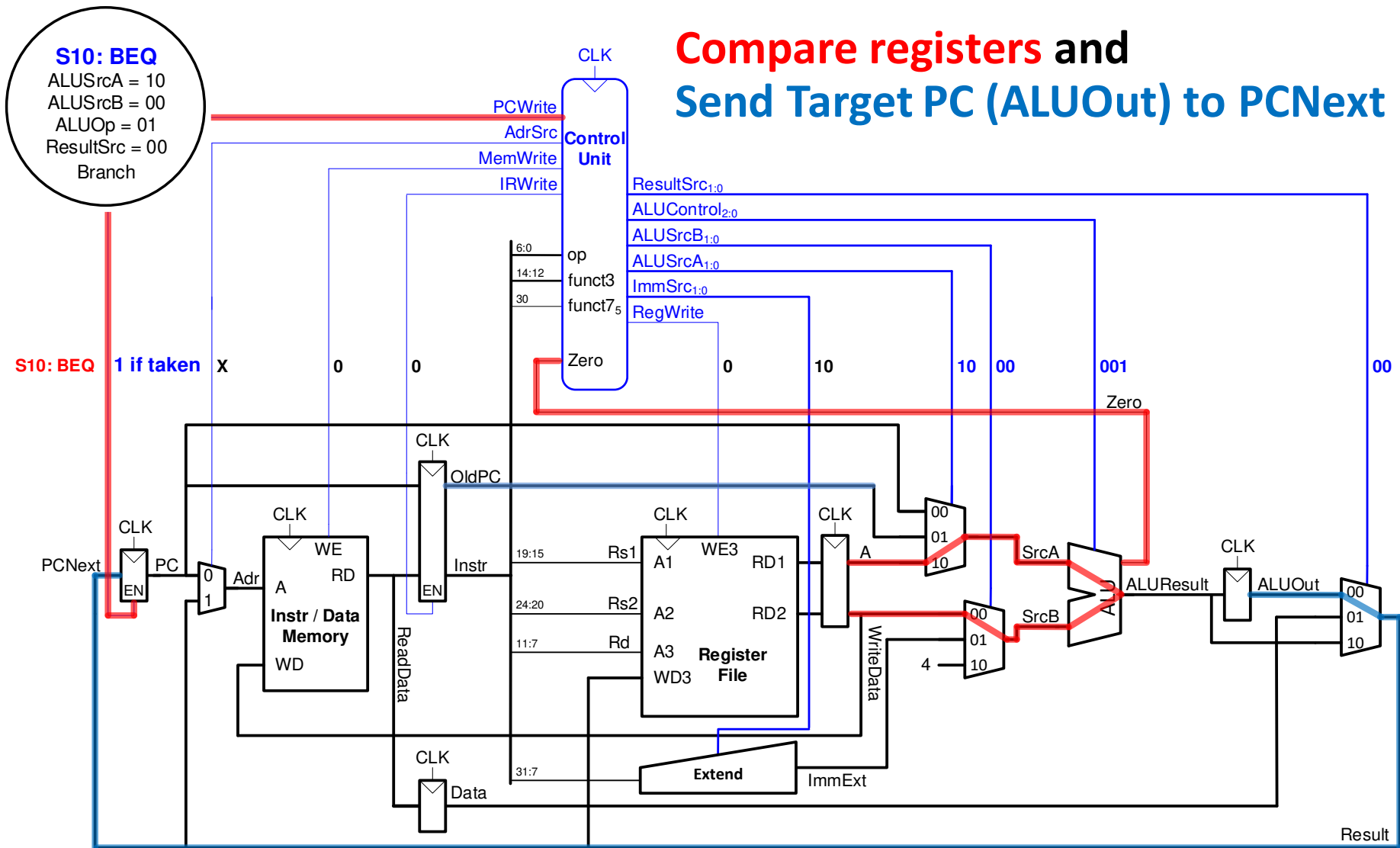


## Chapter 7: Microarchitecture


# **Extending the RISC-V Multicycle Processor**




# Main FSM: I-Type ALU Execute

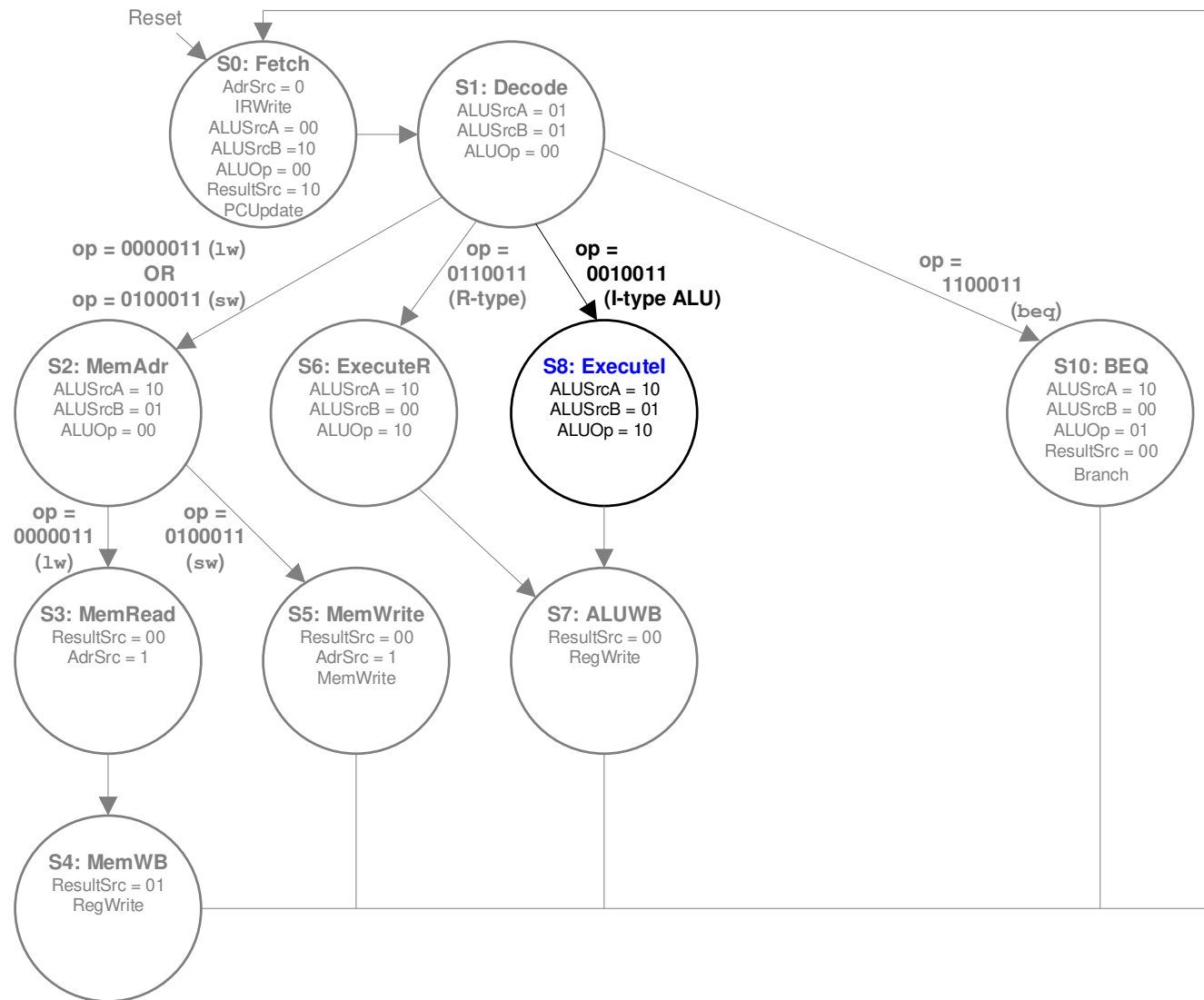

# Main FSM: I-Type ALU Exec. Datapath

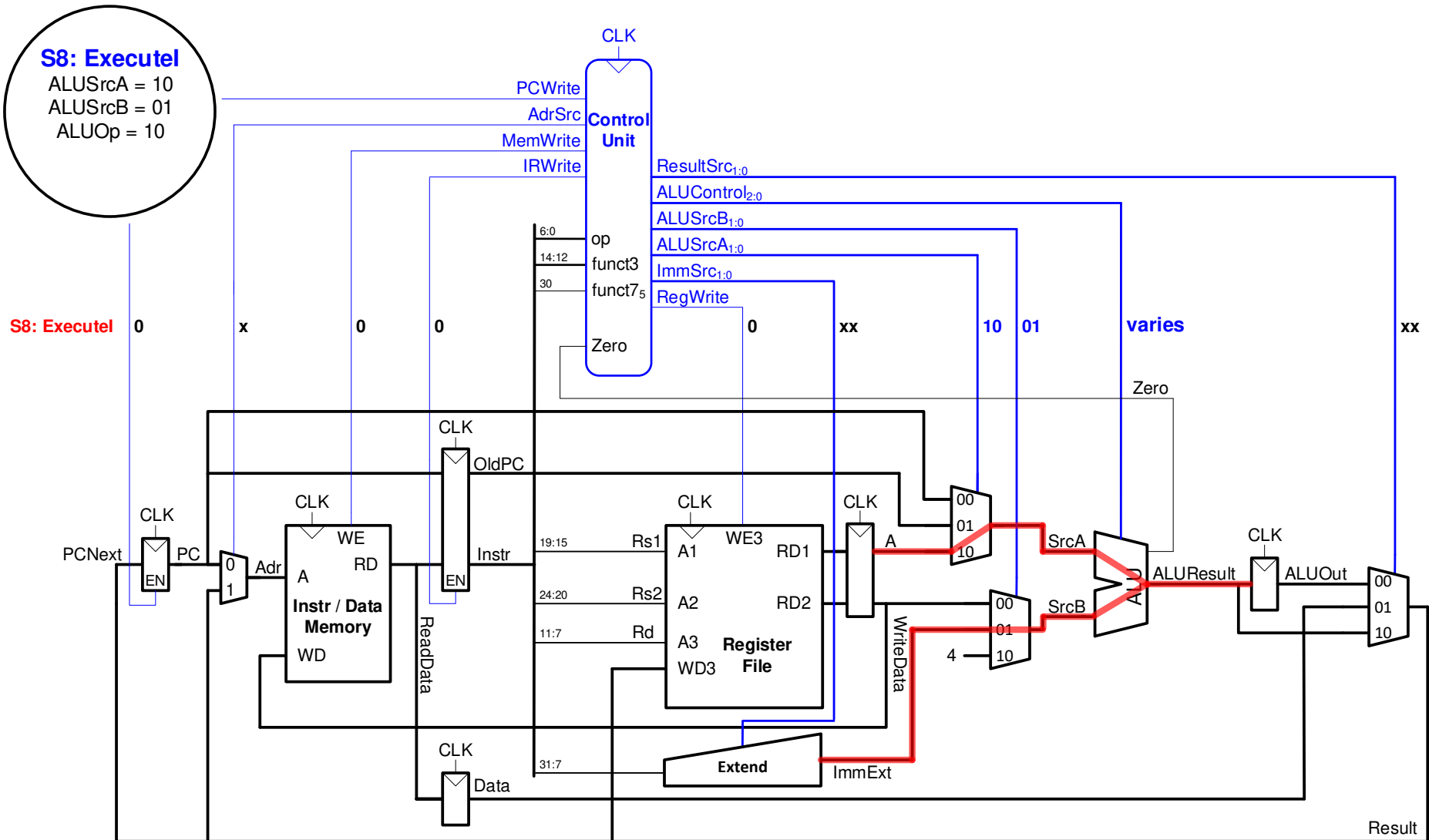

# Main FSM: jal

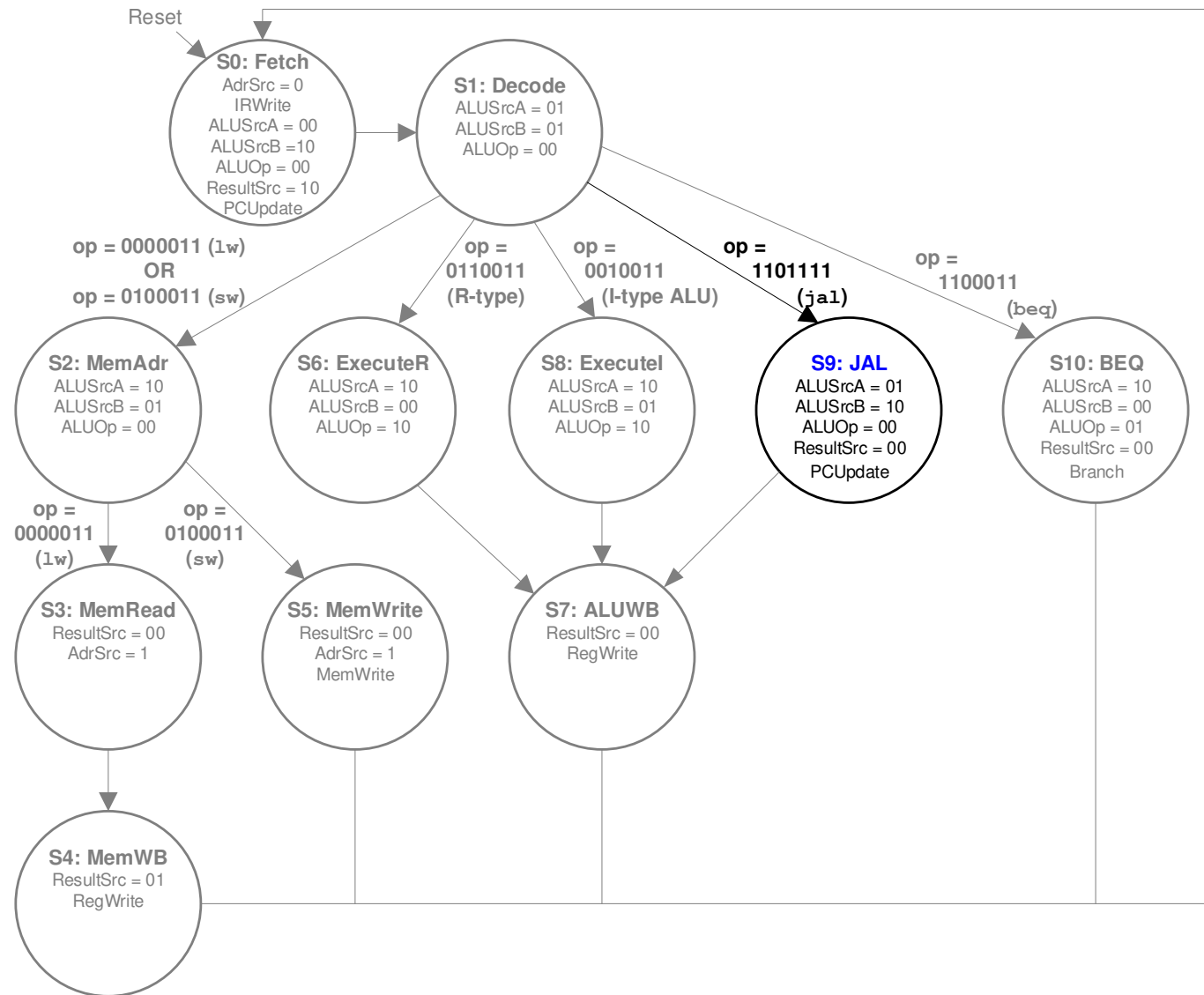


# Main FSM: jal Datapath

**Calculate PC + 4 and**  
**Send Target Address (ALUOut) to PCNext**

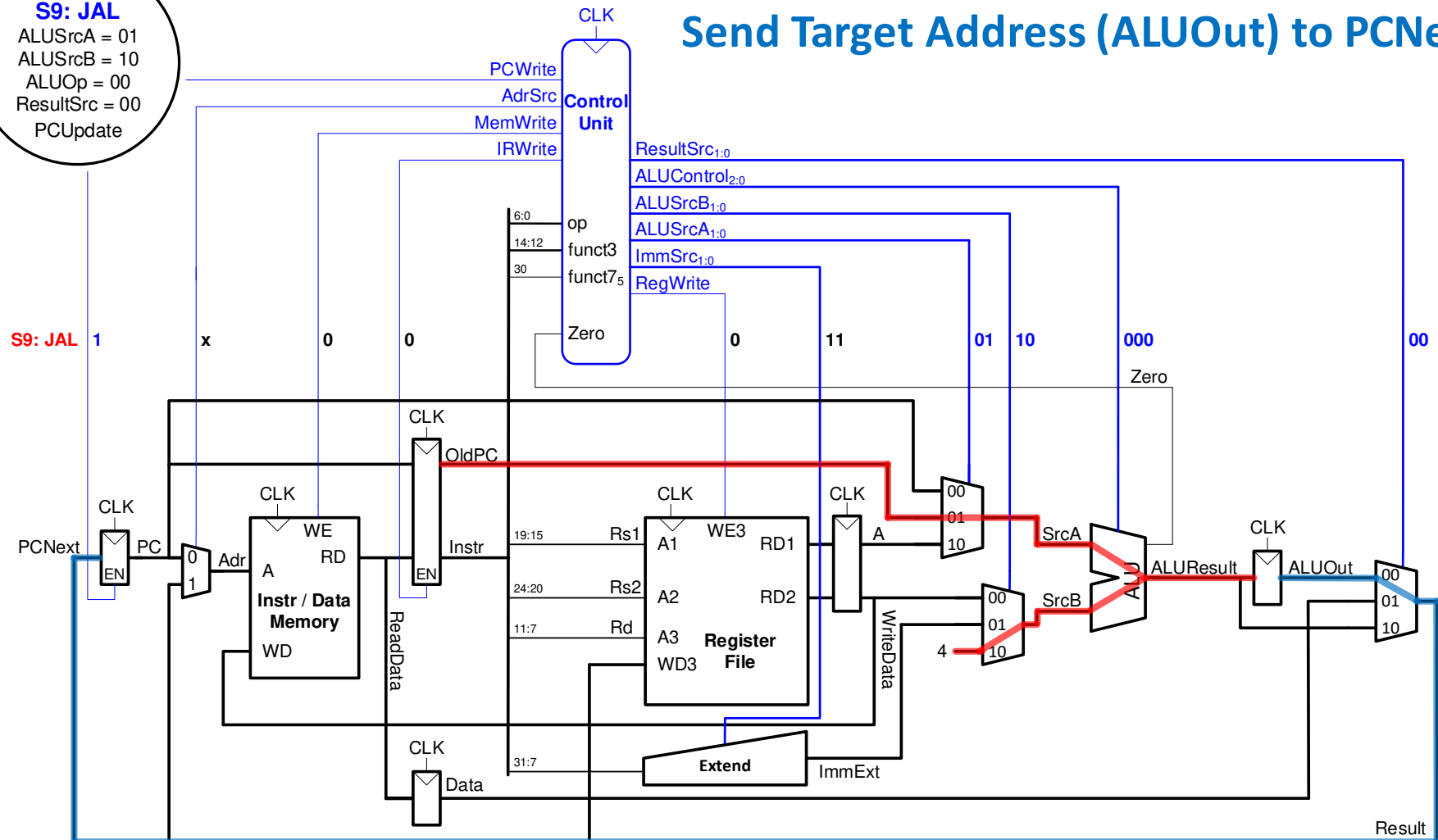
**S9: JAL**

ALUSrcA = 01  
ALUSrcB = 10  
ALUOp = 00  
ResultSrc = 00  
PCUpdate


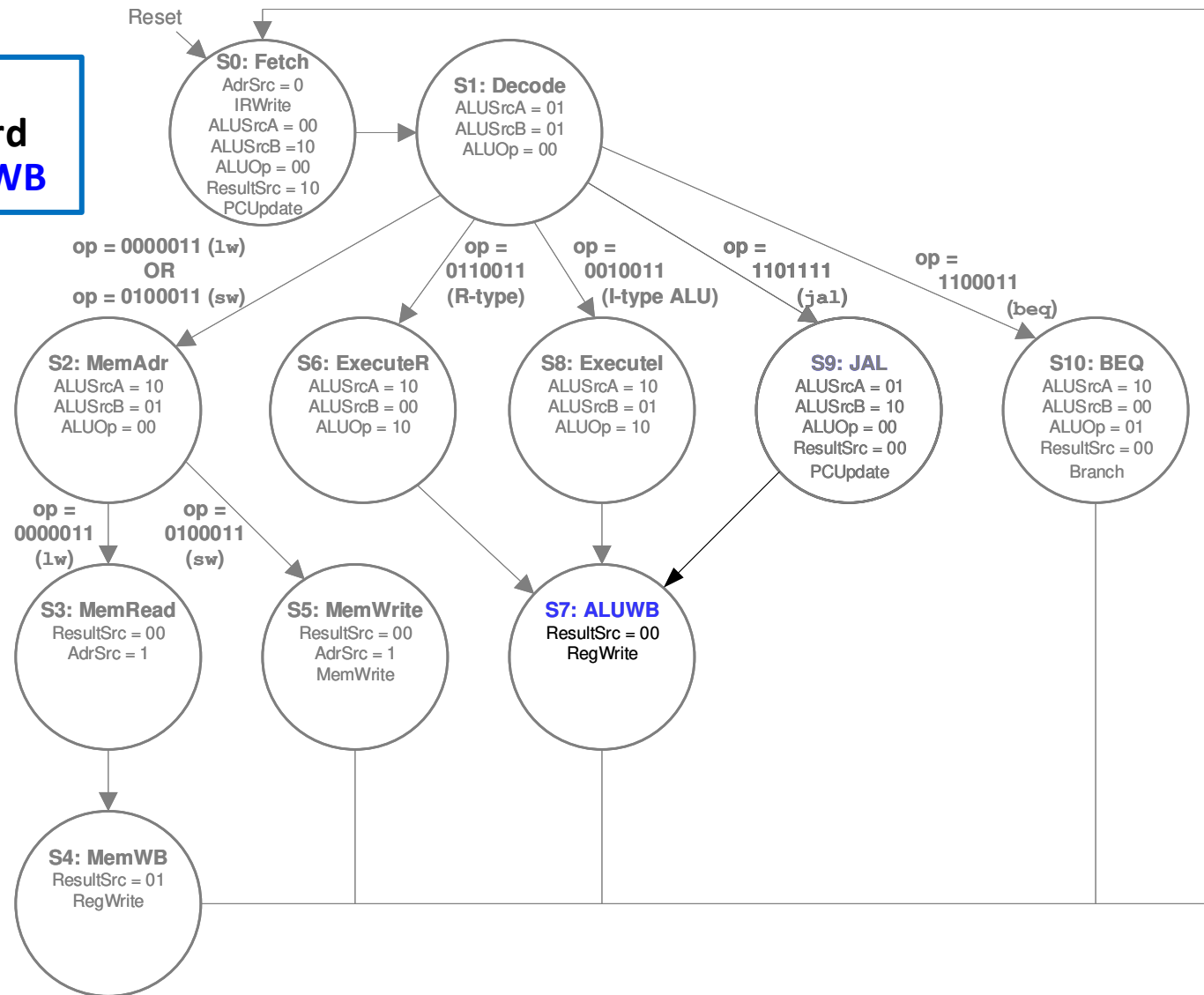
# Main FSM: jal

**PC + 4** is  
written to **rd**  
in **S7: ALUWB**



# Multicycle Processor Main FSM

## State

Fetch

Decode

MemAdr

MemRead

MemWB

MemWrite

ExecuteR

ExecuteI

ALUWB

BEQ

JAL

## Datapath $\mu$ Op

Instr  $\leftarrow$  Mem[PC]; PC  $\leftarrow$  PC+4

ALUOut  $\leftarrow$  PCTarget

ALUOut  $\leftarrow$  rs1 + imm

Data  $\leftarrow$  Mem[ALUOut]

rd  $\leftarrow$  Data

Mem[ALUOut]  $\leftarrow$  rd


ALUOut  $\leftarrow$  rs1 op rs2

ALUOut  $\leftarrow$  rs1 op imm

rd  $\leftarrow$  ALUOut

ALUResult = rs1-rs2; if Zero, PC = ALUOut

PC = ALUOut; ALUOut = PC+4

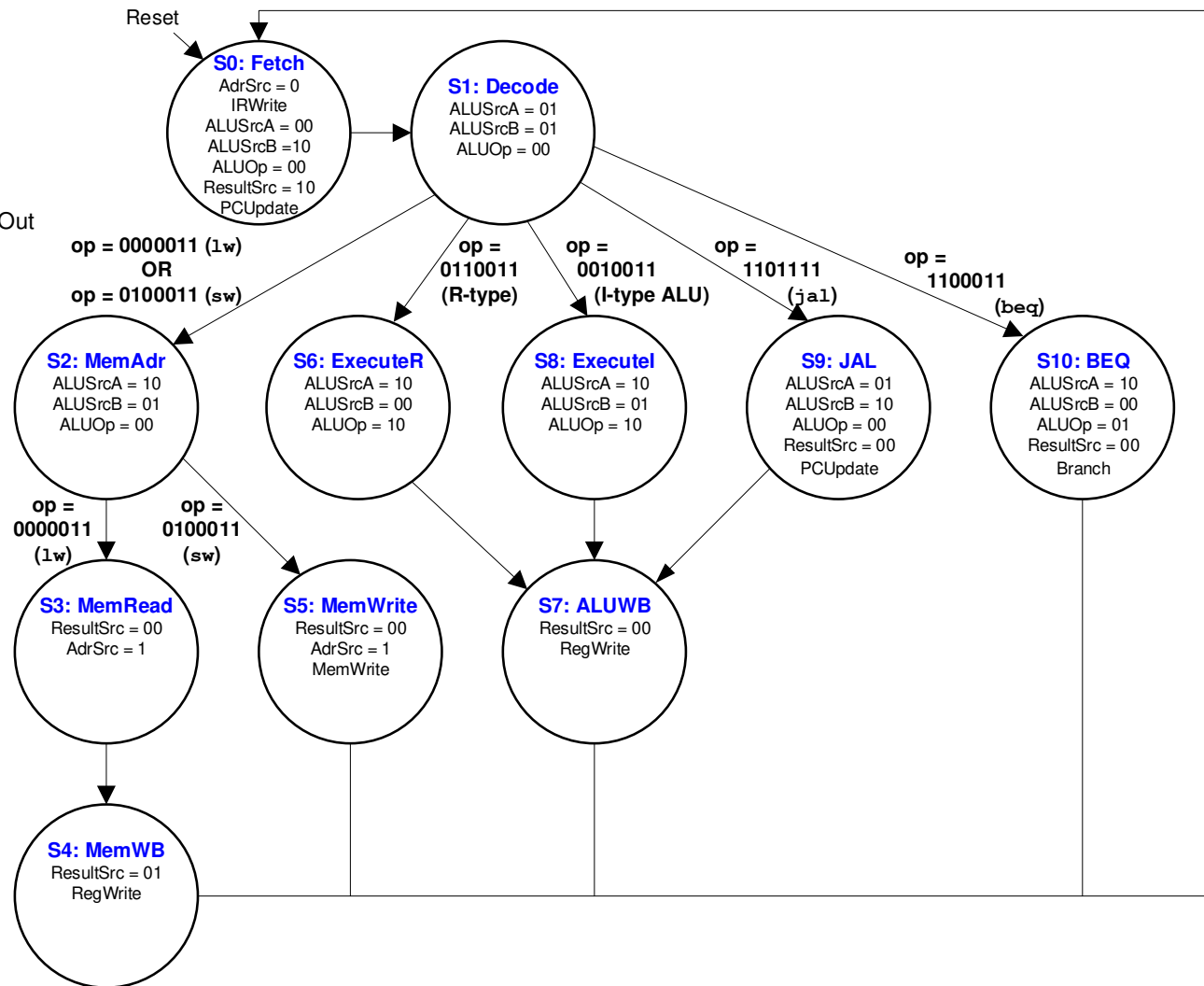

## Chapter 7: Microarchitecture

# **Multicycle Performance**

# Multicycle Processor Performance

- Instructions take different number of cycles:
  - 3 cycles: `beq`
  - 4 cycles: `R-type`, `addi`, `sw`, `jal`
  - 5 cycles: `lw`
- CPI is weighted average
- SPECINT2000 benchmark:
  - 25% loads
  - 10% stores
  - 13% branches
  - 52% R-type


$$\text{Average CPI} = (0.13)(3) + (0.52 + 0.10)(4) + (0.25)(5) = 4.12$$



# Multicycle Critical Path

## Potential Critical Paths:

- Calculate  $PC + 4$  or
- Read Memory

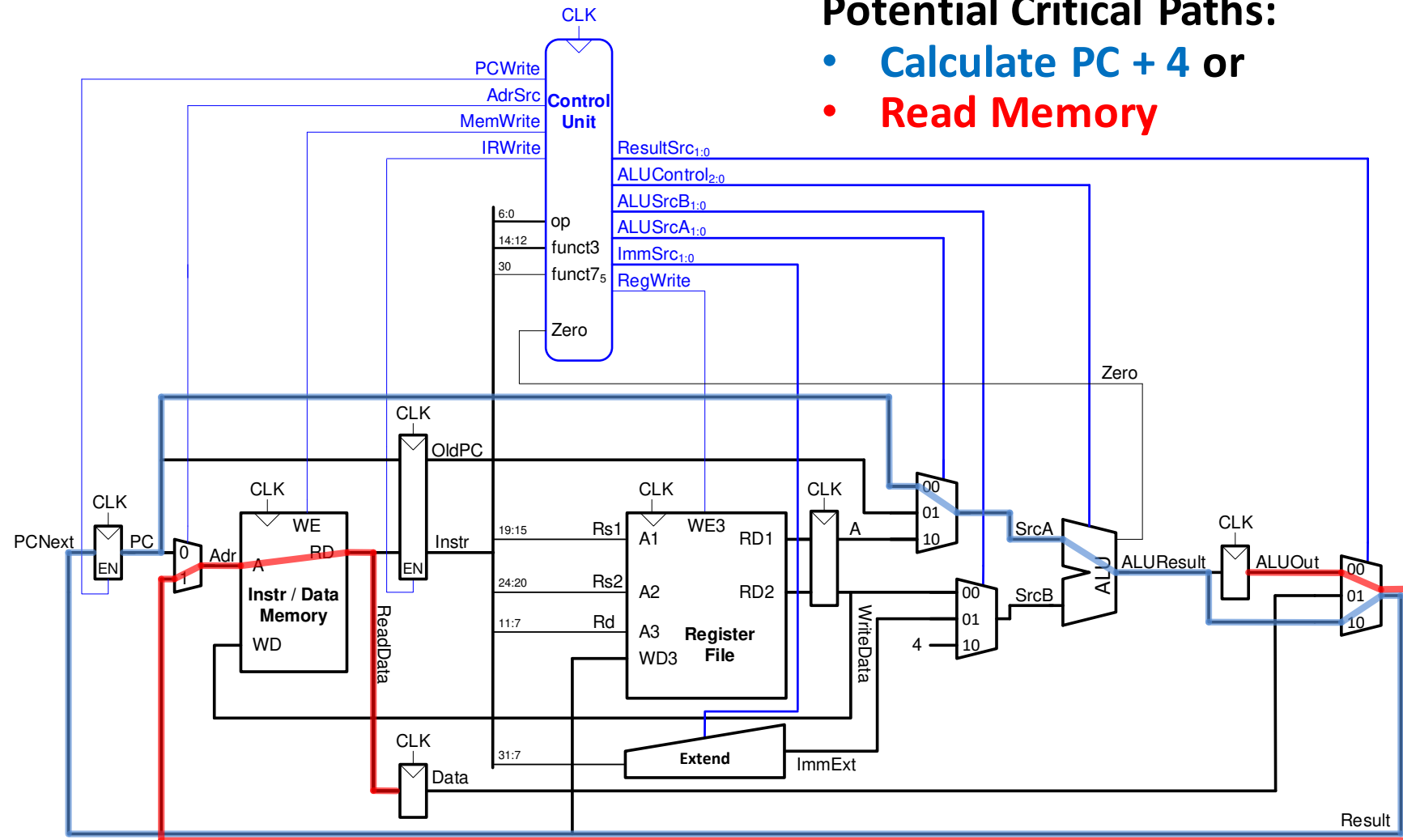

# Multicycle Processor Performance

Multicycle critical path:

- **Assumptions:**
  - RF is faster than memory
  - Writing memory is faster than reading memory

$$T_{c\_multi} = t_{pcq} + t_{dec} + 2t_{mux} + \max(t_{ALU}, t_{mem}) + t_{setup}$$

# Multicycle Performance Example

Element	Parameter	Delay (ps)
Register clock-to-Q	$t_{pcq\_PC}$	40
Register setup	$t_{setup}$	50
Multiplexer	$t_{mux}$	30
AND-OR gate	$t_{AND-OR}$	20
ALU	$t_{ALU}$	120
Decoder (Control Unit)	$t_{dec}$	25
Extend unit	$t_{dec}$	35
Memory read	$t_{mem}$	200
Register file read	$t_{RFread}$	100
Register file setup	$t_{RFsetup}$	60

$$T_{c\_multi} = t_{pcq} + t_{dec} + 2t_{mux} + \max(t_{ALU}, t_{mem}) + t_{setup}$$

$$=$$

# Multicycle Performance Example

For a program with **100 billion** instructions executing on a **multicycle** RISC-V processor

- **CPI** = 4.12 cycles/instruction
- **Clock cycle time:**  $T_{c\_multi} = 375 \text{ ps}$

**Execution Time** = (# instructions)  $\times$  CPI  $\times T_c$