










# **Digital Design & Computer Architecture**

**Sarah Harris & David Harris**

## **Chapter 5: Digital Building Blocks**
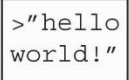
# Chapter 5 :: Topics

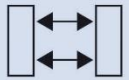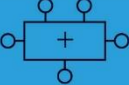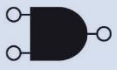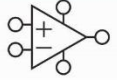- Introduction
- Arithmetic Circuits
- Number Systems
- Sequential Building Blocks
- Memory Arrays
- Logic Arrays

Application Software	
Operating Systems	
Architecture	
Micro-architecture	
Logic	
Digital Circuits	
Analog Circuits	
Devices	
Physics	

# Introduction


- **Digital building blocks:**
  - Gates, multiplexers, decoders, registers, arithmetic circuits, counters, memory arrays, logic arrays
- **Building blocks demonstrate hierarchy, modularity, and regularity:**
  - Hierarchy of simpler components
  - Well-defined interfaces and functions
  - Regular structure easily extends to different sizes
- **We'll use these building blocks in Chapter 7 to build a microprocessor**

## Chapter 5: Digital Building Blocks

# Adders

# 1-Bit Adders

**Half Adder**

 


A	B	C <sub>out</sub>	S
0	0		
0	1		
1	0		
1	1		

$$S =$$

$$C_{out} =$$

**Full Adder**

 

C <sub>in</sub>	A	B	C <sub>out</sub>	S
0	0	0		
0	0	1		
0	1	0		
0	1	1		
1	0	0		
1	0	1		
1	1	0		
1	1	1		


$$S =$$

$$C_{out} =$$

# Multibit Adders: CPAs

- Types of carry propagate adders (CPAs):
  - **Ripple-carry** (slow)
  - **Carry-lookahead** (fast)
  - **Prefix** (faster)
- Carry-lookahead and prefix adders faster for large adders but require more hardware

## Symbol

 


## Chapter 5: Digital Building Blocks

# **Ripple Carry Addition**
 
# Ripple-Carry Adder

- Chain 1-bit adders together
- Carry ripples through entire chain
- Disadvantage: **slow**





 
# Ripple-Carry Adder Delay

$$t_{\text{ripple}} =$$

where  $t_{FA}$  is the delay of a 1-bit full adder



## Chapter 5: Digital Building Blocks

# **Carry Lookahead Addition**

# Carry-Lookahead Adder

Compute  $C_{\text{out}}$  for  $k$ -bit blocks using *generate* and *propagate* signals

## Some definitions:

- Column  $i$  produces a carry out by either **generating** a carry out or **propagating** a carry in to the carry out
- Calculate generate ( $G_i$ ) and propagate ( $P_i$ ) signals for each column:
  - **Generate:** Column  $i$  will generate a carry out if  $A_i$  **and**  $B_i$  are both 1.

$$G_i = A_i B_i$$

- **Propagate:** Column  $i$  will propagate a carry in to the carry out if  $A_i$  **or**  $B_i$  is 1.

$$P_i = A_i + B_i$$

- **Carry out:** The carry out of column  $i$  ( $C_i$ ) is:

$$C_i = A_i B_i + (A_i + B_i) C_{i-1} = G_i + P_i C_{i-1}$$

# Propagate and Generate Signals

**Examples:** Column propagate and generate signals:

Column propagate:  $P_i = A_i + B_i$

Column generate:  $G_i = A_i B_i$

$$\begin{array}{r} 1011 \\ + 0110 \\ \hline \end{array} \quad \begin{array}{l} A_{3:0} \\ B_{3:0} \end{array}$$

$$\begin{array}{r} 1011 \\ + 1001 \\ \hline \end{array} \quad \begin{array}{l} A_{3:0} \\ B_{3:0} \end{array}$$

# Block Propagate and Generate

Now use column Propagate and Generate signals to compute **Block Propagate** and **Block Generate** signals for k-bit blocks, i.e.:

- Compute if a **k-bit group** will **propagate** a carry in (of the block) to the carry out (of the block)
- Compute if a **k-bit group** will **generate** a carry out (of the block)

# Block Propagate and Generate

- **Example: 4-bit blocks**
  - **Block propagate signal:  $P_{3:0}$**  (single-bit signal)
    - A carry-in would propagate through all 4 bits of the block:

$$P_{3:0} = P_3 P_2 P_1 P_0$$

- **Examples:**

$$\begin{array}{r} 1011 \\ + 0100 \\ \hline \end{array}$$

$$\begin{array}{r} 1011 \\ + 0001 \\ \hline \end{array}$$

# Block Propagate and Generate

- **Example: 4-bit blocks**

- **Block propagate signal:  $P_{3:0}$**  (single-bit signal)

- A carry-in would propagate through all 4 bits of the block:

$$P_{3:0} = P_3 P_2 P_1 P_0$$

- **Block generate signal:  $G_{3:0}$**  (single-bit signal)

- A carry is generated:
      - in column 3, **or**
      - in column 2 and propagated through column 3, **or**
      - in column 1 and propagated through columns 2 and 3, **or**
      - in column 0 and propagated through columns 1-3

$$G_{3:0} = G_3 + G_2 P_3 + G_1 P_2 P_3 + G_0 P_1 P_2 P_3$$

$$G_{3:0} = G_3 + P_3 [G_2 + P_2 (G_1 + P_1 G_0)]$$

# Block Propagate and Generate

- **Example: 4-bit blocks**

- **Block generate signal:  $G_{3:0}$**  (single-bit signal)

- A carry is: generated in column 3, **or** generated in column 2 and propagated through column 3, **or** ...

$$G_{3:0} = G_3 + G_2P_3 + G_1P_2P_3 + G_0P_1P_2P_3$$

$$\begin{array}{r} 1001 \\ + 1100 \\ \hline \end{array}$$

$$\begin{array}{r} 1110 \\ + 0100 \\ \hline \end{array}$$

$$\begin{array}{r} 0110 \\ + 0010 \\ \hline \end{array}$$



# Block Propagate and Generate

- **Example: 4-bit blocks**

- **Block propagate signal:**  $P_{3:0}$  (single-bit signal)
  - A carry-in would propagate through all 4 bits of the block:

$$P_{3:0} = P_3 P_2 P_1 P_0$$

- **Block generate signal:**  $G_{3:0}$  (single-bit signal)
  - A carry is generated:
    - in column 3, **or**
    - in column 2 and propagated through column 3, **or**
    - in column 1 and propagated through columns 2 and 3, **or**
    - in column 0 and propagated through columns 1-3

$$G_{3:0} = G_3 + G_2 P_3 + G_1 P_2 P_3 + G_0 P_1 P_2 P_3$$

$$G_{3:0} = G_3 + P_3 [G_2 + P_2 (G_1 + P_1 G_0)]$$

$$C_3 = G_{3:0} + P_{3:0} C_{-1}$$

# Block Propagate and Generate


- **Example:** Block propagate and generate signals for 4-bit blocks ( $P_{3:0}$  and  $G_{3:0}$ ):

$$P_{3:0} = P_3 P_2 P_1 P_0$$

$$G_{3:0} = G_3 + P_3 (G_2 + P_2 (G_1 + P_1 G_0))$$

$$C_3 = G_{3:0} + P_{3:0} C_{-1}$$

# 32-bit CLA with 4-bit Blocks

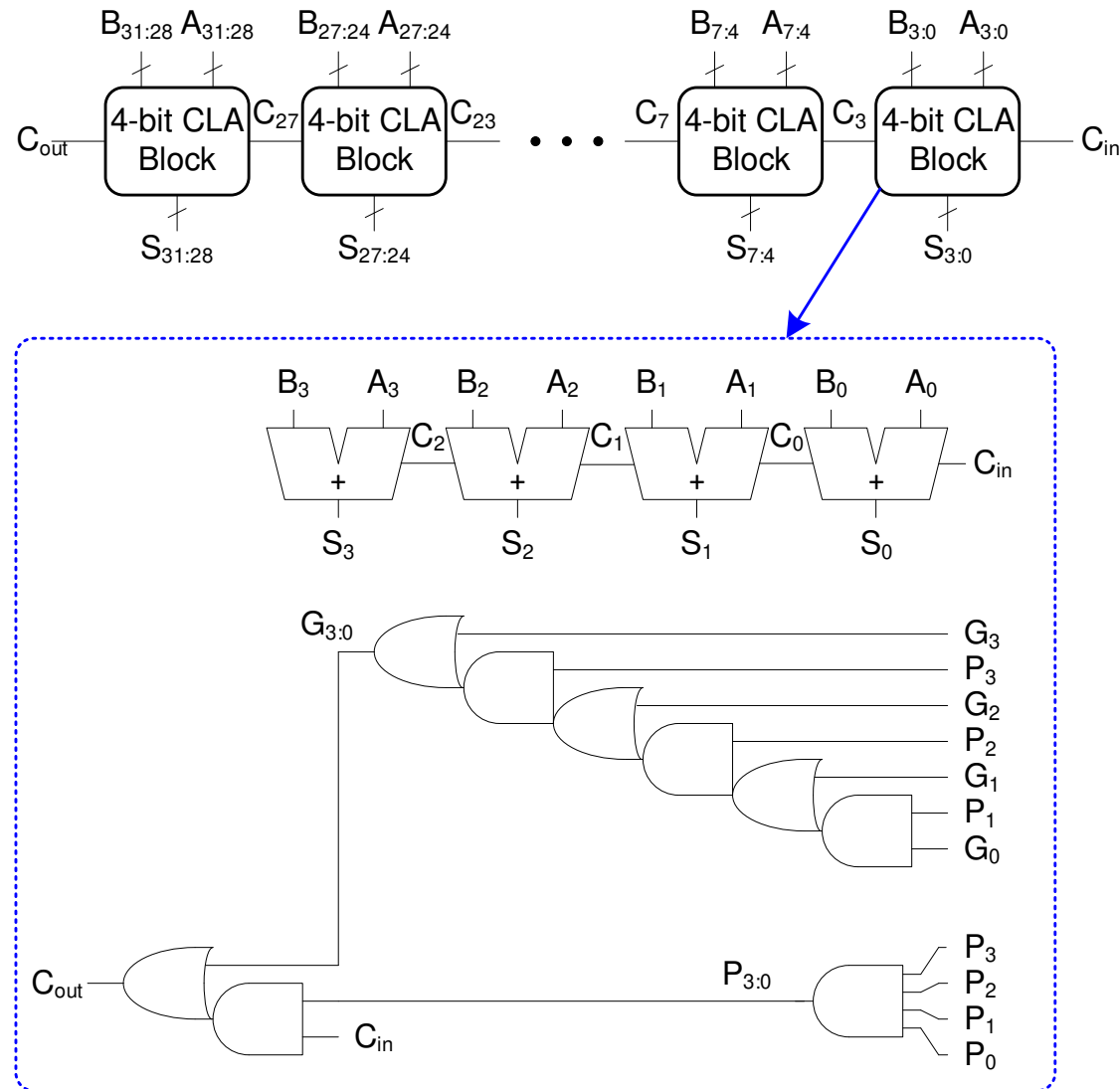

# Carry-Lookahead Addition

- **Step 1:** Compute  $G_i$  and  $P_i$  for all columns
- **Step 2:** Compute  $G$  and  $P$  for  $k$ -bit blocks
- **Step 3:**  $C_{in}$  propagates through each  $k$ -bit propagate/generate logic (meanwhile computing sums)
- **Step 4:** Compute sum for most significant  $k$ -bit block

# Carry-Lookahead Addition

- **Step 1:** Compute  $G_i$  and  $P_i$  for all columns

$$G_i = A_i B_i$$

$$P_i = A_i + B_i$$

# Carry-Lookahead Addition


- **Step 1:** Compute  $G_i$  and  $P_i$  for all columns
- **Step 2:** Compute  $G$  and  $P$  for  $k$ -bit blocks

$$P_{3:0} = P_3 P_2 P_1 P_0$$

$$G_{3:0} = G_3 + P_3 (G_2 + P_2 (G_1 + P_1 G_0))$$

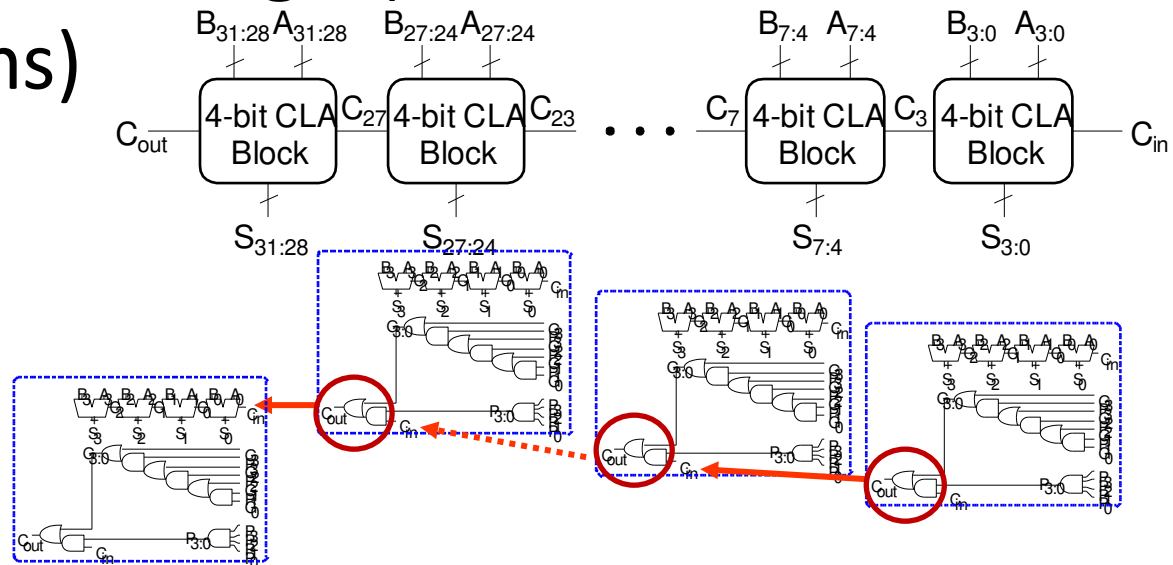
# Carry-Lookahead Addition

- **Step 1:** Compute  $G_i$  and  $P_i$  for all columns
- **Step 2:** Compute  $G$  and  $P$  for  $k$ -bit blocks
- **Step 3:**  $C_{in}$  propagates through each  $k$ -bit propagate/generate logic (meanwhile computing sums)



 
# Carry-Lookahead Addition

- **Step 1:** Compute  $G_i$  and  $P_i$  for all columns
- **Step 2:** Compute  $G$  and  $P$  for  $k$ -bit blocks
- **Step 3:**  $C_{in}$  propagates through each  $k$ -bit propagate/generate logic (meanwhile computing sums)
- **Step 4:** Compute sum for most significant  $k$ -bit block





# 32-bit CLA with 4-bit Blocks

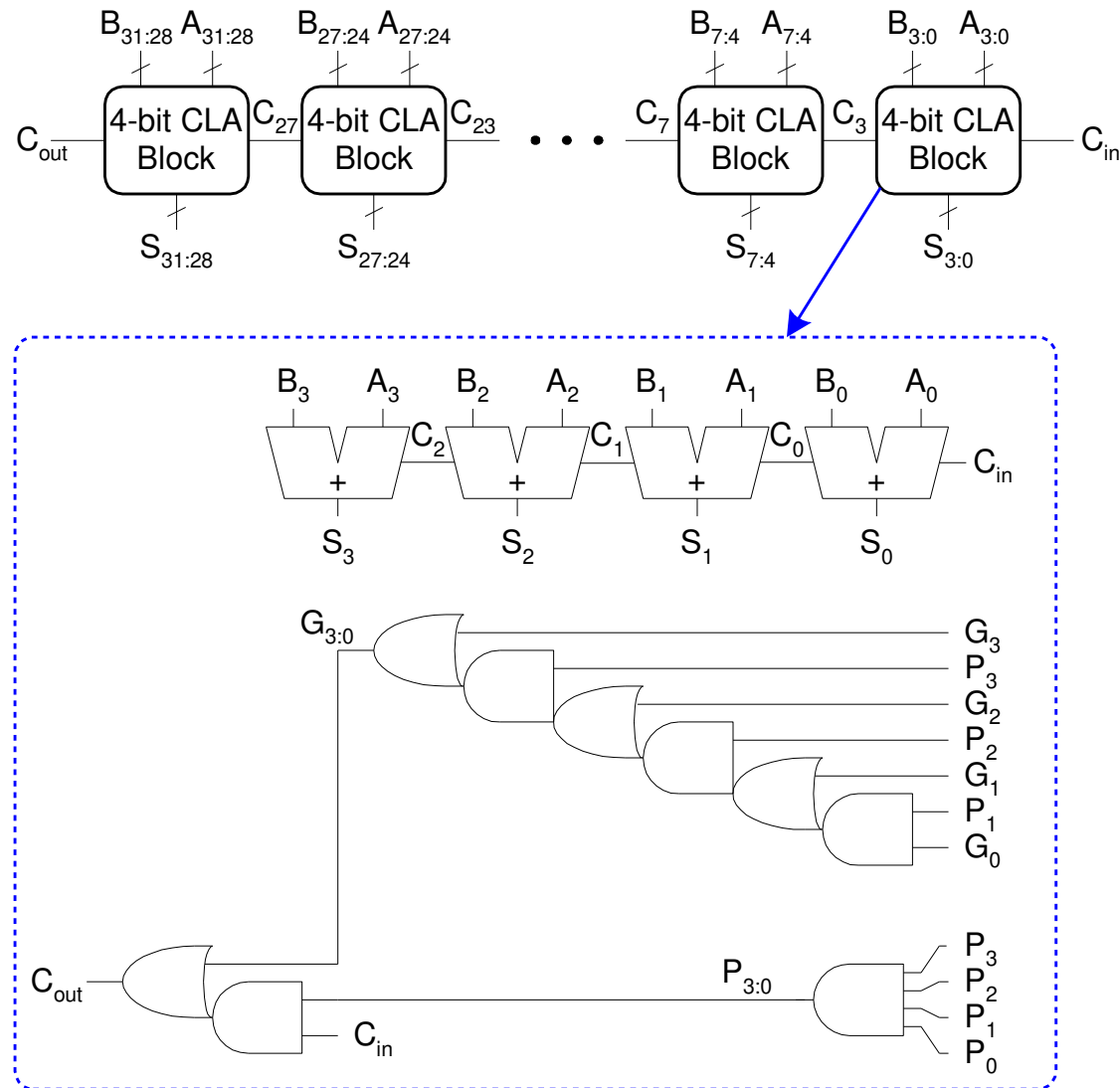

# Carry-Lookahead Adder Delay

For  $N$ -bit CLA with  $k$ -bit blocks:

$$t_{CLA} = t_{pg} + t_{pg\_block} + (N/k - 1)t_{AND\_OR} + kt_{FA}$$

- $t_{pg}$ : delay to generate all  $P_i, G_i$
- $t_{pg\_block}$ : delay to generate all  $P_{i:j}, G_{i:j}$
- $t_{AND\_OR}$ : delay from  $C_{in}$  to  $C_{out}$  of final AND/OR gate in  $k$ -bit CLA block

An  $N$ -bit carry-lookahead adder is generally much faster than a ripple-carry adder for  $N > 16$

# Chapter 5: Digital Building Blocks

## **Prefix Addition**

# Prefix Adder

- Computes carry in ( $C_{i-1}$ ) for each column, then computes sum:

$$S_i = (A_i \oplus B_i) \oplus C_{i-1}$$

- It computes  $C_{i-1}$  by:
  - Computing  $G$  and  $P$  for 1-, 2-, 4-, 8-bit blocks, etc. until all  $G_i$  (carry in) known
  - $G_i = C_i$
- $\log_2 N$  stages

# Prefix Adder

- Carry out either *generated* in a column or *propagated* from a previous column.

- Column -1 holds  $C_{in}$ , so

$$G_{-1} = C_{in}, P_{-1} = X \text{ (not used)}$$

- Carry in to column  $i$  = carry out of column  $i-1$ :

$$C_{i-1} = G_{i-1:-1}$$

$G_{i-1:-1}$ : generate signal spanning columns  $i-1$  to -1

- Sum equation:

$$S_i = (A_i \oplus B_i) \oplus G_{i-1:-1}$$

- **Goal:** Quickly compute  $G_{0:-1}, G_{1:-1}, G_{2:-1}, G_{3:-1}, G_{4:-1}, G_{5:-1}, \dots$   
(called *prefixes*)  $(= C_0, C_1, C_2, C_3, C_4, C_5, \dots)$

# Prefix Adder

- Generate and propagate signals for a block spanning bits  $i:j$

$$G_{i:j} = G_{i:k} + P_{i:k} G_{k-1:j}$$

$$P_{i:j} = P_{i:k} P_{k-1:j}$$

- In words:
  - **Generate:** block  $i:j$  will generate a carry if:
    - **upper part** ( $i:k$ ) generates a carry ( $G_{i:k}$ ) **or**
    - upper part ( $i:k$ ) propagates a carry ( $P_{i:k}$ ) generated in lower part ( $k-1:j$ ) ( $G_{k-1:j}$ )
  - **Propagate:** block  $i:j$  will propagate a carry if *both* the upper and lower parts propagate the carry ( $P_{i:k}$  **AND**  $P_{k-1:j}$ )

# Prefix Adder Example

**Step 1.** Calculate P's and G's  
for **1-bit block**



**Step 2.** Calculate P's and G's  
for **2-bit blocks**

**Step 3.** Calculate P's and G's  
for **4-bit blocks**

**Step 4.** Continue to calculate P's and  
G's for larger blocks (8-bit, 16-bit, etc.)

**Step 5.** Use prefixes to calculate  
sums

# Prefix Adder Schematic

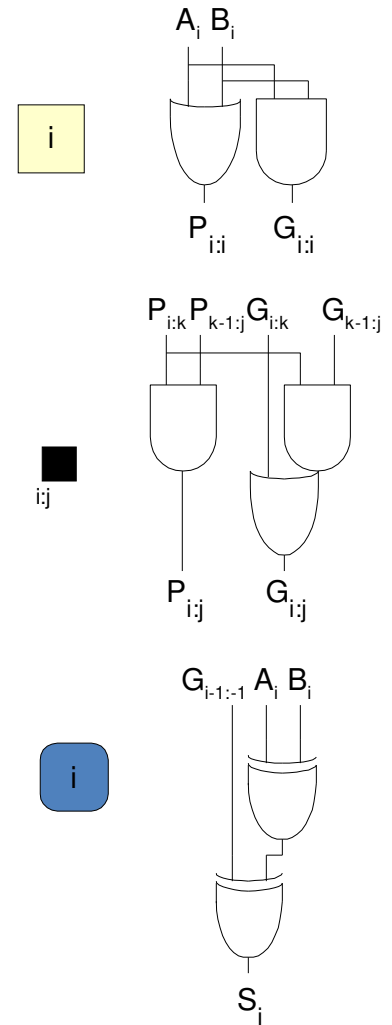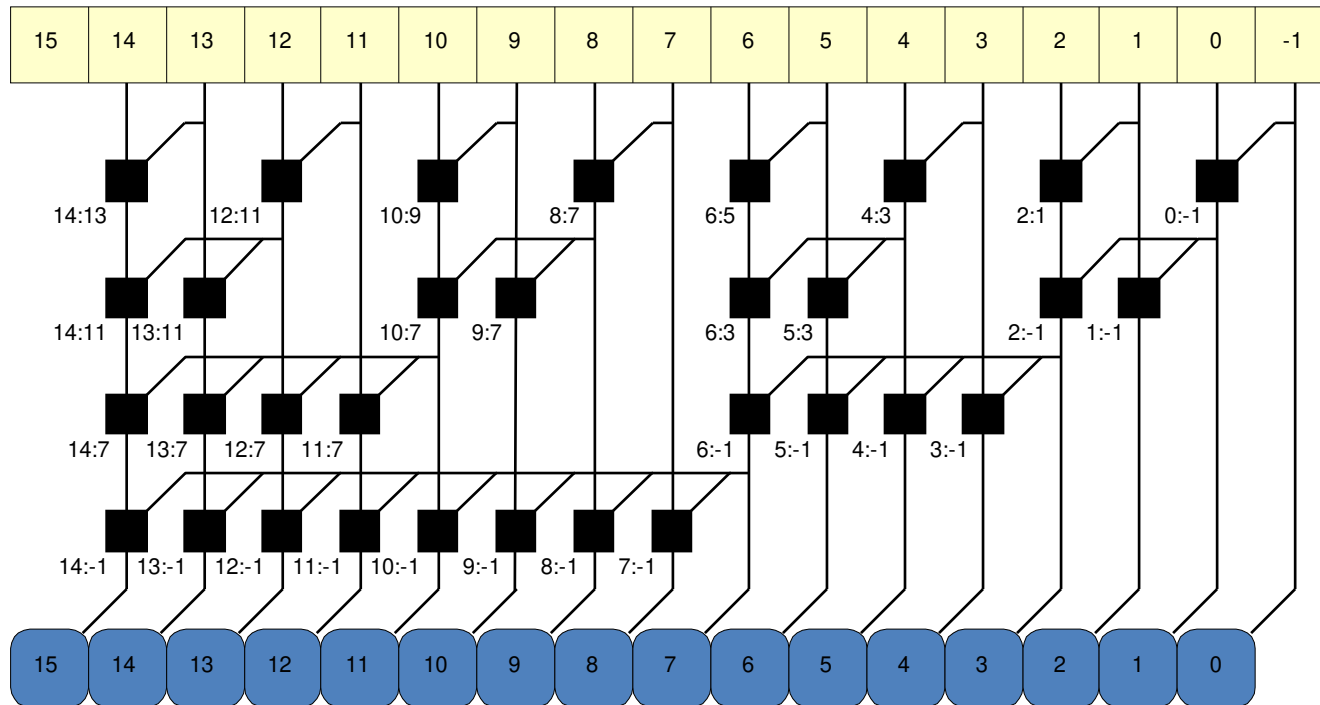



# Prefix Adder Delay

$$t_{PA} = t_{pg} + \log_2 N (t_{pg\_prefix}) + t_{XOR}$$

$t_{pg}$ : delay to produce  $P_i, G_i$  (AND or OR gate)

$t_{pg\_prefix}$ : delay of black prefix cell (AND-OR gate)

# Adder Delay Comparisons

**Compare the delay of: 32-bit ripple-carry, CLA, and prefix adders**

- CLA has 4-bit blocks
- 2-input gate delay = 100 ps; full adder delay = 300 ps

$t_{\text{ripple}}$

$t_{CLA}$

$t_{PA}$

## Chapter 5: Digital Building Blocks


# **Subtractors & Comparators**

# Subtractor

$$A - B = A + \bar{B} + 1$$


Symbol

Implementation

 

# Comparator: Equality

Symbol

 


Implementation

# Comparator: Signed Less Than

**$A < B$  if  $A - B$  is negative**

**Beware of overflow**

 

## Chapter 5: Digital Building Blocks

**ALU:**

**Arithmetic Logic Unit**

# ALU: Arithmetic Logic Unit


## **ALU should perform:**

- Addition
- Subtraction
- AND
- OR



# ALU: Arithmetic Logic Unit

ALUControl <sub>1:0</sub>	Function
00	Add
01	Subtract
10	AND
11	OR

 

**Example:** Perform  $A \text{ OR } B$

$ALUControl_{1:0} = 11$

$Result = A \text{ OR } B$

# ALU: Arithmetic Logic Unit


ALUControl <sub>1:0</sub>	Function
00	Add
01	Subtract
10	AND
11	OR

## Example: Perform $A \text{ OR } B$

$ALUControl_{1:0} = 11$

Mux selects output of OR gate as *Result*,  
so:

**$Result = A \text{ OR } B$**

 

# ALU: Arithmetic Logic Unit

ALUControl <sub>1:0</sub>	Function
00	Add
01	Subtract
10	AND
11	OR

**Example: Perform  $A + B$**

$ALUControl_{1:0} = 00$


$ALUControl_0 = 0$ , so:

$C_{in}$  to adder = 0

2<sup>nd</sup> input to adder is  $B$


Mux selects *Sum* as *Result*, so

**$Result = A + B$**

 


# ALU with Status Flags


Flag	Description
<i>N</i>	Result is <b>N</b> egative
<i>Z</i>	Result is <b>Z</b> ero
<i>C</i>	Adder produces <b>C</b> arry out
<i>V</i>	Adder o <b>V</b> erflowed

 

# ALU with Status Flags

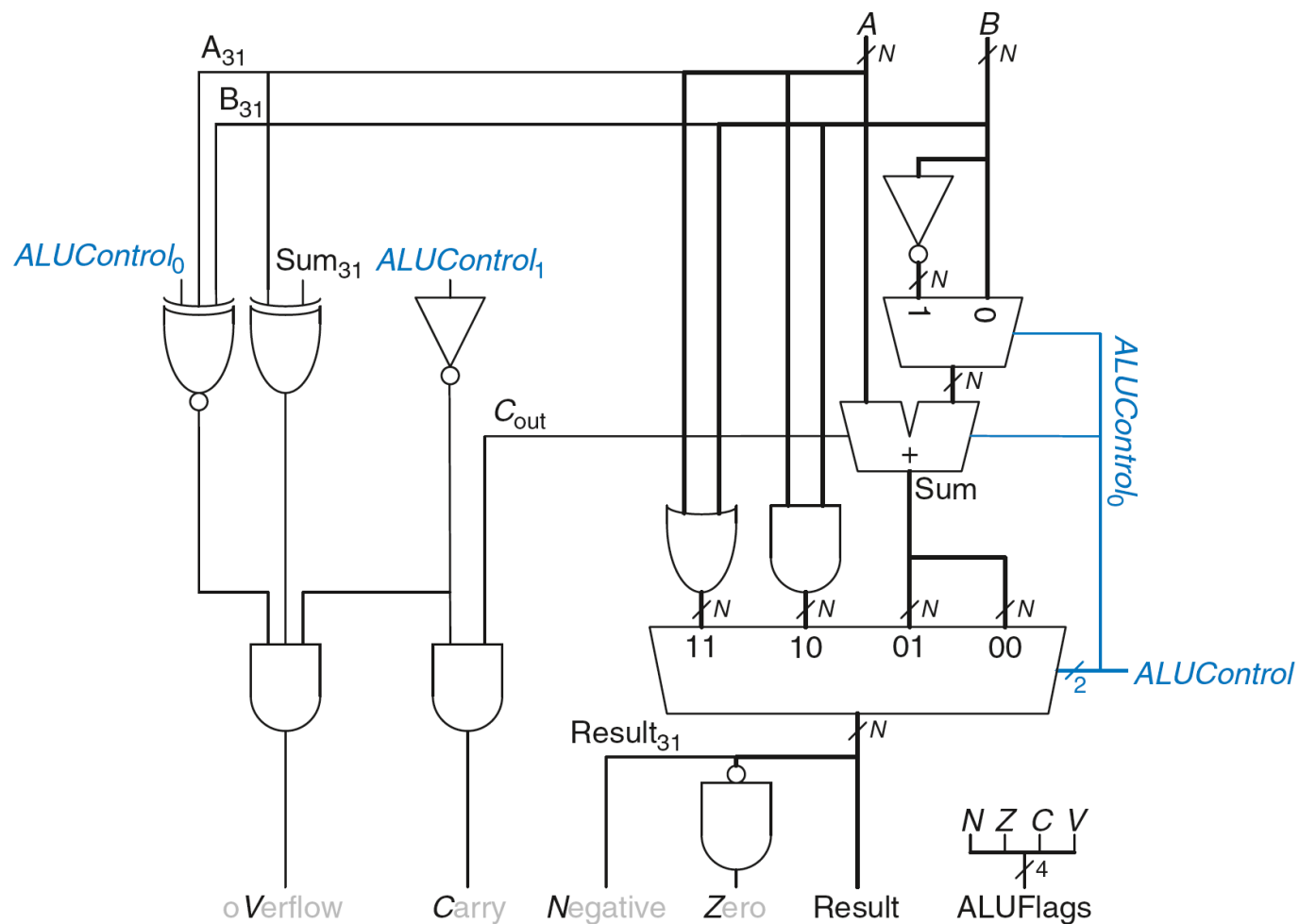

## ALU with Status Flags: Negative

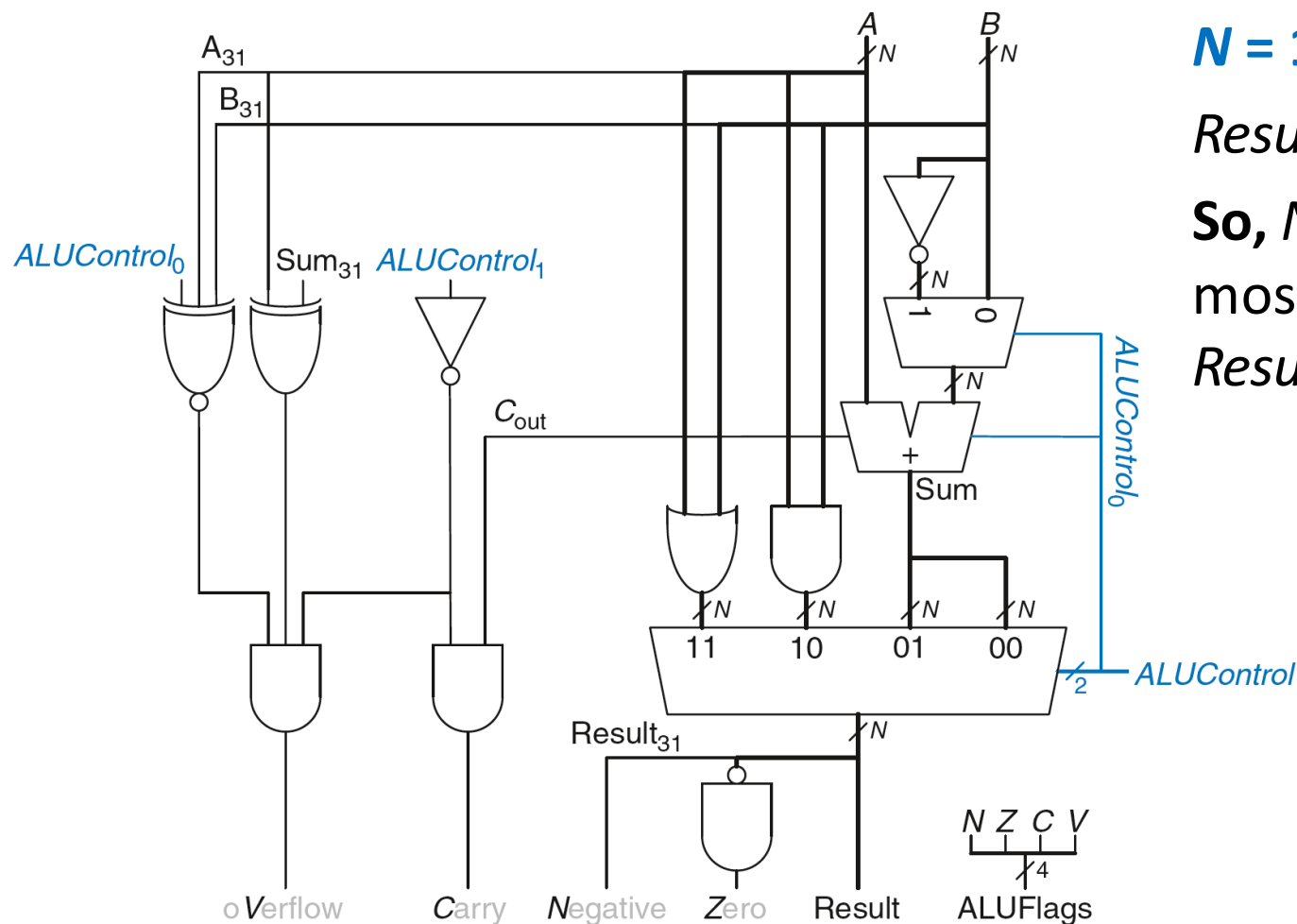


**$N = 1$  if:**

*Result* is **negative**

**So,  $N$  is connected to most significant bit of *Result*.**


# ALU with Status Flags: Zero

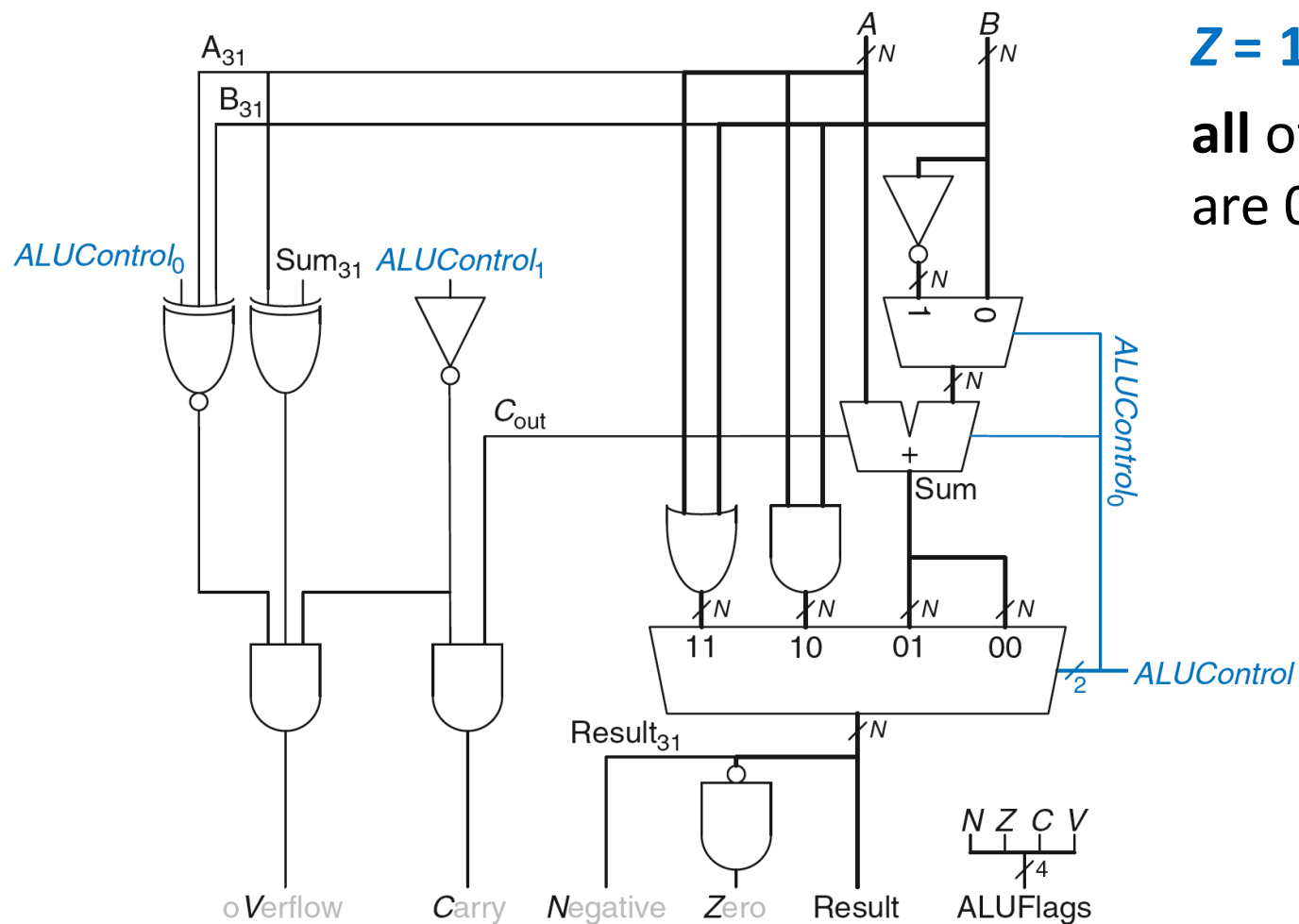

**Z = 1** if:

**all** of the bits of *Result*  
are 0

# ALU with Status Flags: Carry

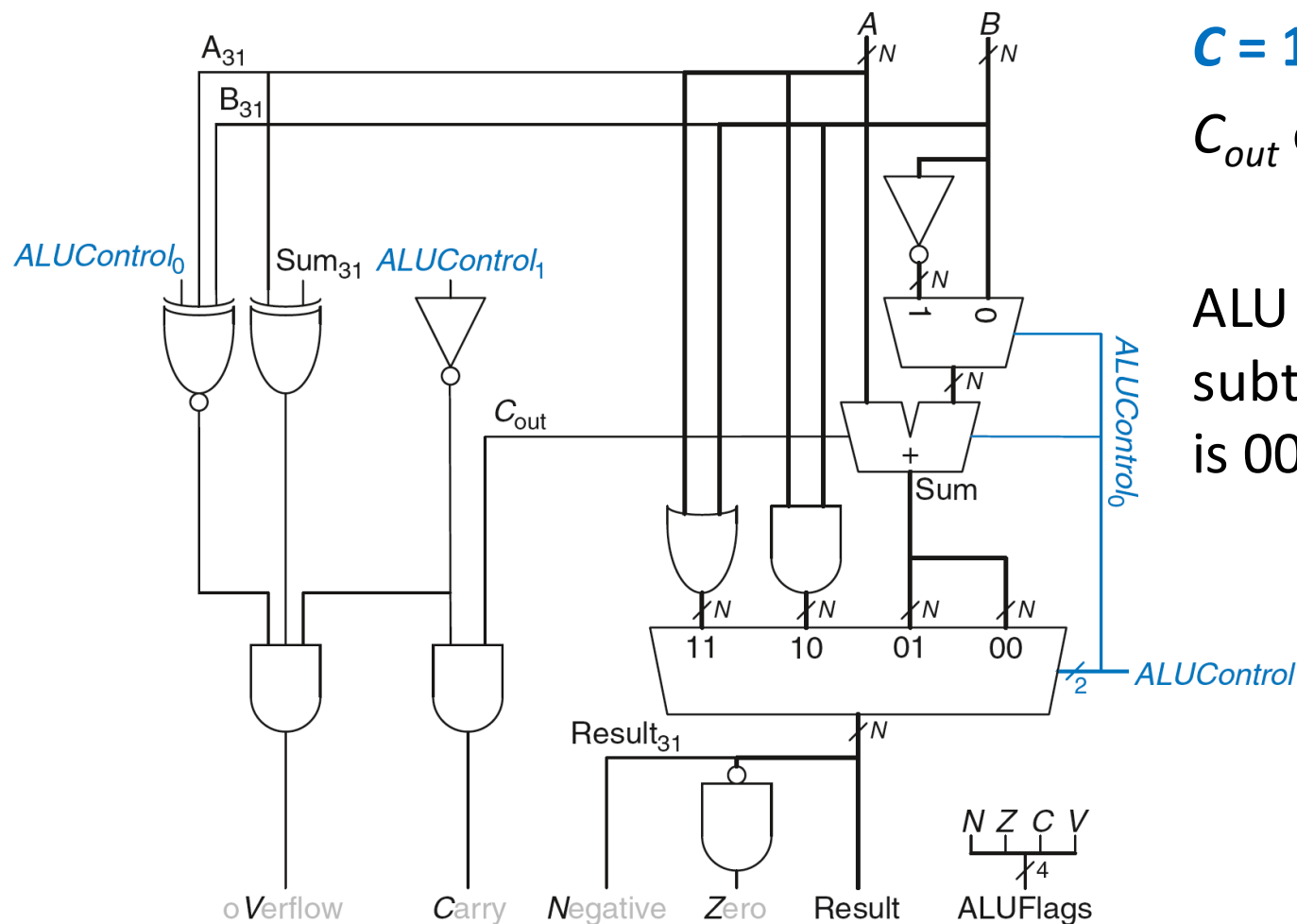

**C = 1** if:


$C_{out}$  of Adder is 1

**AND**

ALU is adding or  
subtracting (ALUControl  
is 00 or 01)




# ALU with Status Flags: o**V**erflow

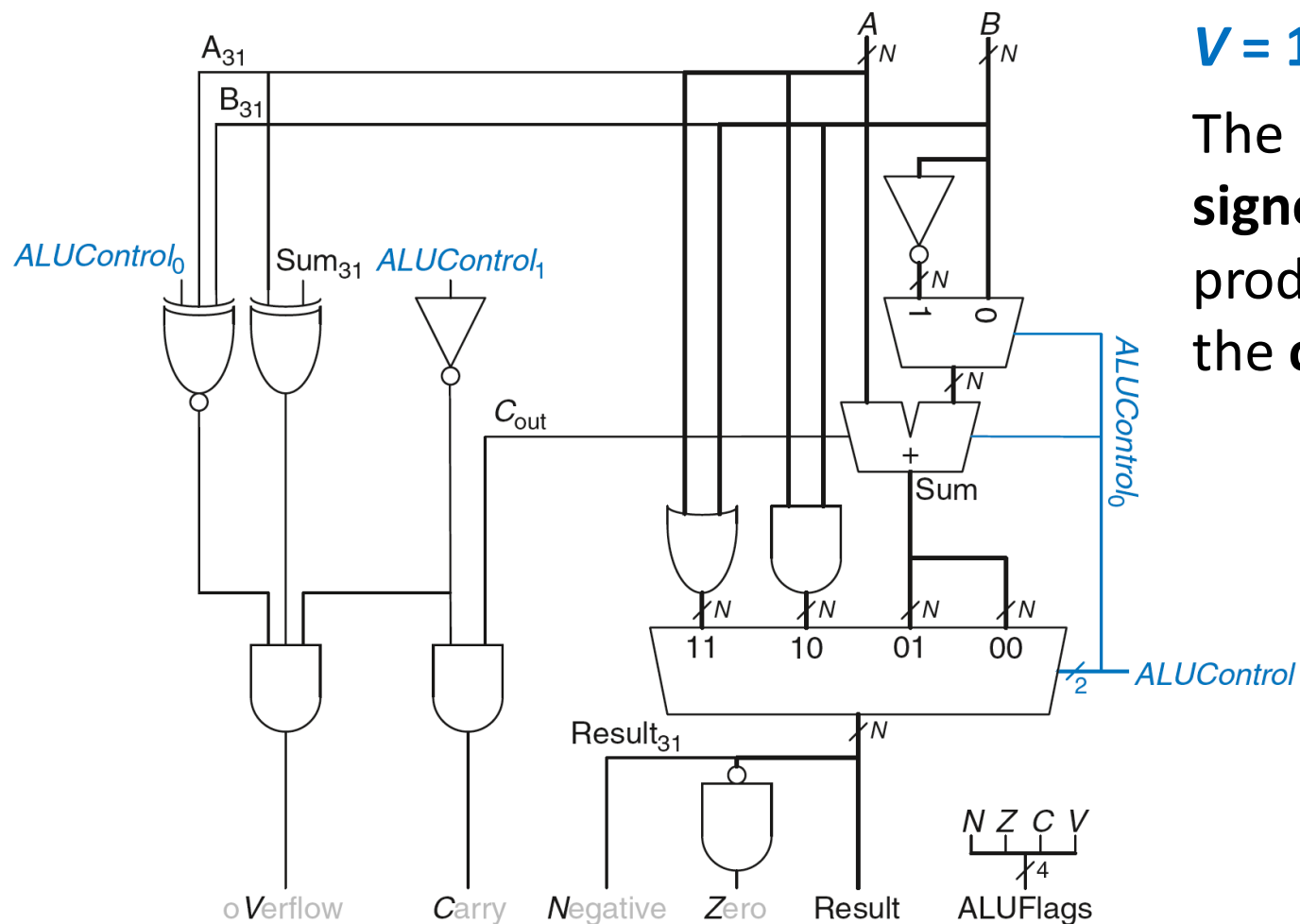

**V = 1** if:

The addition of 2 **same-signed numbers** produces a result with the **opposite sign**

# ALU with Status Flags: o**V**erflow

 

**$V = 1$**  if:

ALU is performing addition or subtraction

( $ALUControl_1 = 0$ )

**AND**

A and Sum have opposite signs

**AND**

A and B have same signs for addition


( $ALUControl_0 = 0$ )

**OR**

A and B have different signs for subtraction

( $ALUControl_0 = 1$ )

# ALU with Status Flags

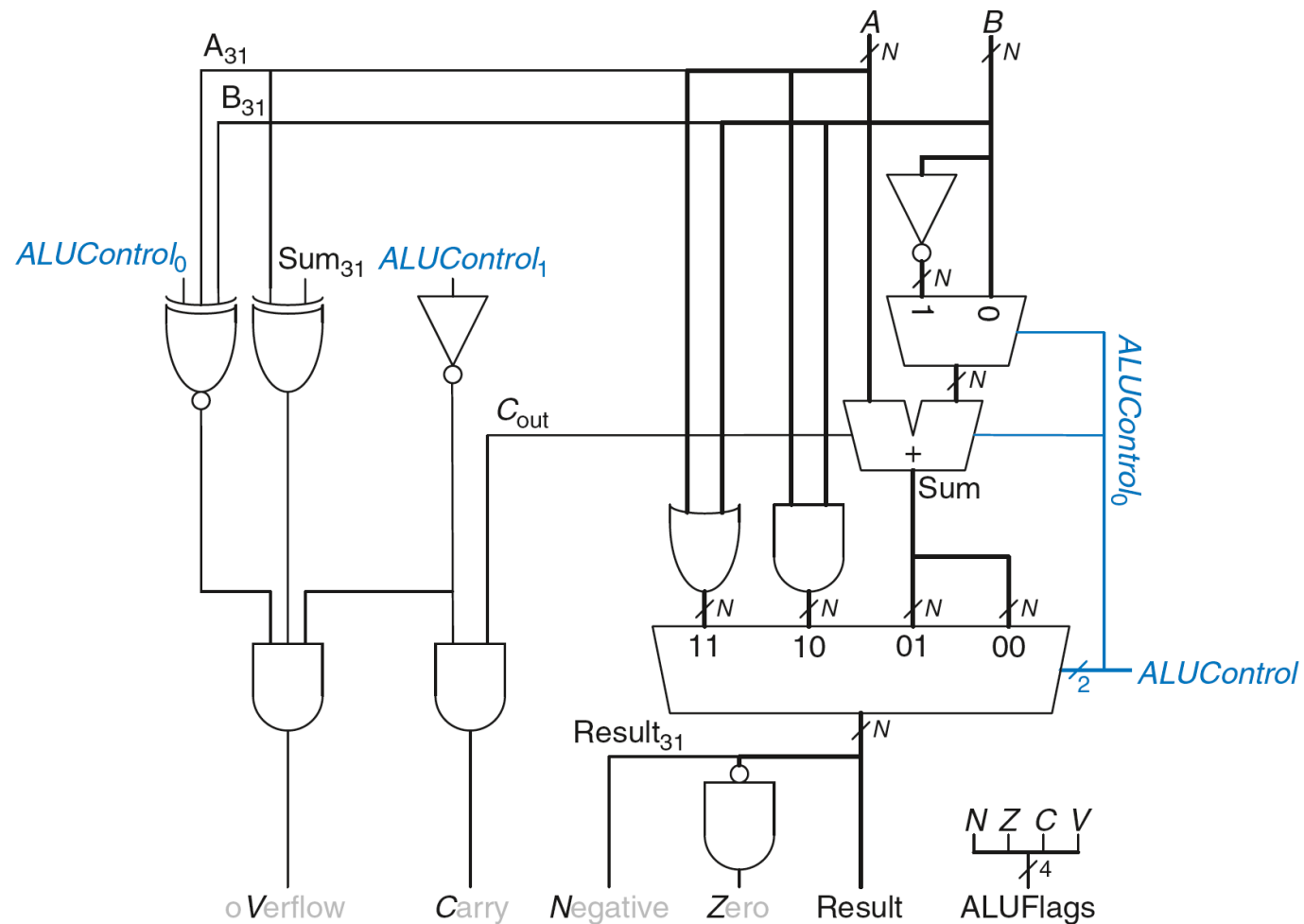

# Comparison based on Flags

Compare by subtracting and checking flags

Different for signed and unsigned


Comparison	Signed	Unsigned
==	Z	Z
!=	$\sim Z$	$\sim Z$
<	$N \wedge V$	$\sim C$
<=	$Z \mid (N \wedge V)$	$Z \mid \sim C$
>	$\sim Z \ \& \ \sim(N \wedge V)$	$\sim Z \ \& \ C$
>=	$\sim(N \wedge V)$	C

# Other ALU Operations

- **Set Less Than** (also called Set if Less Than)
  - **Sets lsb** of result if  $A < B$ 
    - Result = 0000...001 if  $A < B$
    - Result = 0000...000 otherwise
  - Comes in signed and unsigned flavors
- **XOR**
  - Result =  $A \text{ XOR } B$

# Extending ALU: SLT

ALUControl <sub>2:0</sub>	Function
00	add
01	subtract
10	and
11	or
	<b>SLT</b>

 

## Chapter 5: Digital Building Blocks

# **Shifters, Multipliers, & Dividers**

# Shifters

**Logical shifter:** shifts value to left or right and fills empty spaces with 0's

- Ex:  $11001 \gg 2 =$
- Ex:  $11001 \ll 2 =$

**Arithmetic shifter:** same as logical shifter, but on right shift, fills empty spaces with the old most significant bit (msb)

- Ex:  $11001 \ggg 2 =$
- Ex:  $11001 \lll 2 =$


**Rotator:** rotates bits in a circle, such that bits shifted off one end are shifted into the other end

- Ex:  $11001 \text{ ROR } 2 =$
- Ex:  $11001 \text{ ROL } 2 =$




# Shifter Design





Shift Left

 

Logical Shift Right

 

Arithmetic Shift Right

    

# Shifters as Multipliers and Dividers

- $A \ll N = A \times 2^N$
- $A \gg N = A \div 2^N$

# Multipliers

- **Partial products** formed by multiplying a single digit of the multiplier with multiplicand
- **Shifted** partial products **summed** to form result

## Decimal

$$\begin{array}{r} 230 \\ \times 42 \\ \hline 460 \\ + 920 \\ \hline 9660 \end{array}$$

multiplicand  
multiplier  
partial  
products

result

$$230 \times 42 = 9660$$


## Binary

$$\begin{array}{r} 0101 \\ \times 0111 \\ \hline 0101 \\ 0101 \\ 0101 \\ + 0000 \\ \hline 0100011 \end{array}$$

$$5 \times 7 = 35$$
 
# 4 x 4 Multiplier

$$\begin{array}{r}
 \begin{array}{cccc}
 & A_3 & A_2 & A_1 & A_0 \\
 x & B_3 & B_2 & B_1 & B_0 \\
 \hline
 & A_3B_0 & A_2B_0 & A_1B_0 & A_0B_0 \\
 & A_3B_1 & A_2B_1 & A_1B_1 & A_0B_1 \\
 & A_3B_2 & A_2B_2 & A_1B_2 & A_0B_2 \\
 + & A_3B_3 & A_2B_3 & A_1B_3 & A_0B_3 \\
 \hline
 P_7 & P_6 & P_5 & P_4 & P_3 & P_2 & P_1 & P_0
 \end{array}
 \end{array}$$



# Dividers

$$A/B = Q + R/B$$

**Decimal Example:**  $2584/15 = 172 \text{ R}4$

**Long-Hand:**

$$\begin{array}{r} 172 \text{ R}4 \\ 15 \overline{) 2584} \\ \underline{-15} \phantom{00} \\ 108 \phantom{00} \\ \underline{-105} \phantom{00} \\ 34 \phantom{00} \\ \underline{-30} \phantom{00} \\ 4 \end{array}$$

**Long-Hand Revisited:**

$$\begin{array}{r} 0002 \\ - 15 \\ \hline -13 \end{array} \quad \begin{array}{r} 0 \\ \hline 3 \phantom{0} \phantom{0} \phantom{0} \phantom{0} \end{array}$$
$$\begin{array}{r} 0025 \\ - 15 \\ \hline 10 \end{array} \quad \begin{array}{r} 0 \phantom{0} 1 \\ \hline 3 \phantom{0} \phantom{0} \phantom{0} \phantom{0} \end{array}$$
$$\begin{array}{r} 0108 \\ - 105 \\ \hline 3 \end{array} \quad \begin{array}{r} 0 \phantom{0} 1 \phantom{0} 7 \\ \hline 3 \phantom{0} \phantom{0} \phantom{0} \phantom{0} \end{array}$$
$$\begin{array}{r} 0034 \\ - 30 \\ \hline 4 \end{array} \quad \begin{array}{r} 0 \phantom{0} 1 \phantom{0} 7 \phantom{0} 2 \\ \hline 3 \phantom{0} \phantom{0} \phantom{0} \phantom{0} \end{array}$$

# Dividers

$$A/B = Q + R/B$$

**Decimal:** 2584/15 = 172 R4    **Binary:** 1101/0010 = 0110 R1

$$\begin{array}{r} 0002 \\ - 15 \\ \hline -13 \end{array}$$

$$\begin{array}{r} 0 \\ \hline 3 \end{array} \begin{array}{r} \phantom{0} \\ \hline 2 \end{array} \begin{array}{r} \phantom{0} \\ \hline 1 \end{array} \begin{array}{r} \phantom{0} \\ \hline 0 \end{array}$$

$$\begin{array}{r} 0025 \\ - 15 \\ \hline 10 \end{array}$$

$$\begin{array}{r} 0 \phantom{0} 1 \\ \hline 3 \end{array} \begin{array}{r} \phantom{0} \\ \hline 2 \end{array} \begin{array}{r} \phantom{0} \\ \hline 1 \end{array} \begin{array}{r} \phantom{0} \\ \hline 0 \end{array}$$

$$\begin{array}{r} 0108 \\ - 105 \\ \hline 3 \end{array}$$

$$\begin{array}{r} 0 \phantom{0} 1 \phantom{0} 7 \\ \hline 3 \end{array} \begin{array}{r} \phantom{0} \\ \hline 2 \end{array} \begin{array}{r} \phantom{0} \\ \hline 1 \end{array} \begin{array}{r} \phantom{0} \\ \hline 0 \end{array}$$

$$\begin{array}{r} 0034 \\ - 30 \\ \hline 4 \end{array}$$

$$\begin{array}{r} 0 \phantom{0} 1 \phantom{0} 7 \phantom{0} 2 \\ \hline 3 \end{array} \begin{array}{r} \phantom{0} \\ \hline 2 \end{array} \begin{array}{r} \phantom{0} \\ \hline 1 \end{array} \begin{array}{r} \phantom{0} \\ \hline 0 \end{array}$$

$$\begin{array}{r} 0001 \\ - 0010 \\ \hline 1111 \end{array}$$

$$\begin{array}{r} 0 \\ \hline 3 \end{array} \begin{array}{r} \phantom{0} \\ \hline 2 \end{array} \begin{array}{r} \phantom{0} \\ \hline 1 \end{array} \begin{array}{r} \phantom{0} \\ \hline 0 \end{array}$$

$$\begin{array}{r} 0011 \\ - 0010 \\ \hline 0001 \end{array}$$

$$\begin{array}{r} 0 \phantom{0} 1 \\ \hline 3 \end{array} \begin{array}{r} \phantom{0} \\ \hline 2 \end{array} \begin{array}{r} \phantom{0} \\ \hline 1 \end{array} \begin{array}{r} \phantom{0} \\ \hline 0 \end{array}$$

$$\begin{array}{r} 0010 \\ - 0010 \\ \hline 0000 \end{array}$$

$$\begin{array}{r} 0 \phantom{0} 1 \phantom{0} 1 \\ \hline 3 \end{array} \begin{array}{r} \phantom{0} \\ \hline 2 \end{array} \begin{array}{r} \phantom{0} \\ \hline 1 \end{array} \begin{array}{r} \phantom{0} \\ \hline 0 \end{array}$$

$$\begin{array}{r} 0001 \\ - 0010 \\ \hline 1111 \end{array}$$

$$\begin{array}{r} 0 \phantom{0} 1 \phantom{0} 1 \phantom{0} 0 \\ \hline 3 \end{array} \begin{array}{r} \phantom{0} \\ \hline 2 \end{array} \begin{array}{r} \phantom{0} \\ \hline 1 \end{array} \begin{array}{r} \phantom{0} \\ \hline 0 \end{array} \text{ R1}$$

# Dividers

$$A/B = Q + R/B$$

$$R' = 0$$

for  $i = N-1$  to 0

$$R = \{R' \ll 1, A_i\}$$

$$D = R - B$$

if  $D < 0$ ,  $Q_i = 0$ ;  $R' = R$


else  $Q_i = 1$ ;  $R' = D$

$$R = R'$$

**Binary:**  $1101/10 = 0110 \text{ R}1$



$\begin{array}{r} 0001 \\ -0010 \\ \hline 1111 \end{array}$	$\begin{array}{cccc} 0 & & & \\ \hline 3 & 2 & 1 & 0 \end{array}$
$\begin{array}{r} 0011 \\ -0010 \\ \hline 0001 \end{array}$	$\begin{array}{cccc} 0 & 1 & & \\ \hline 3 & 2 & 1 & 0 \end{array}$
$\begin{array}{r} 0010 \\ -0010 \\ \hline 0000 \end{array}$	$\begin{array}{cccc} 0 & 1 & 1 & \\ \hline 3 & 2 & 1 & 0 \end{array}$
$\begin{array}{r} 0001 \\ -0010 \\ \hline 1111 \end{array}$	$\begin{array}{cccc} 0 & 1 & 1 & 0 \\ \hline 3 & 2 & 1 & 0 \end{array} \text{ R}1$

# 4 x 4 Divider

 

Each row computes one iteration of the division algorithm.

Legend

  

**Division:**  $A/B = Q + R/B$

$R' = 0$

for  $i = N-1$  to  $0$

$R = \{R' \ll 1, A_i\}$

$D = R - B$


if  $D < 0$ ,  $Q_i=0$ ,  $R'=R$

else  $Q_i=1$ ,  $R'=D$



$R=R'$



# 4 x 4 Divider

 

Legend

  

0001	
-0010	0 3 2 1 0
1111	
0011	
-0010	0 1 3 2 1 0
0001	
0010	
-0010	0 1 1 3 2 1 0
0000	
0001	
-0010	0 1 1 0 3 2 1 0 R1
1111	

Each row computes one iteration of the division algorithm.

## Chapter 5: Digital Building Blocks

# **Fixed-Point Numbers**

# Number Systems

Numbers we can represent using binary representations

- **Positive numbers**
  - Unsigned binary
- **Negative numbers**
  - Two's complement
  - Sign/magnitude numbers

What about **fractions**?

# Numbers with Fractions

Two common notations:

- **Fixed-point:** binary point fixed
- **Floating-point:** binary point floats to the right of the most significant 1

# Fixed-Point Numbers

- 6.75 using 4 integer bits and 4 fraction bits:

01101100

0110.1100

$$2^2 + 2^1 + 2^{-1} + 2^{-2} = 6.75$$

- Binary point is implied
- The number of integer and fraction bits must be agreed upon beforehand

# Unsigned Fixed Point Formats

- **Ua.b**: unsigned number with
  - **a** integer bits
  - **b** fractional bits.
- **Example: 6.75** is
  - **U4.4**: 01101100
  - **U3.5**: 11011000
  - **U6.2**: 00011011
- 8, 16, and 32-bit fixed point numbers are common
  - **U8.8** often represents sensor data, audio, pixels
  - **U16.16** used for higher precision signal processing

# Signed Fixed Point Formats

- **Qa.b:** signed 2's complement number with
  - **a** integer bits (including the sign bit)
  - **b** fractional bits
- **To negate a Q fixed point number:**
  - Invert the bits
  - Add one to the LSB
- **Example:** write **-6.75** in Q4.4
  - $6.75 =$  01101100
  - Invert: 10010011
  - Add 1 LSB: 10010100
- **Q1.15** (aka Q15) is common for signal processing (1, -1]

# Saturating Arithmetic

- Fixed point **overflow** is usually bad
  - Produces undesired artifacts:
    - Video: dark pixel in middle of bright pixels
    - Audio: clicking sounds
- **Saturating arithmetic**
  - Instead of overflowing, use largest value
  - In U4.4:  $11000000 + 01111000 = 11111111$   
 $12 \quad \quad + 7.5 \quad \quad = 15.9375$



## Chapter 5: Digital Building Blocks

# **Floating-Point Numbers**

# Floating-Point Numbers

- Binary point floats to the right of the most significant 1
- Similar to decimal scientific notation

- For example, write  $273_{10}$  in scientific notation:

$$273 = 2.73 \times 10^2$$

- In general, a number is written in scientific notation as:


$$\pm M \times B^E$$

- $M$  = mantissa
- $B$  = base
- $E$  = exponent
- In the example,  $M = 2.73$ ,  $B = 10$ , and  $E = 2$

# Floating vs. Fixed Point Numbers

- Floating point numbers are like **scientific notation**
  - Allow a **greater dynamic range** of smallest to largest
  - **Arithmetic is harder**
    - Mantissa must be aligned before adding
    - This costs performance and power
- Fixed point numbers are **harder for the programmer**
  - **Smaller dynamic range**
  - Take care of **overflow**
- **Floating Point** is preferred for general-purpose computing where programming time is most important
- **Fixed Point** is preferred for signal processing performance, power, and hardware cost matter most
  - Machine learning, video

# Floating-Point Numbers

 

- **Example:** represent the value  $228_{10}$  using a 32-bit floating point representation

We show three versions – **the final version** is called the:

**IEEE 754 floating-point standard**

# Floating-Point Representation 1

1. Convert decimal to binary:


$$228_{10} = 11100100_2$$

2. Write the number in “binary scientific notation”:

$$11100100_2 = 1.11001_2 \times 2^7$$

 
3. Fill in each field of the 32-bit floating point number:

- The sign bit is positive (0)
- The 8 exponent bits represent the value 7
- The remaining 23 bits are the mantissa


 
# Floating-Point Representation 2

- First bit of the mantissa is always 1:
  - $228_{10} = 11100100_2 = \mathbf{1.11001} \times 2^7$
- So, no need to store it: *implicit leading 1*
- Store just **fraction bits** in 23-bit field



# Floating-Point Representation 3


- **Biased exponent:** bias = 127 ( $01111111_2$ )

- Biased exponent = bias + exponent

- Exponent of 7 is stored as:

$$127 + 7 = 134 = 0x10000110_2$$

 - The **IEEE 754 32-bit floating-point representation** of  $228_{10}$



in hexadecimal: **0x43640000**

# Floating-Point Example

Write  $-58.25_{10}$  in floating point (IEEE 754)

1. Convert magnitude of decimal to binary:

$$58.25_{10} = 111010.01_2$$

2. Write in binary scientific notation:


$$1.1101001 \times 2^5$$

3. Fill in fields:

Sign bit: 1 (negative)

8 exponent bits:  $(127 + 5) = 132 = 10000100_2$

 23 fraction bits: 110 1001 0000 0000 0000 0000



in hexadecimal: 0xC2690000



# Floating-Point Special Cases

Number	Sign	Exponent	Fraction
0	X	00000000	0000000000000000000000000000
$\infty$	0	11111111	0000000000000000000000000000
$-\infty$	1	11111111	0000000000000000000000000000
NaN	X	11111111	non-zero

# Floating-Point Precision

- **Single-Precision:**

- 32-bit
- 1 sign bit, 8 exponent bits, 23 fraction bits
- bias = 127

- **Double-Precision:**

- 64-bit
- 1 sign bit, 11 exponent bits, 52 fraction bits
- bias = 1023

# Floating-Point Rounding & Overflow

- **Overflow:** number too large to be represented
- **Underflow:** number too small to be represented
- **Rounding modes:**
  - Down
  - Up
  - Toward zero
  - To nearest
- **Example:** round 1.100101 (1.578125) to only 3 fraction bits
  - **Down:** 1.100
  - **Up:** 1.101
  - **Toward zero:** 1.100
  - **To nearest:** 1.101 (1.625 is closer to 1.578125 than 1.5 is)

## Chapter 5: Digital Building Blocks

# **Floating-Point Addition**

# Floating-Point Addition

1. **Extract** exponent and fraction bits
2. **Prepend** leading 1 to form mantissa
3. **Compare** exponents
4. **Shift** smaller mantissa if necessary
5. **Add** mantissas
6. **Normalize** mantissa and adjust exponent if necessary
7. **Round** result
8. **Assemble** exponent and fraction back into floating-point format

# Floating-Point Addition Example

**Add the following floating-point numbers:**

0x3FC00000

0x40500000

# Floating-Point Addition Example

## 1. Extract exponent and fraction bits

	1 bit	8 bits	23 bits
0x3FC00000	0	01111111	100 0000 0000 0000 0000 0000
	Sign	Exponent	Fraction
	1 bit	8 bits	23 bits
0x40500000	0	10000000	101 0000 0000 0000 0000 0000
	Sign	Exponent	Fraction

For first number (N1):  $S = 0, E = 127, F = .1$

For second number (N2):  $S = 0, E = 128, F = .101$

## 2. Prepend leading 1 to form mantissa

N1: 1.1

N2: 1.101

# Floating-Point Addition Example

## 3. Compare exponents

$127 - 128 = -1$ , so shift N1 right by 1 bit

## 4. Shift smaller mantissa if necessary

shift N1's mantissa:  $1.1 \gg 1 = 0.11$  ( $\times 2^1$ )

## 5. Add mantissas

$$\begin{array}{r} 0.11 \times 2^1 \\ + 1.101 \times 2^1 \\ \hline 10.011 \times 2^1 \end{array}$$



# Floating-Point Addition Example

6. **Normalize mantissa and adjust exponent if necessary**

$$10.011 \times 2^1 = 1.0011 \times 2^2$$

7. **Round result**

No need (fits in 23 bits)

8. **Assemble exponent and fraction back into floating-point format**

$$S = 0, E = 2 + 127 = 129 = 10000001_2, F = 001100\dots$$

1 bit	8 bits	23 bits
0	10000001	001 1000 0000 0000 0000 0000
<b>Sign</b>	<b>Exponent</b>	<b>Fraction</b>

in hexadecimal: **0x40980000**

## Chapter 5: Digital Building Blocks


# **Counters & Shift Registers**

# Counters

- Increments on each clock edge
- Used to cycle through numbers. For example,
  - 000, 001, 010, 011, 100, 101, 110, 111, 000, 001...
- **Example uses:**
  - Digital clock displays
  - Program counter: keeps track of current instruction executing

**Symbol**

**Implementation**

 

# Counter SystemVerilog Idiom

```
module counter(input  logic      clk, reset,
               output logic [7:0] q);
```

```
    always_ff @(posedge clk)
        if (reset) q <= 0;    // synchronous reset
        else      q <= q+1; //
end
```

```
// alternative more verbose
module counter(input  logic      clk, reset,
               output logic [7:0] q);

    logic [7:0] nextq;

    assign nextq = q + 1; // adder
    always_ff @(posedge clk) // state register with synchronous reset
        if (reset) q <= 0;
        else      q <= nextq;
end
```

# Divide-by- $2^N$ Counter

- Most significant bit of an N-bit counter toggles every  $2^N$  cycles.
- Useful for slowing a clock. Ex: blink an LED
- Example: 50 MHz clock, 24-bit counter
  - 2.98 Hz


# Digitally Controlled Oscillator

- N-bit counter
- Add p on each cycle, instead of 1
- Most significant bit toggles at  $f_{\text{out}} = f_{\text{clk}} * p / 2^N$
- Example:  $f_{\text{clk}} = 50 \text{ MHz}$  clock
  - How to generate a  $f_{\text{out}} = 200 \text{ Hz}$  signal?
  - $p/2^N = 200 / 50 \text{ MHz}$
- Try  $N = 24, p = 67 \rightarrow f_{\text{out}} = 199.676 \text{ Hz}$
- Or  $N = 32, p = 17179 \rightarrow f_{\text{out}} = 199.990 \text{ Hz}$


# Shift Registers

- Shift a new bit in on each clock edge
- Shift a bit out on each clock edge
- *Serial-to-parallel converter*: converts serial input ( $S_{in}$ ) to parallel output ( $Q_{0:N-1}$ )

**Symbol:**

 


**Implementation:**

 
 
# Shift Register with Parallel Load

- When  $Load = 1$ , acts as a normal  $N$ -bit register
- When  $Load = 0$ , acts as a shift register
- Now can act as a *serial-to-parallel converter* ( $S_{in}$  to  $Q_{0:N-1}$ ) or a *parallel-to-serial converter* ( $D_{0:N-1}$  to  $S_{out}$ )





# Shift Register SystemVerilog Idiom

```
module shiftreg #(parameter N=8)
    (input  logic      clk,
     input  logic      reset, load,
     input  logic      sin,
     input  logic [N-1:0] d,
     output logic [N-1:0] q,
     output logic      sout);

    always_ff @(posedge clk, posedge reset)
        if (reset)      q <= 0;
        else if (load) q <= d;
        else            q <= {q[N-2:0], sin};


    assign sout = q[N-1];
end
```

# Chapter 5: Digital Building Blocks

## **Memory**


 
# Memory Arrays

- Efficiently store large amounts of data
- $M$ -bit data value read/written at each unique  $N$ -bit address
- 3 common types:
  - Dynamic random access memory (DRAM)
  - Static random access memory (SRAM)
  - Read only memory (ROM)


  
# Memory Arrays


- 2-dimensional array of bit cells
- Each bit cell stores one bit
- $N$  address bits and  $M$  data bits:
  - $2^N$  rows and  $M$  columns
  - **Depth:** number of rows (number of words)
  - **Width:** number of columns (size of word)
  - **Array size:** depth  $\times$  width =  $2^N \times M$




Address	Data			
11	0	1	0	depth ↑ ↓
10	1	0	0	
01	1	1	0	
00	0	1	1	
	width ←→			
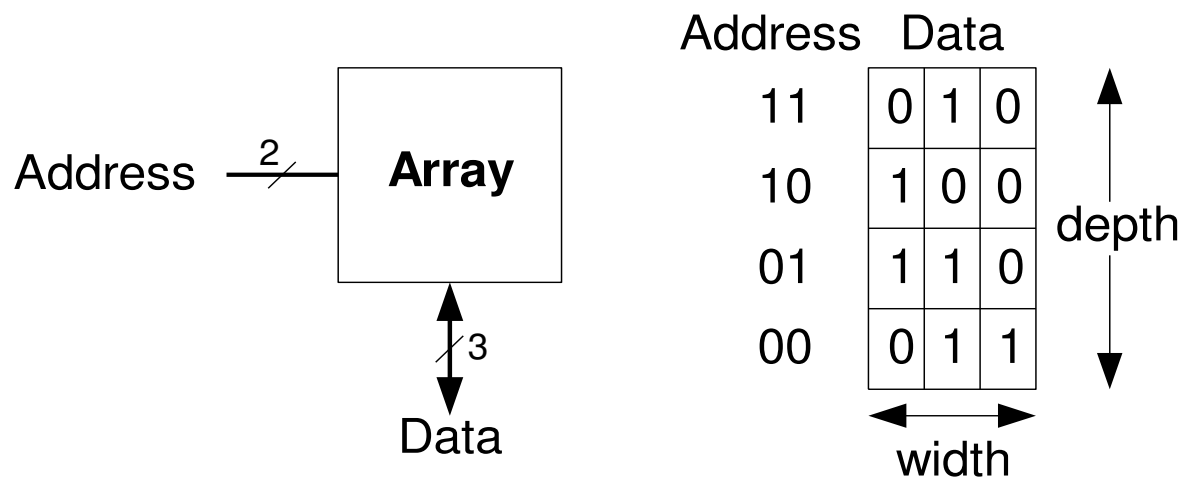
# Memory Array Example



- $2^2 \times 3$ -bit array
- Number of words: 4
- Word size: 3-bits
- For example, the 3-bit word stored at address 10 is 100



# Memory Arrays

 


# Memory Array Bit Cells

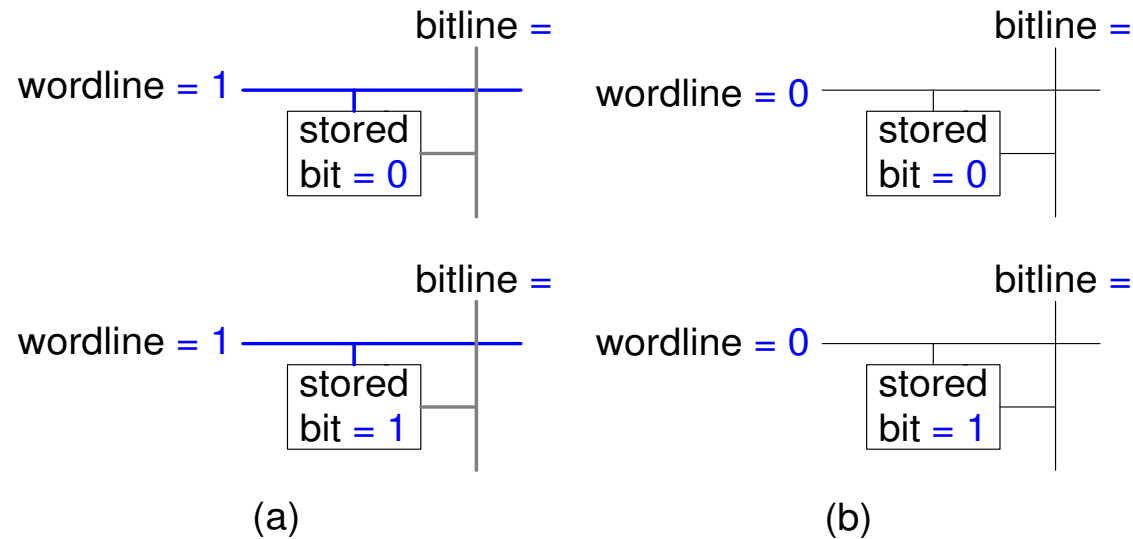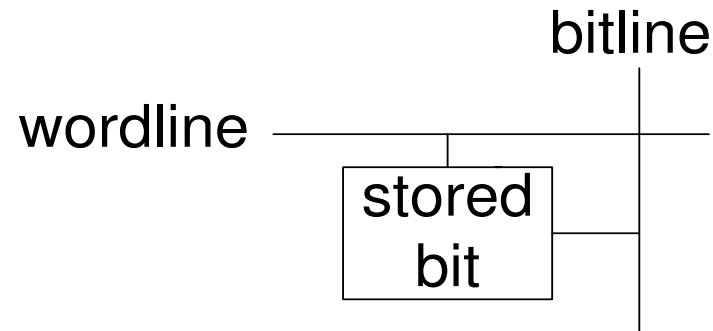
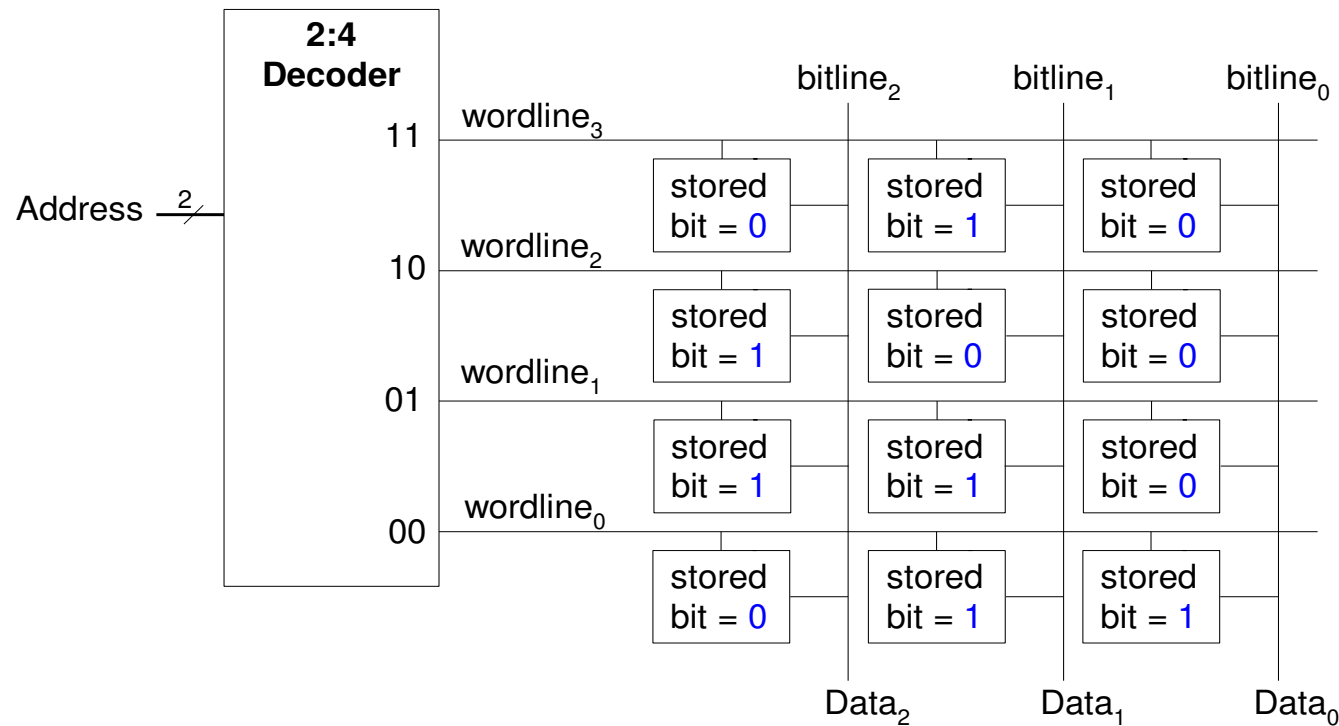
# Memory Array

- **Wordline:**

- like an enable
- single row in memory array read/written
- corresponds to unique address
- only one wordline **HIGH** at once





# Types of Memory

- Random access memory (RAM): **volatile**
- Read only memory (ROM): **nonvolatile**

# RAM: Random Access Memory

- **Volatile:** loses its data when power off
- Read and written quickly
- Main memory in your computer is RAM (DRAM)

Historically called *random access* memory because any data word accessed as easily as any other (in contrast to sequential access memories such as a tape recorder)

# ROM: Read Only Memory

- **Nonvolatile:** retains data when power off
- Read quickly, but writing is impossible or slow
- Flash memory in cameras, thumb drives, and digital cameras are all ROMs

Historically called *read only* memory because ROMs were written at time of fabrication or by burning fuses. Once a ROM was configured, it could not be written again. This is no longer the case for Flash memory and other types of ROMs.

# Chapter 5: Digital Building Blocks

**RAM**

# Types of RAM

- **DRAM** (Dynamic random access memory)
- **SRAM** (Static random access memory)
- Differ in how they store data:
  - DRAM uses a capacitor
  - SRAM uses cross-coupled inverters


# Robert Dennard, 1932 -

- Invented DRAM in 1966 at IBM
- Others were skeptical that the idea would work
- By the mid-1970's DRAM in virtually all computers




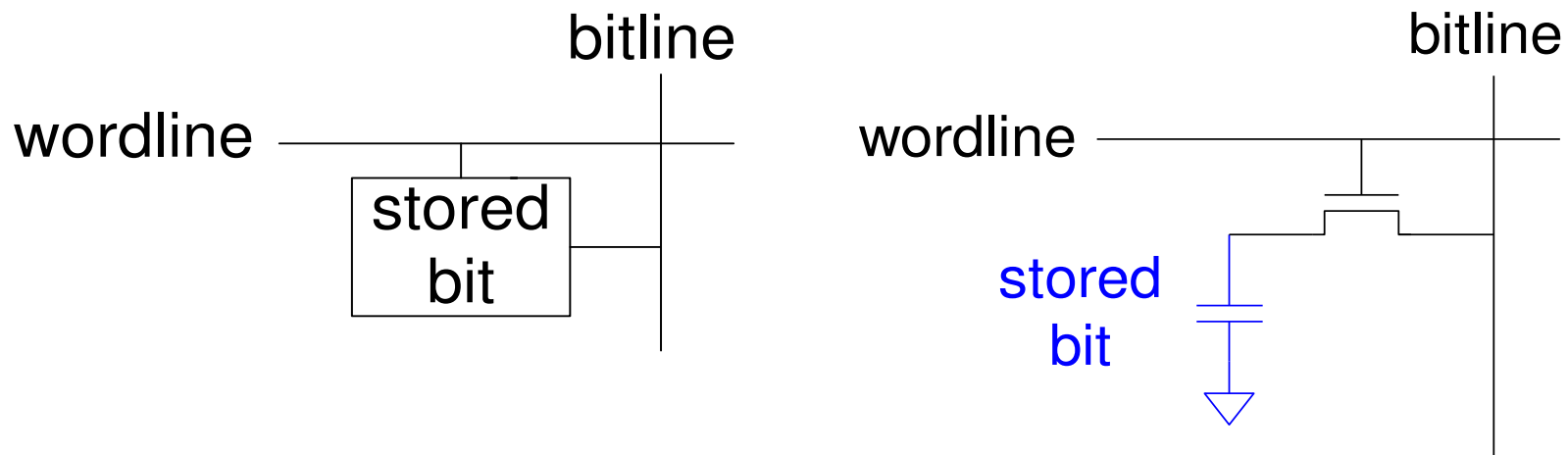
# DRAM

- Data bits stored on **capacitor**
- *Dynamic* because the value needs to be **refreshed** (rewritten) periodically and after read:
  - Charge leakage from the capacitor degrades the value
  - Reading destroys the stored value





# DRAM

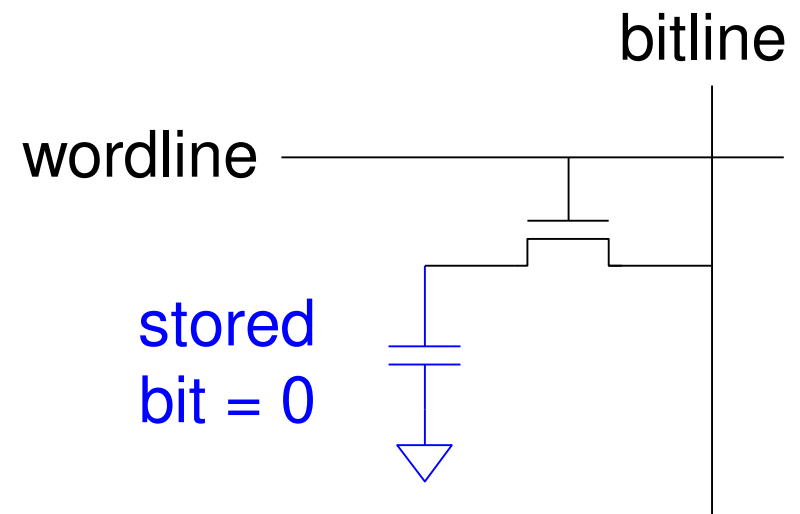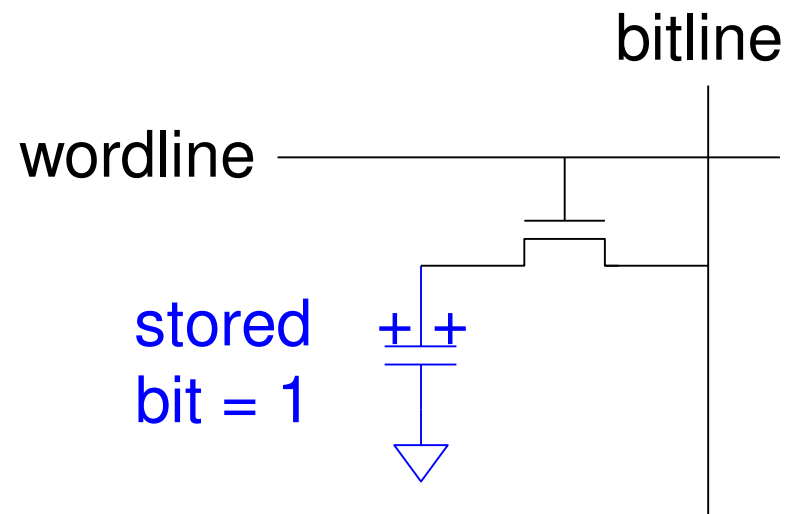





# SRAM

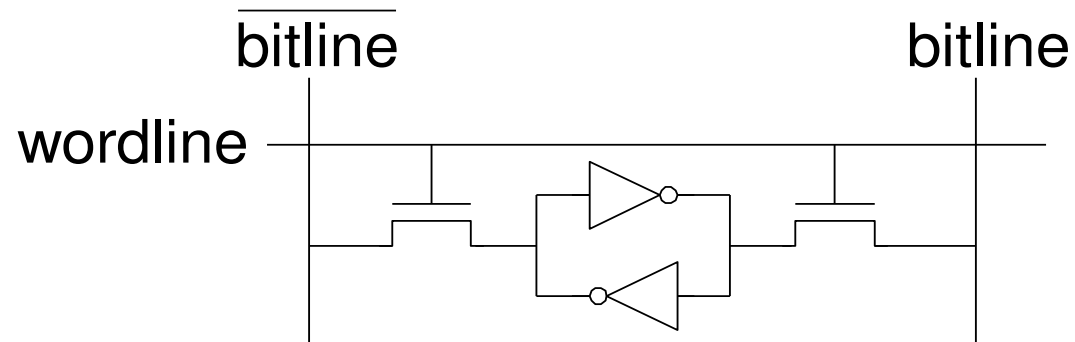 


# Memory Arrays Review

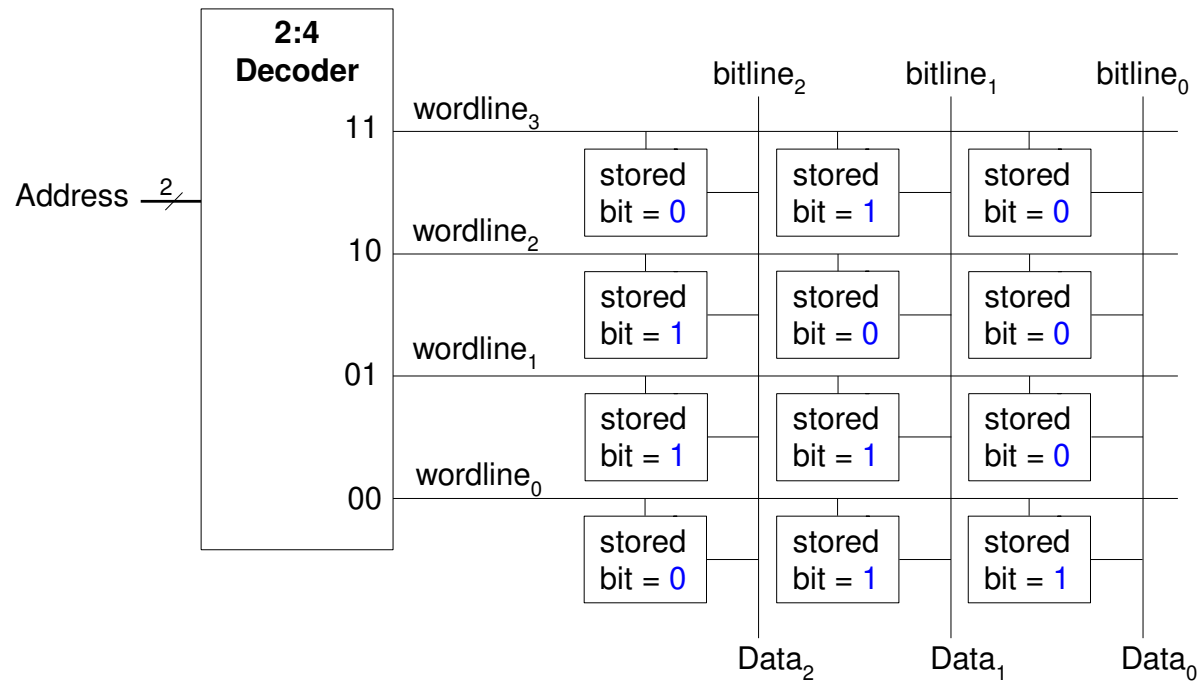

**DRAM bit cell:**

 


**SRAM bit cell:**

 


# Chapter 5: Digital Building Blocks

**ROM**

# ROM: Dot Notation

 

# ROM Storage

 

Address	Data		
11	0	1	0
10	1	0	0
01	1	1	0
00	0	1	1

width


depth

# Fujio Masuoka, 1944 -

- Developed memories and high speed circuits at Toshiba, 1971-1994
- Invented Flash memory as an unauthorized project pursued during nights and weekends in the late 1970's
- The process of erasing the memory reminded him of the flash of a camera
- Toshiba slow to commercialize the idea; Intel was first to market in 1988
- Flash has grown into a \$25 billion per year market



# ROM Logic

 

$$Data_2 = A_1 \oplus A_0$$


$$Data_1 = \bar{A}_1 + A_0$$

$$Data_0 = \bar{A}_1 \bar{A}_0$$
 
# Example: Logic with ROMs


Implement the following logic functions using a  $2^2 \times 3$ -bit ROM:

- $X = AB$
- $Y = A + B$
- $Z = A \overline{B}$





# Logic with Any Memory Array

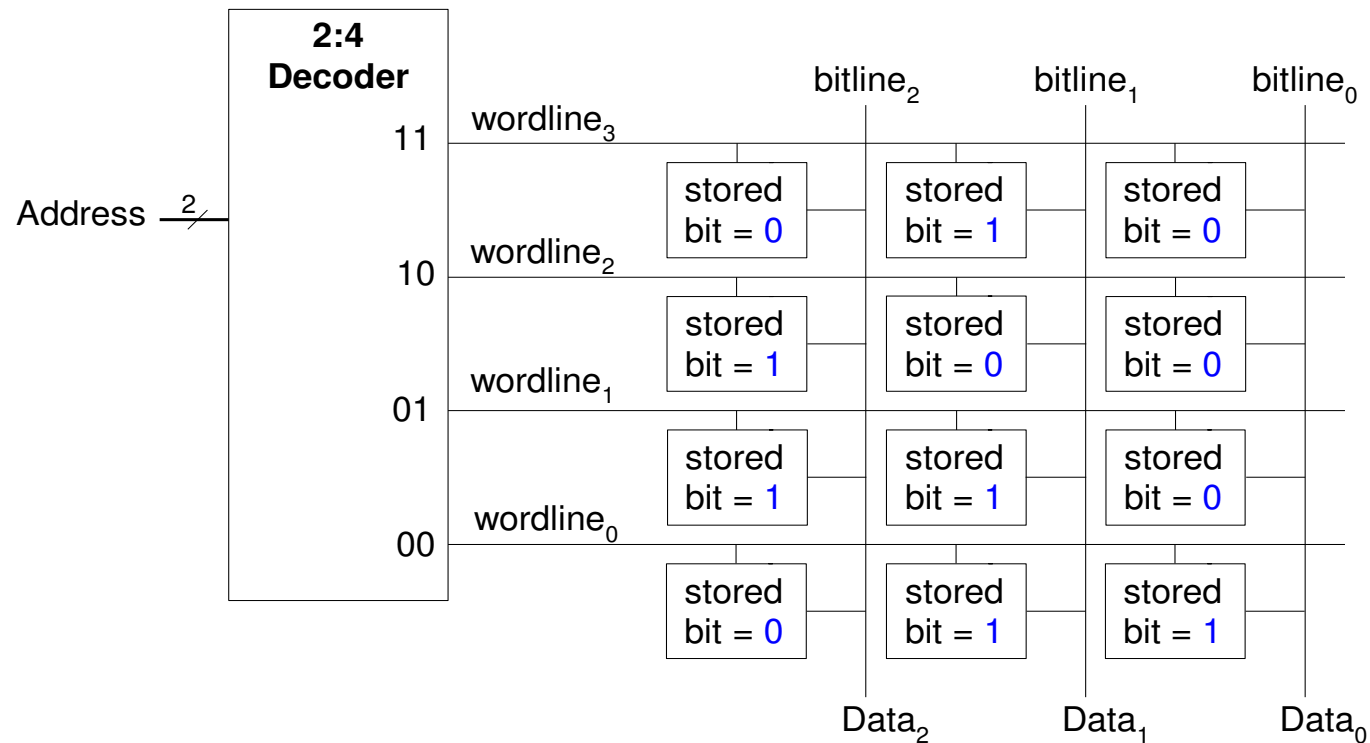

$Data_2 =$  \_\_\_\_\_


$Data_1 =$  \_\_\_\_\_

$Data_0 =$  \_\_\_\_\_
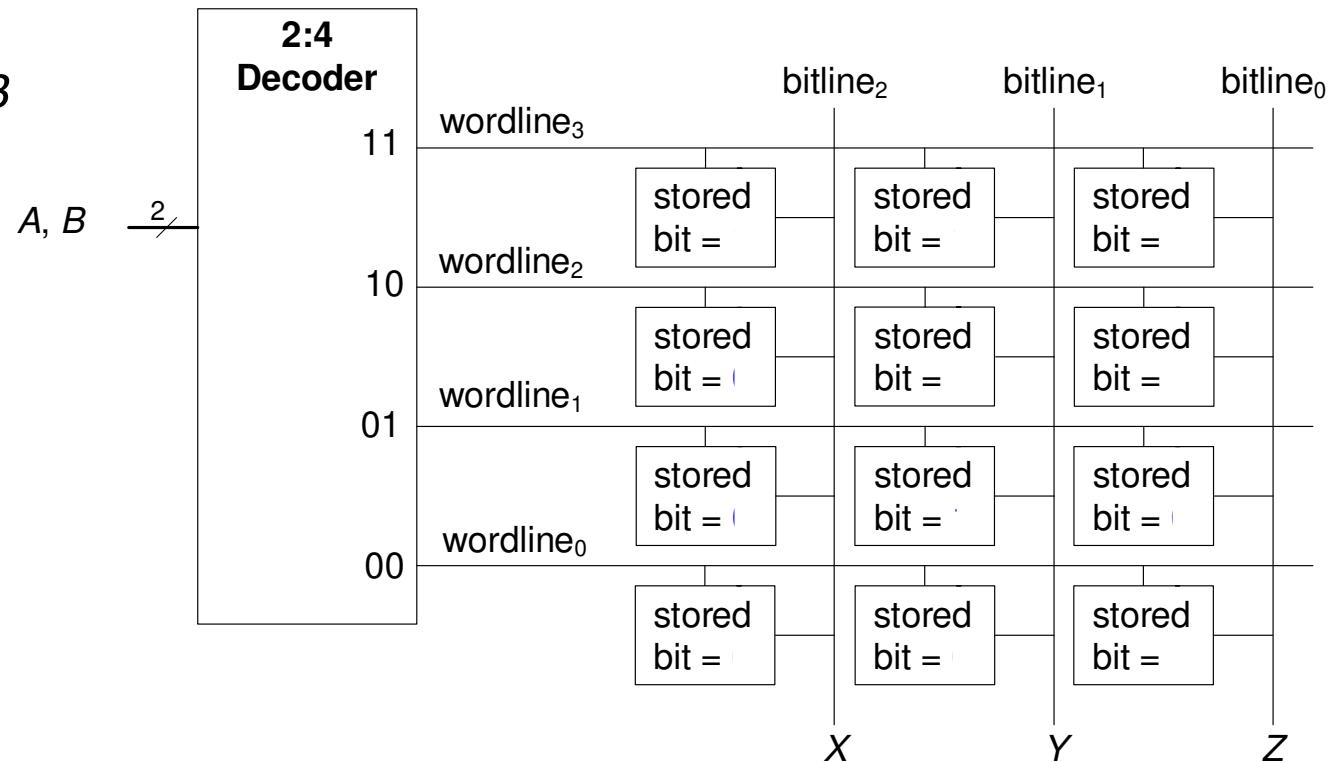
# Logic with Memory Arrays


Implement the following logic functions using a  $2^2 \times 3$ -bit memory array:

- $X = AB$
- $Y = A + B$
- $Z = A \overline{B}$


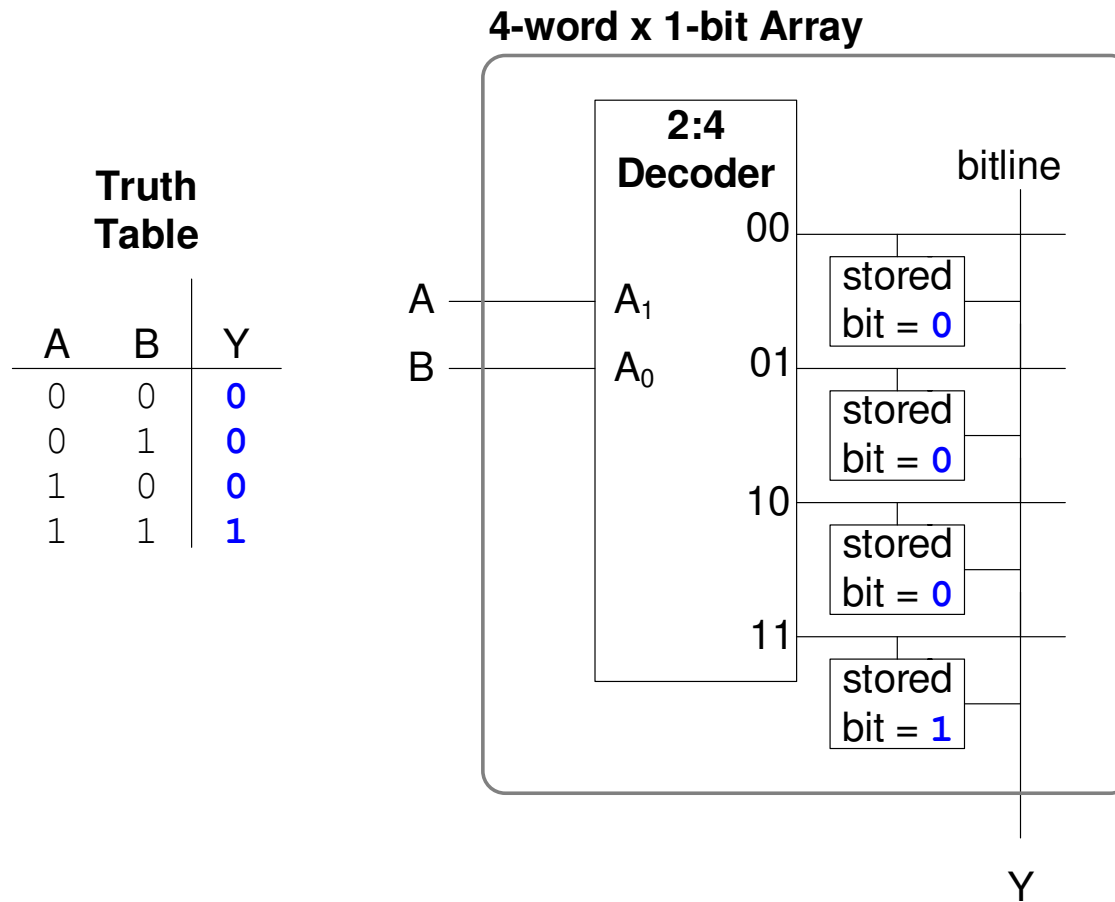
# Logic with Memory Arrays

Called *lookup tables* (**LUTs**): look up output at each input combination (address)



## Chapter 5: Digital Building Blocks

# **SystemVerilog & Multiported Memories**

# SystemVerilog RAM

```
// 256 x 3 RAM with one read/write port
module ram(input logic      clk, we,
           input logic [7:0] a,
           input logic [2:0] wd,
           output logic [2:0] rd);

    logic [2:0] RAM[255:0];

    assign rd = RAM[a];

    always @(posedge clk)
        if (we)
            RAM[a] <= wd;
endmodule
```

# SystemVerilog ROM

```
// 128 x 32 ROM with one read port
// Contents initialized from file
module rom(input  logic [6:0]  a,
           output logic [31:0] rd);

    logic [31:0] ROM[127:0];

    // initialize contents from file
    initial
        $readmemh("memfile.dat", ROM);


    // read port
    assign rd = ROM[a];
endmodule
```

# SystemVerilog ROM memfile

```
// memfile.dat
// Contains up to 128 lines of 32-bit hex numbers
// defining the contents of the ROM
01234567
89ABCDEF
FFFFFFFFF
A5A5A5A5
...
```
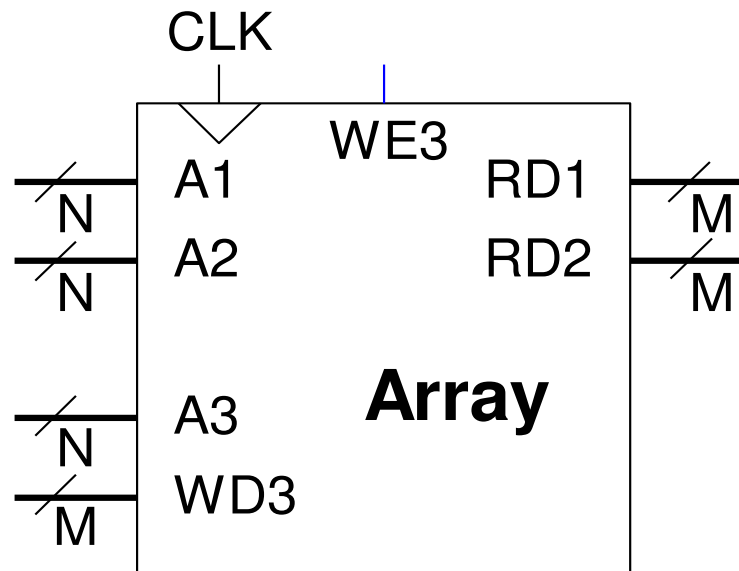
# Multi-ported Memories

- **Port:** address/data pair
- 3-ported memory
  - 2 read ports (A1/RD1, A2/RD2)
  - 1 write port (A3/WD3, WE3 enables writing)
- **Register file:** small multi-ported memory





# SystemVerilog Memory Arrays

```
// 32 x 32 register file with 2 read, 1 write port
// register 0 hardwired to read as 0
module regfile(input  logic          clk,
               input  logic          we3,
               input  logic [4:0]    ra1, ra2, wa3,
               input  logic [31:0]   wd3,
               output logic [31:0]   rd1, rd2);

    logic [31:0] rf[31:0];

    always_ff @(posedge clk)
        if (we3) rf[wa3] <= wd3;

    assign rd1 = (ra1 == 5'b00000) ? 32'b0 : rf[ra1];
    assign rd2 = (ra2 == 5'b00000) ? 32'b0 : rf[ra2];
endmodule
```

# Chapter 5: Digital Building Blocks


## **Logic Arrays: PLAs & FPGAs**

# Logic Arrays

- **PLAs** (Programmable logic arrays)
  - AND array followed by OR array
  - Combinational logic only
  - Fixed internal connections
- **FPGAs** (Field programmable gate arrays)
  - Array of Logic Elements (LEs)
  - Combinational and sequential logic
  - Programmable internal connections

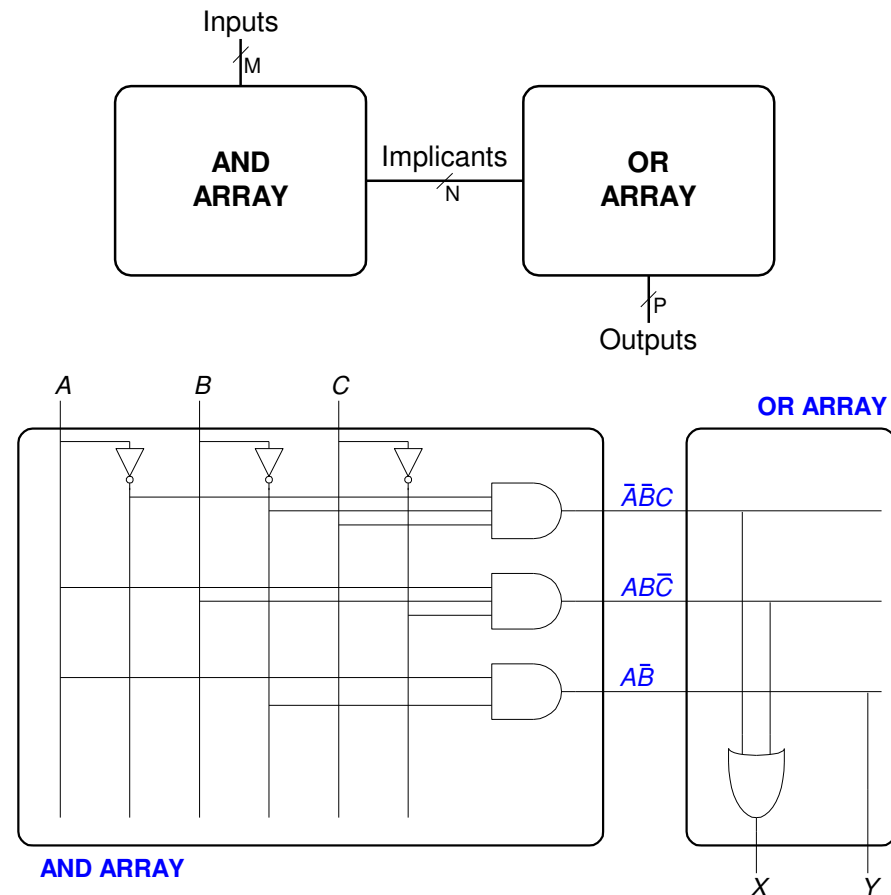
# PLAs: Programmable Logic Arrays

- $X = \bar{A}\bar{B}C + A\bar{B}\bar{C}$
- $Y = A\bar{B}$



# PLAs: Dot Notation


- $X = ABC + \bar{A}BC$
- $Y = AB$

 

# FPGAs: Field Programmable Gate Arrays

- Composed of:
  - **LEs** (Logic elements): perform logic
  - **IOEs** (Input/output elements): interface with outside world
  - **Programmable interconnection:** connect LEs and IOEs
  - Some FPGAs include other building blocks such as multipliers and RAMs

# General FPGA Layout

 


# LE: Logic Element

- Composed of:
  - **LUTs** (lookup tables): perform combinational logic
  - **Flip-flops**: perform sequential logic
  - **Multiplexers**: connect LUTs and flip-flops



# Altera Cyclone IV LE

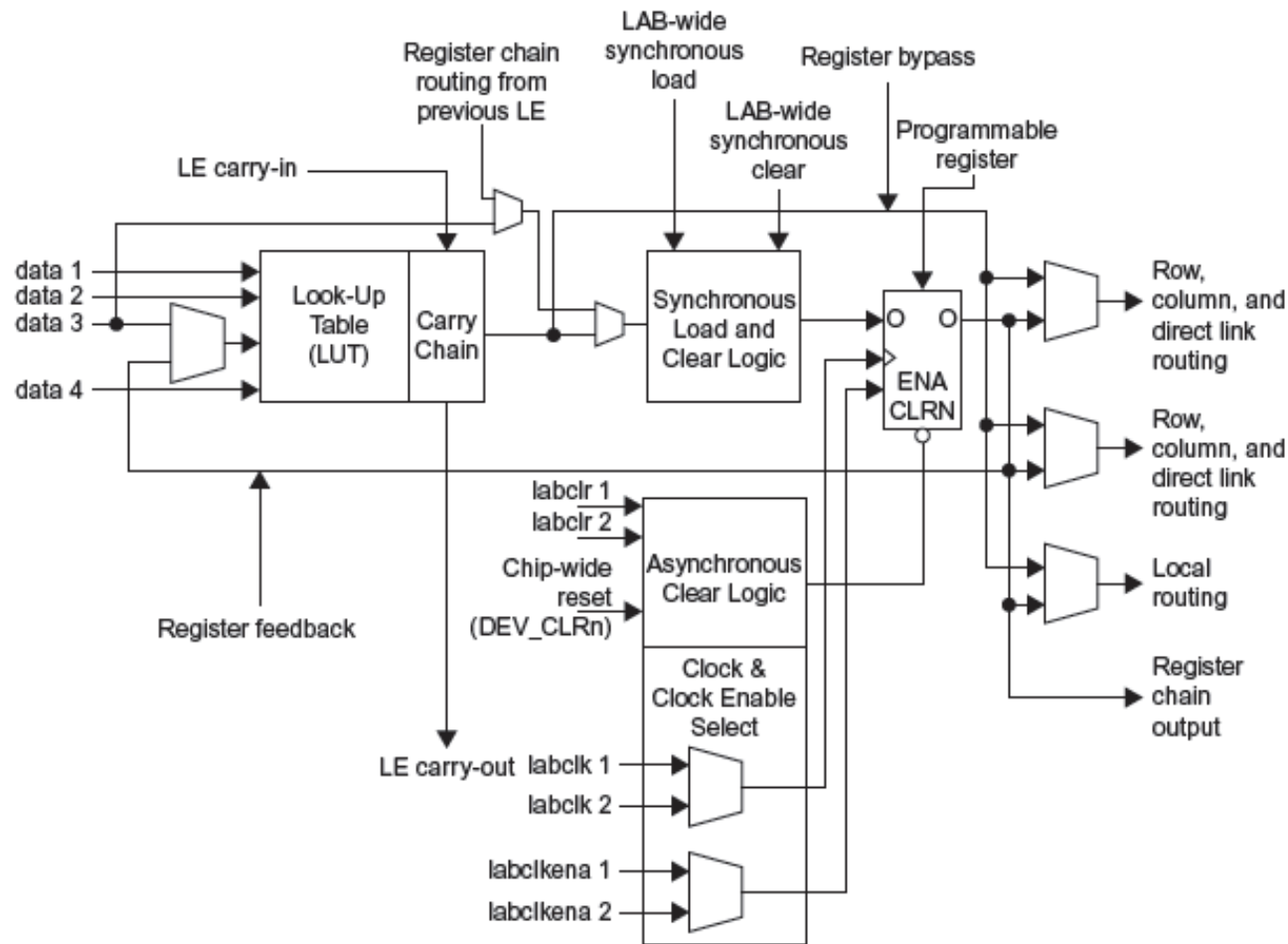

*From Cyclone IV datasheet*

# Altera Cyclone IV LE

- **The Altera Cyclone IV LE has:**
  - 1 four-input **LUT**
  - 1 **registered output**
  - 1 **combinational output**

# LE Configuration Example

Show how to configure a Cyclone IV LE to perform the following functions:

- $X = \overline{A}\overline{B}C + A\overline{B}C$
- $Y = A\overline{B}$

# Logic Elements Example 1

How many Cyclone IV LEs are required to build

$$Y = A1 \oplus A2 \oplus A3 \oplus A4 \oplus A5 \oplus A6$$

**Solution:**

# Logic Elements Example 2

How many Cyclone IV LEs are required to build

32-bit 2:1 multiplexer

**Solution:**

# Logic Elements Example 3

How many Cyclone IV LEs are required to build

Arbitrary FSM with 2 bits of state, 2 inputs, 3 outputs

**Solution:**

# FPGA Design Flow

Using a CAD tool (such as Altera's Quartus II)

- **Enter the design** using schematic entry or an HDL
- **Simulate** the design
- **Synthesize** design and map it onto FPGA
- **Download the configuration** onto the FPGA
- **Test** the design

# About these Notes

**Digital Design and Computer Architecture Lecture Notes**

**© 2021 Sarah Harris and David Harris**

**These notes may be used and modified for educational and/or non-commercial purposes so long as the source is attributed.**